

Transistor Sizing

Logical Effort



Lecture 7

18-322 Fall 2003

Textbook: [5.1, 5.2, 6.1, 6.2-6.2.1]


Overview



- Static CMOS circuit design
 - ▣ Transistor sizing
 - ▣ For symmetrical response
 - ▣ For performance
 - ▣ Large Fanin gates
 - ▣ Chains of logic gates

- Logical effort introduction

Transistors Everywhere...

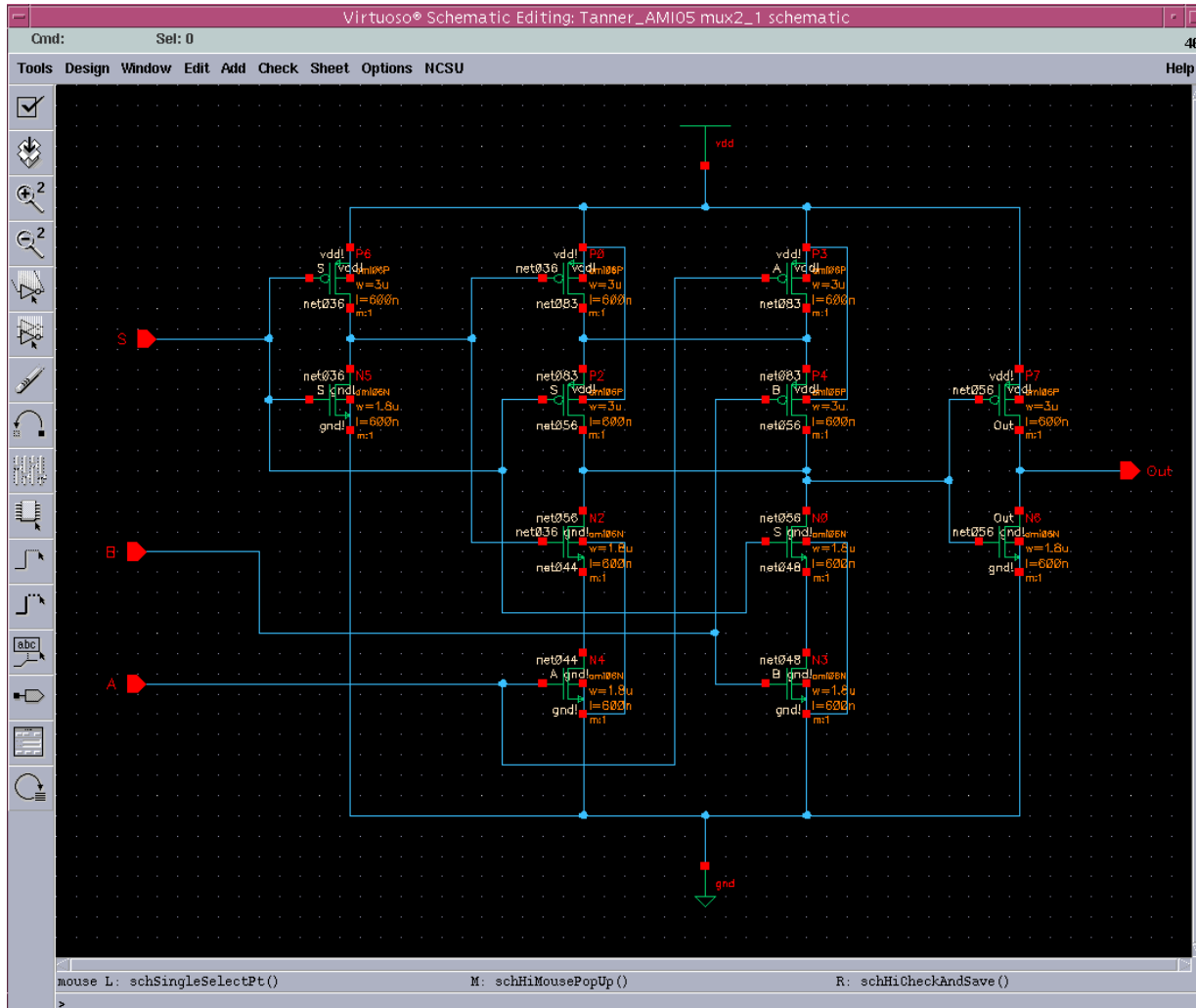


■ Node centric perspective

- Focus on devices and their properties (today)

■ Network centric perspective

- Focus on interconnects (next lectures)

The MOS Transistor

 

It is very difficult to design modern transistors. Calculations with

What is a Transistor?




$$R_n = \frac{1}{\mu_n C_{ox} (V_{GS} - V_{Tn})} \left(\frac{L}{W} \right)$$

$$C_{ox} = \epsilon_{ox} / t_{ox} \text{ oxide capacitance [F/cm}^2\text{]}$$

$$\beta_n = \mu_n C_{ox} \left(\frac{W}{L} \right) = k'_n \left(\frac{W}{L} \right) \quad \text{device transconductance [A/V}^2\text{]}$$

$$C_G = C_{ox} (WL) \quad \text{gate capacitance [F]}$$

  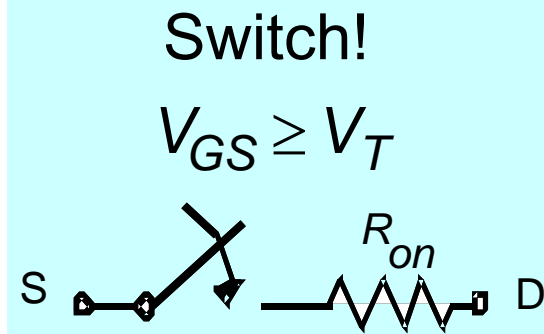Increasing W decreases the resistance which allows more current to flow!



What is Different Between nFET and pFET?

$$R_n = \frac{1}{\beta_n (V_{DD} - V_{Tn})}$$

$$\beta_n = \mu_n C_{ox} \left(\frac{W}{L} \right)_n$$


$$R_p = \frac{1}{\beta_p (V_{DD} - |V_{Tp}|)}$$

$$\beta_p = \mu_p C_{ox} \left(\frac{W}{L} \right)_p$$


$$\frac{\mu_n}{\mu_p} = r \quad \text{typically } (2 \dots 3)$$

Balancing Rise and Fall Time


■ Inverter

 

charging
 V_{out} rising

 


discharging
 V_{out} falling

 


If $(W/L)_p = r (W/L)_n$ then $\beta_n = \beta_p$ ($R_n = R_p$) \rightarrow symmetrical inverter

Make PMOS bigger (wider) by r times

FET Sizing and the Unit Transistor

 


 - The electrical characteristics of transistors determine the switching speed of a circuit
 - Need to select the aspect ratios $(W/L)_n$ and $(W/L)_p$ of every FET in the circuit






- Define the *unit transistor* (R_1, C_1)
 - L/W_{\min} -> highest resistance (needs scaling)
 - $R_2 = R_1/2$ and $C_2 = 2C_1$
 - Separate nFET and pFET unit transistors
 - Unit devices are *not* restricted to individual transistors (see next example)


Scaling of Series-Connected FET Chains

 

Transistor Resistance Model

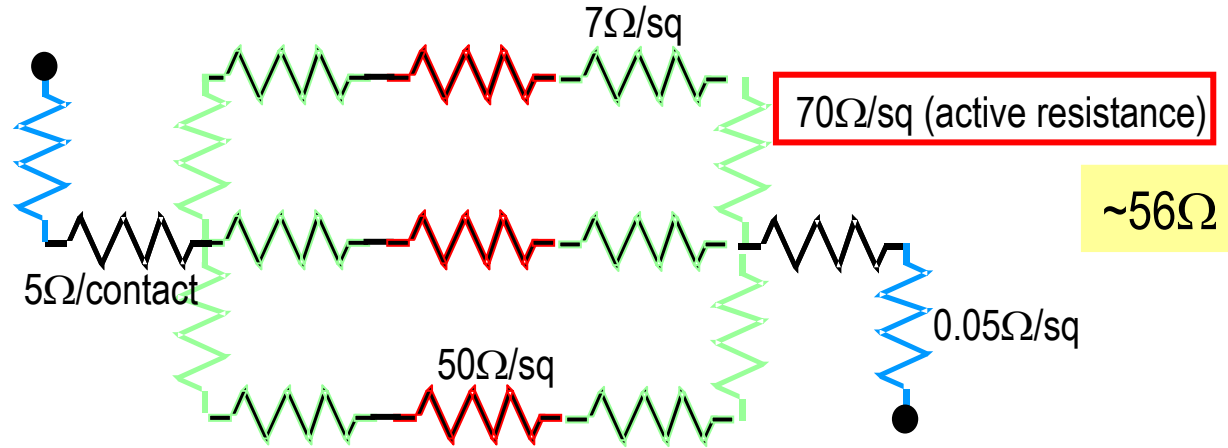 
 


$\sim 56\Omega$

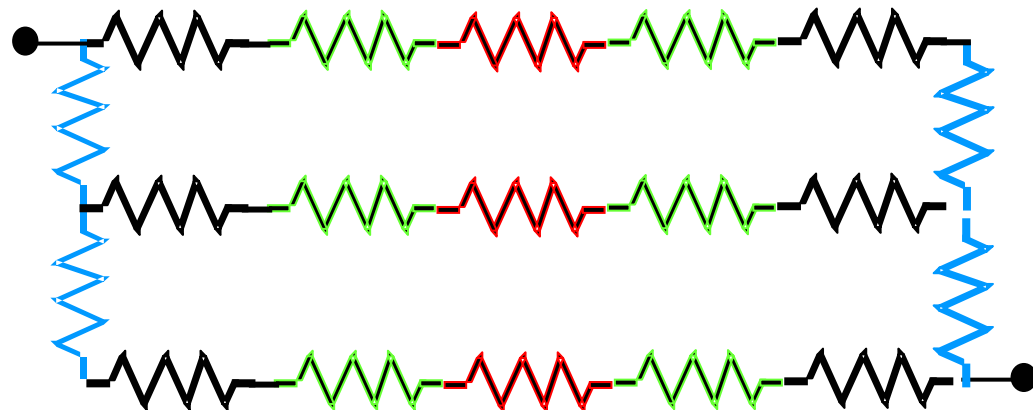

$\sim 25\Omega$
Better reliability

Transistor Capacitance Model


 
 


$$C_S = C_{GS} + C_{SB}$$

$$C_D = C_{GD} + C_{DB}$$

Capacitances increase with channel width!

Inverter Propagation Delay

   

$$t_{pf} = \ln 2 (R_n C_L) = 0.69 (R_n C_L)$$


$$t_{pr} = \ln 2 (R_p C_L)$$

$$t_p = \frac{1}{2} (t_{pf} + t_{pr})$$


- $W_p = 2W_n$ (symmetrical design)
 - approx. equal resistances $R_n = R_p$
 - approx. equal rise and fall delays

- $t_p \sim 1/(\beta V_{DD}) C_L \rightarrow$ minimize load, increase width of the driving transistor, increase V_{DD} ???


Symmetrical Inverter

 

Larger pFET design

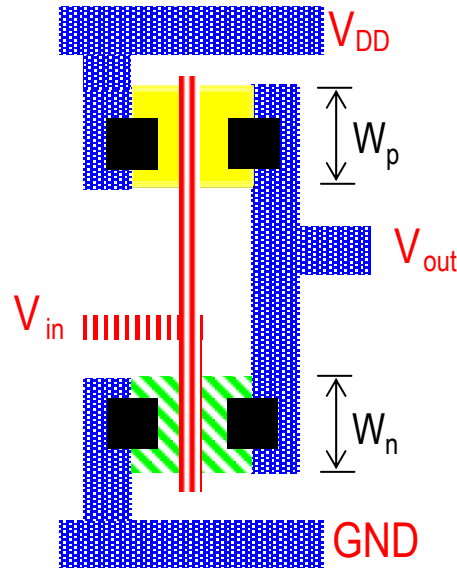


Equal aspect ratios

 


Dependence of V_M on the device ratio

$V_{DD} = 3\text{ V}$
 $V_{Tn} = +0.7\text{ V}$
 $V_{Tp} = -0.7\text{ V}$

 Propagation Delay Analysis - The Switch Model




(a) Inverter

 

(b) 2-input NAND


$$t_p = 0.69 R_{on} C_L$$

(assuming that C_L dominates!)

 

(c) 2-input NOR

Analysis of Propagation Delay

 

2-input NAND


1. Assume $R_n=R_p$ = resistance of minimum sized NMOS inverter
2. Determine “**Worst Case Input**” transition (Delay depends on input values)
3. Example: t_{pLH} for 2input NAND
 - Worst case when only ONE PMOS Pulls up the output node
 - For 2 PMOS devices in parallel, the resistance is lower

$$t_{pLH} = 0.69R_p C_L$$

4. Example: t_{pHL} for 2input NAND
 - Worst case : TWO NMOS in series

$$t_{pHL} = 0.69(2R_n)C_L$$

Transistor Sizing: NAND2

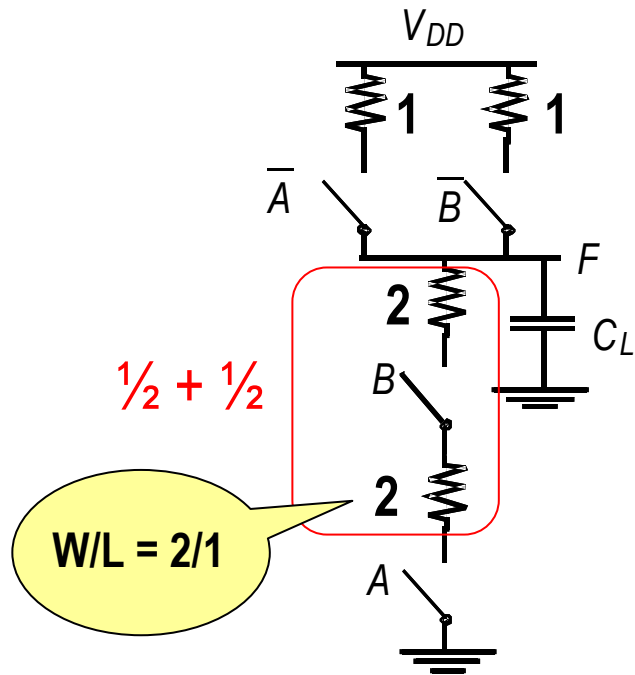


Input Dependent


Focus on worst-case

Here it is assumed that $R_p = R_n$

Designing for Worst-Case

 


Here it is assumed that $R_p = R_n$

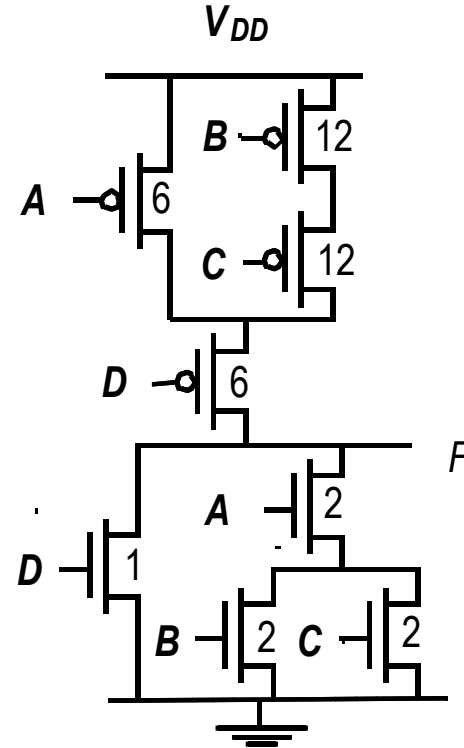


($W_p = 3W_n$ assumed)

Equivalent Inverter

 

$$\beta_{\text{series}} = \beta_n / 3$$

 
$$t_{\text{series}} = k \frac{C_L}{(\beta_n / 3) V_{DD}}$$



Big Fanin Gates



- So, how would NAND scale with fanin N
 - ☒ Assume all transistors are 1x
 - ☒ Rise time: best case $C_L R_p / N$, worst case: $C_L R_p$
 - ☒ Fall time: best/worst case $N C_L R_n$
 - ☒ Problem 1: Big fanin gates have big difference for rise and fall
 - ☒ Problem 2: The truth is actually worse than that

The Truth about Transistor Chains

 

- Series Transistors add series resistance
- Series Transistors also add Capacitance
- We'll talk about estimating delay of distributed RC on Thursday
- Result: Quadratic, not linear relationship of delay and fanin


t_p as a function of Fan-In

  

AVOID LARGE FAN-IN GATES! (Typically not more than $FI < 4$)

Chains of Gates

 
- Making W/L bigger decreases R_{on}
- Decreases t_{HL} or t_{LH}



- But wait! Doesn't increased W increase capacitance


The Big Trade-off

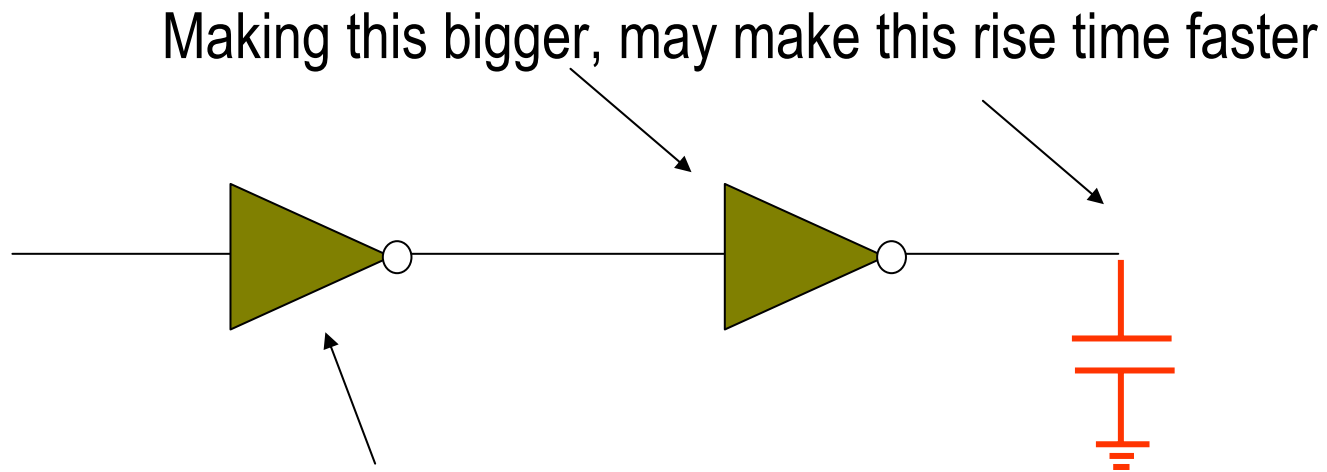- Making a gate bigger increases its output drive
- But also increases its input capacitance



But it makes this slower because it has to drive more load

How to Optimize?

 

$$\text{Delay} \sim 3 W C_n * R_n + 5C_n * R_n / W$$

How to optimize?

Summary



- Switching delays increase with the external load
- The layout geometries affect the transient response of logic gates
- Switching delays increase with the fan-in
- Increasing the “drive” of a gate increases the load to be driven by the previous gate

Overview



- ✓ Static CMOS circuit design
 - ⊞ Transistor sizing
 - ⊞ For symmetrical response
 - ⊞ For performance
- Logical effort

Logical Effort



- A way of thinking about **delay** in MOS circuits. It seeks to determine quickly a circuit's *maximum* possible speed and *how* to achieve it.
- Book: “*Logical effort: Designing fast CMOS Circuits*” by I. Sutherland, B. Sproull and D. Harris

Formula for Gate Delay (inverter)

$$t_p = 0.69 R_{eq} (C_{int} + C_{ext})$$

$$t_p = t_{p0} \left(1 + \frac{C_{ext}}{C_{int}} \right) \quad t_p = t_{p0} \left(1 + \frac{C_{ext}}{\gamma C_g} \right)$$

“intrinsic”: if $C_{ext} = 0$ C_{int} is linear with gate size

$$f = \frac{C_{ext}}{C_g} \quad f \text{ is "effective fanout"} \quad t_p = t_{p0} \left(1 + \frac{f}{\gamma} \right)$$

Definitions



- The logical effort of a logical gate is defined as the ratio of its input capacitance to that of an *inverter* that delivers equal output current.
 - ☒ How much worse a gate is at producing output current than an inverter, assuming inverter and gate have same input capacitance
 - ☒ How much more input capacitance a gate presents to deliver the same output current as an inverter
- Use inverter as the reference gate

Delay Formula for Complex Gates

$$t_p = t_{p0} \left(1 + \frac{f}{\gamma} \right) \quad \Rightarrow \quad t_p = t_{p0} \left(p + \frac{gf}{\gamma} \right)$$


g is logical effort

Assume PMOS 2x wider than NMOS in inverter gates

Rise time == Fall time


Gate	1 inp	2 inp	3 inp
INV	1		
NAND		4/3	5/3
NOR		5/3	7/3
XOR		4	12

Determining Logical Effort

 


$$C_{in} = 3$$

$$g = 1$$

 

$$C_{in} = 4$$

$$g = 4/3$$

 

$$C_{in} = 5$$

$$g = 5/3$$

Delay thru a Path of Gates

$$t_p = t_{p0} \sum_{i=1}^N \left(p_i + \frac{g_i f_i}{\gamma} \right)$$

to Optimize:

$$f_1 g_1 = f_2 g_2 = \dots = f_N g_N$$

Logical Effort (cont'd)




- Type of efforts
 - logical path effort ($G = \prod g_i$)
 - electrical path effort ($F = C_{out}/C_{in}$)
 - branching effort ($B = \prod b_i$)

- Path effort
 - $H = GFB$

Optimization

- N-stage logic network
- **Idea:** *The path delay is least when each stage in the path bears the same stage effort*
 - $h_i = g_i f_i = (H)^{1/N}$
- **Main result:** minimum delay achievable along a path
 - $\mathcal{D} = N (H)^{1/N} + P$ (where $P = \sum p_i$)
 - $C_{ini} = (1/f) g_i C_{outi}$ (**used for transistor sizing!**)
- The method of logical effort achieves an *approximate optimum!*

Example

 

$$G = (4/3)^3 = 2.37$$

$$B = 1$$

$$F = C/C = 1$$

$$H = 2.37$$

$$D = 3(2.37)^{1/3} + 3(2p_{inv}) = 10 \text{ delay units (min delay)}$$

$$f = (2.37)^{1/3} = 4/3 \text{ (this is the stage effort)}$$

$$z = C (4/3) / (4/3) = C$$

$$y = z (4/3) / (4/3) = C$$

(all 3 gates should have the same input capacitance)

Gate	1 inp	2 inp	3 inp
INV	1		
NAND		4/3	5/3
NOR		5/3	7/3
XOR		4	12

Gate	P
Inv	$P_{inv} = 1$
n-NAND	np_{inv}
n-NOR	np_{inv}
XOR	$4p_{inv}$