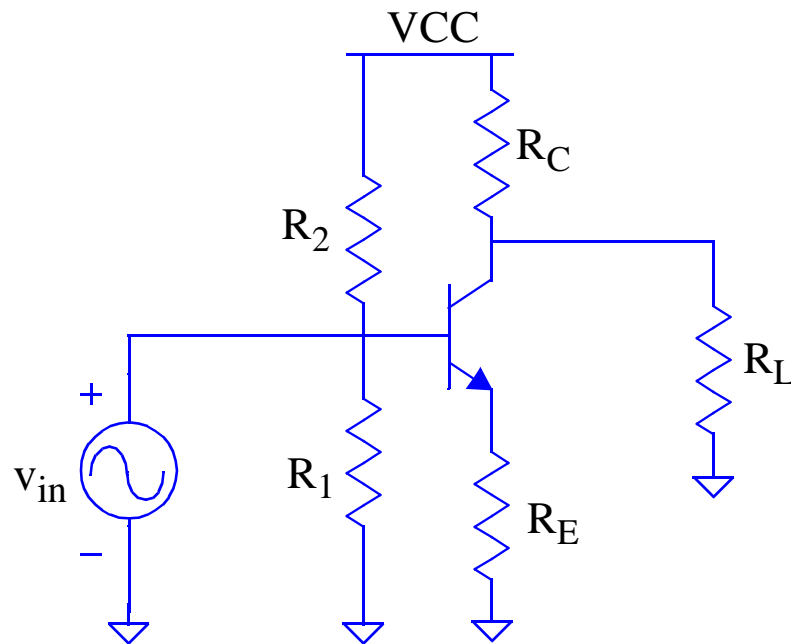



dc Bias Point Calculations

- Instead of supplying two dc voltages, the V_{BE} is generally established by a voltage divider using the V_{CC} supply
- But then the ac input cannot be attached as shown. Why?




Decoupling

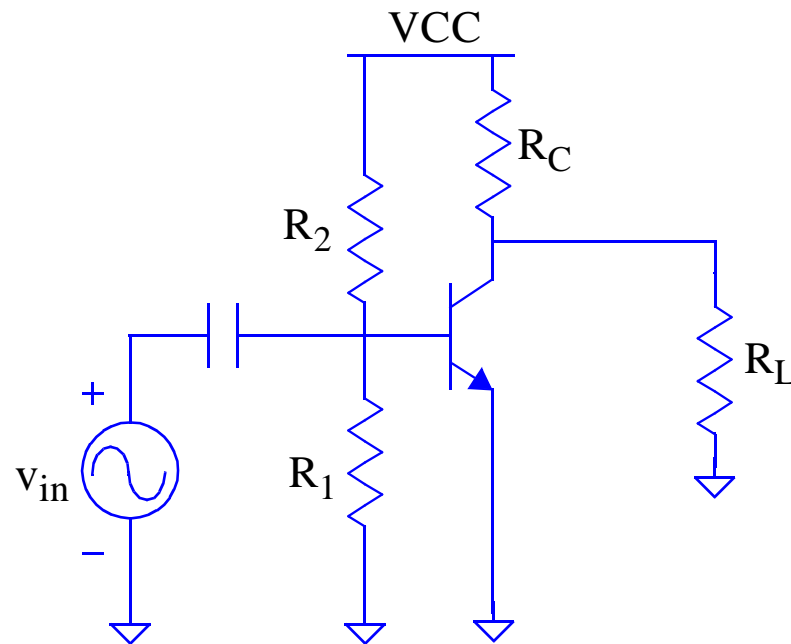- What is the advantage of adding decoupling to this circuit?




Output Decoupling

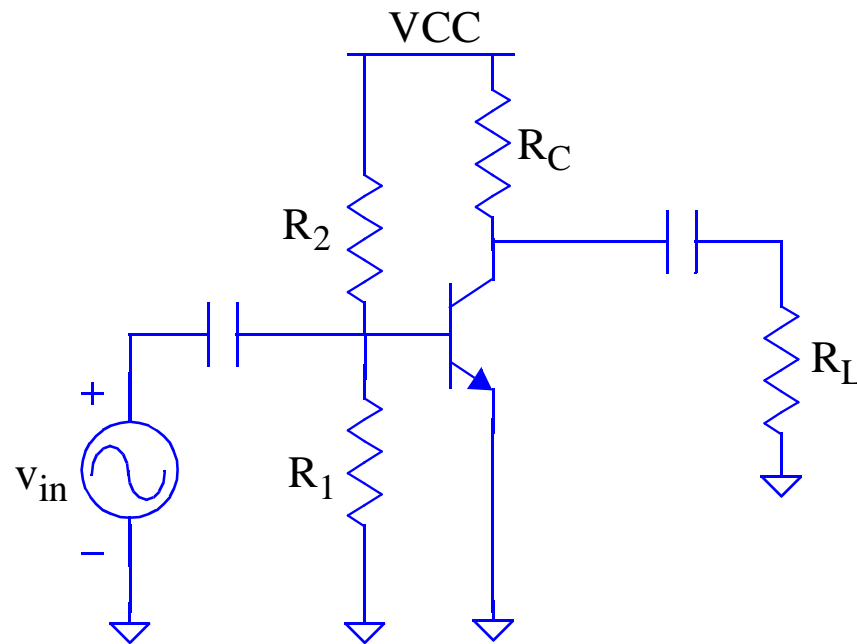- What would be the ideal values for these capacitors?
- How do we select the capacitor values?




PNP Amplifiers

- dc bias voltages are negative

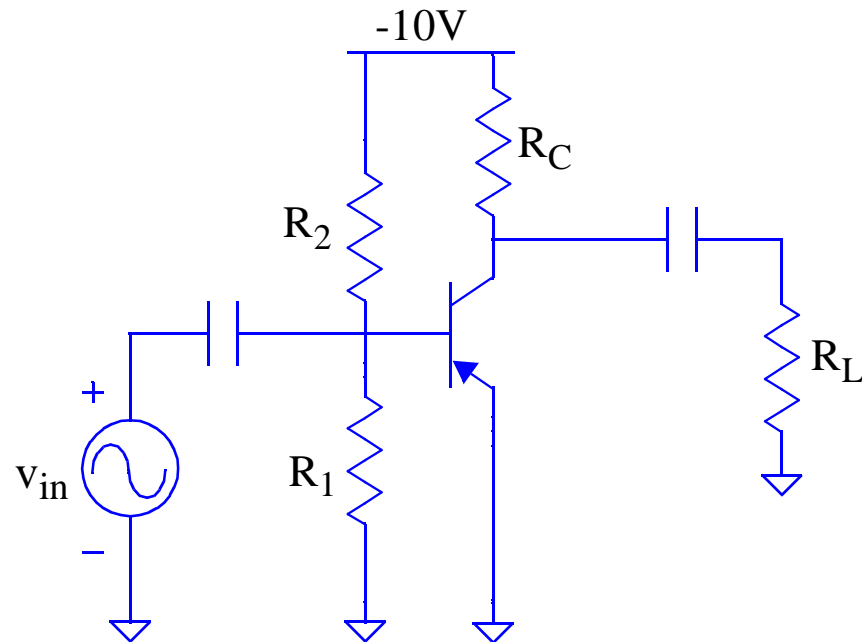


PNP Amplifiers

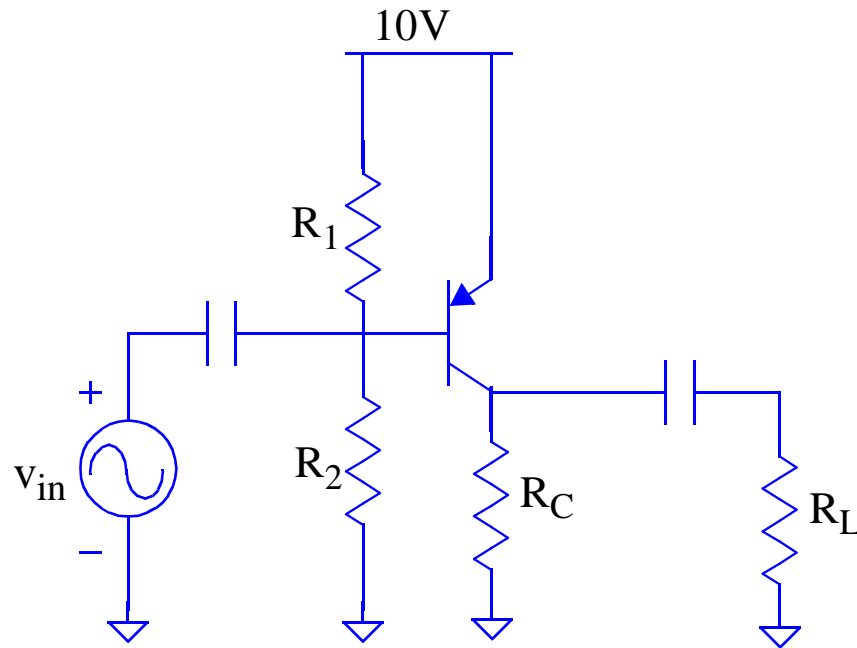- Which can also be designed by shifting all of the dc voltages by the same potential:




Decoupling and Biasing

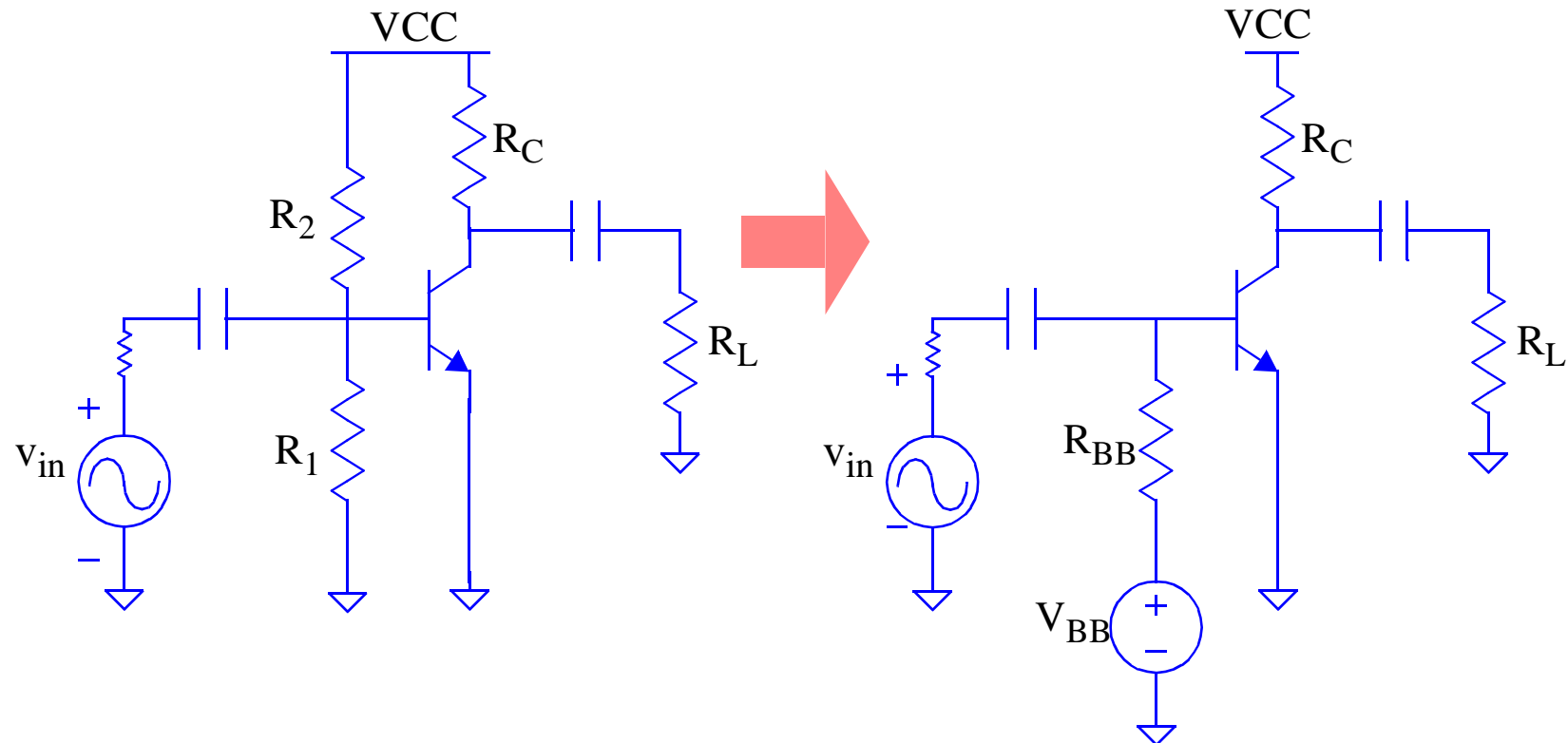- Decoupling also allows us to specify the effective base resistance, R_{BB} , independent of V_{in}




Decoupling and Biasing

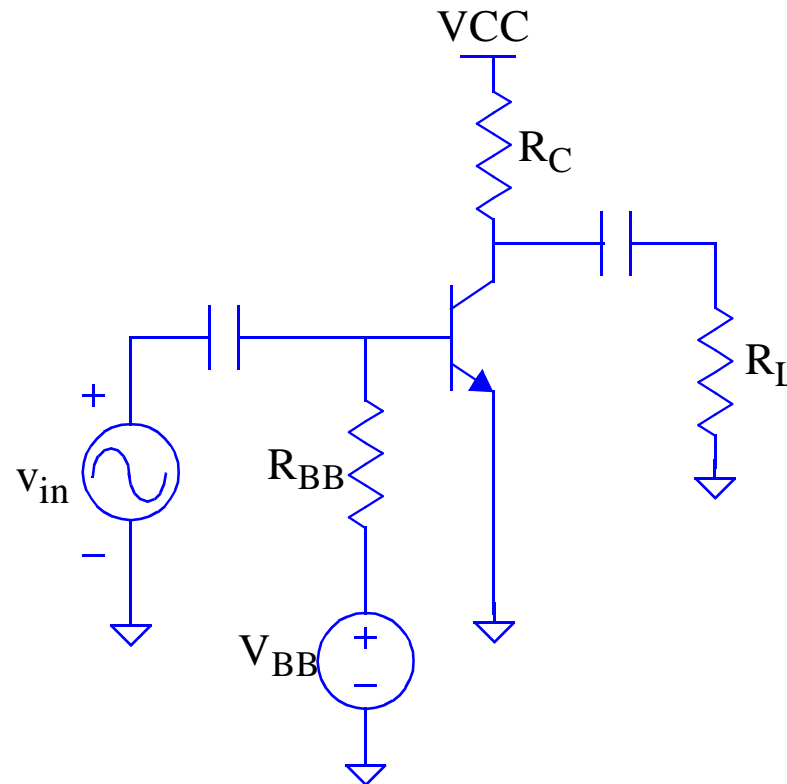- We'd like to have $V_{BB} \gg V_{BE}$ so that the currents are not overly dependent on V_{BE} . Why is this dependency undesirable?
- But what is the problem with a large V_{BB} ?




SPICE

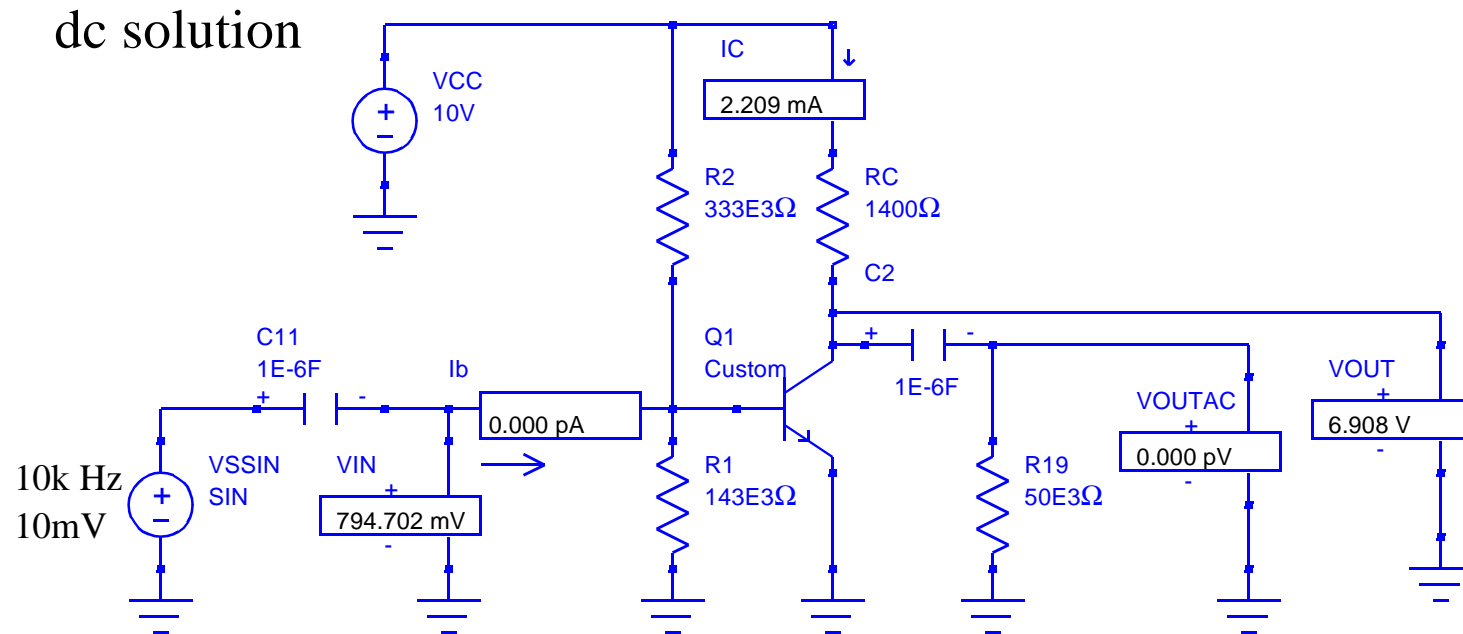- Discrete amplifier design rules of thumb: select bias point so that the expected ac signal can swing from max to min without clipping at the supply or forcing the transistor into saturation




SPICE

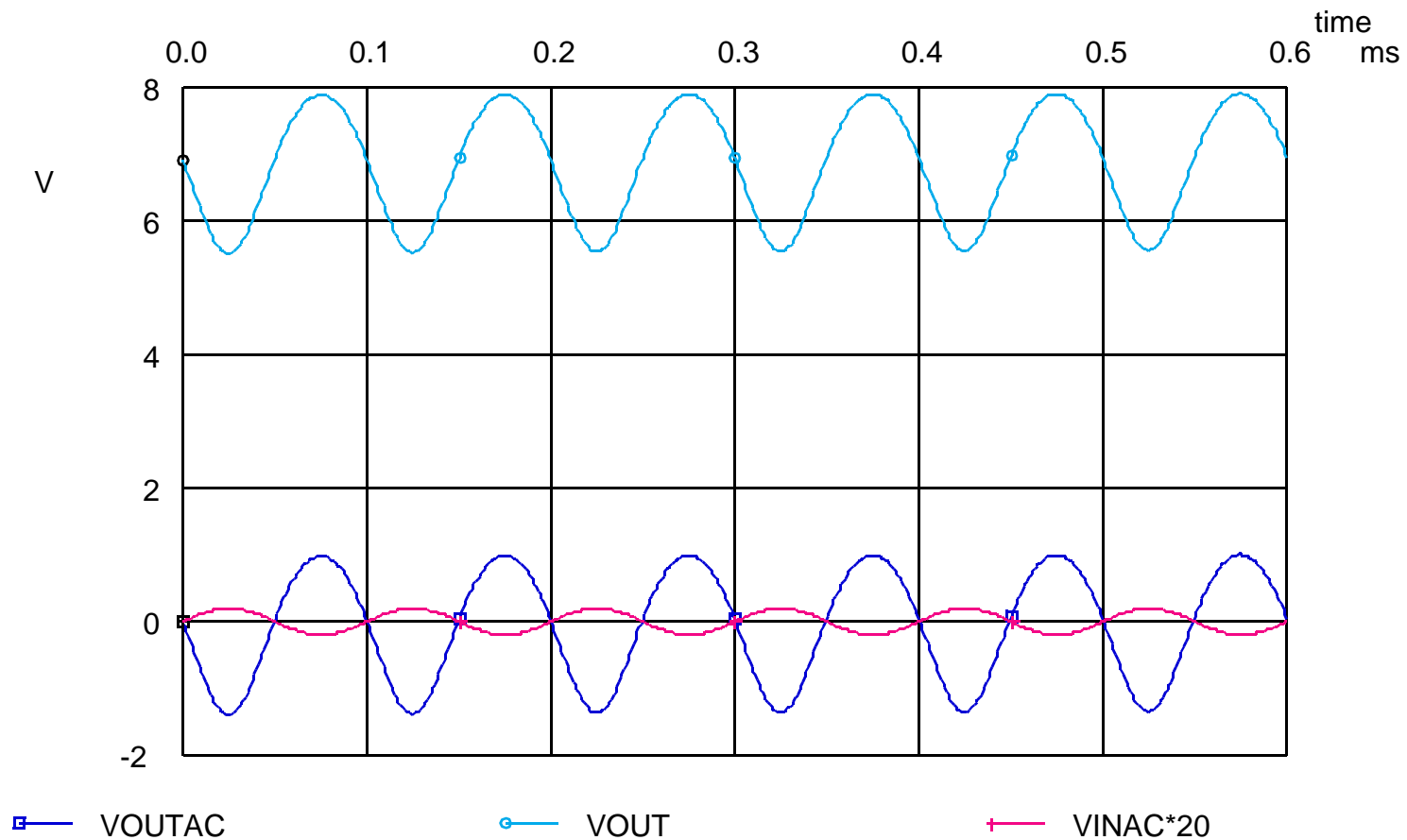- The $1\mu\text{F}$ capacitors are nearly perfect at decoupling the input and output dc signal components at this 10kHz frequency




SPICE

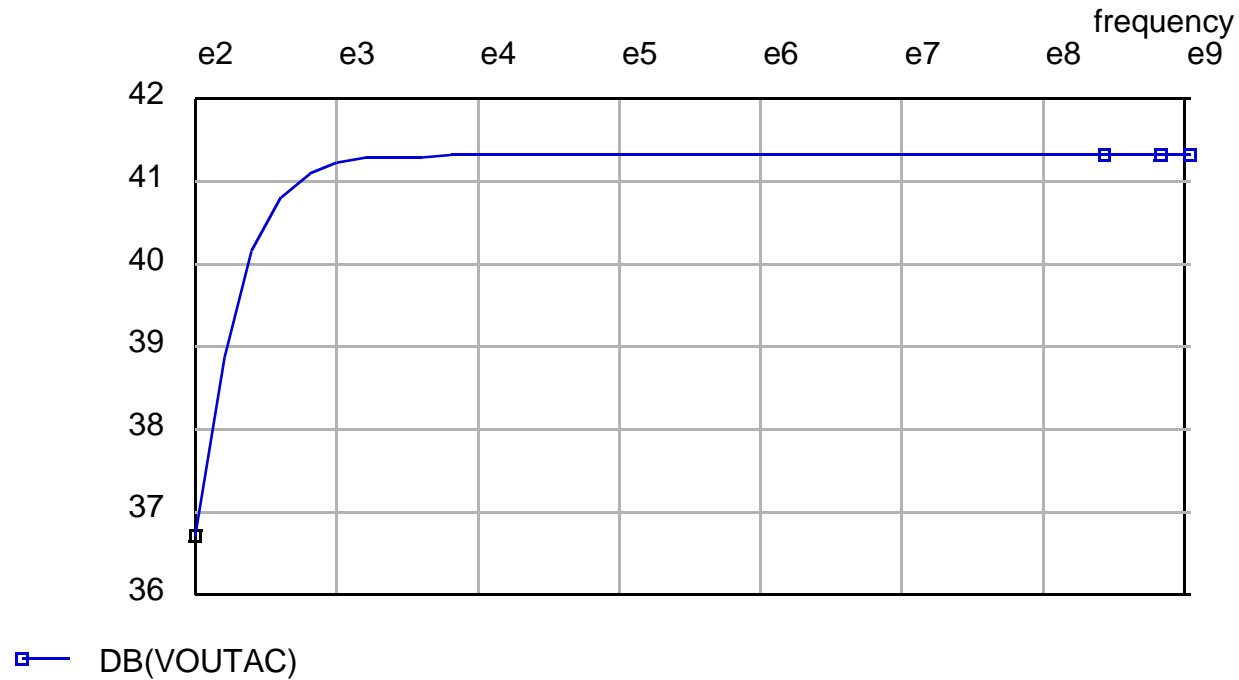- Decoupling is evident from the frequency response
- Decoupling would cause distortion at low frequency




SPICE

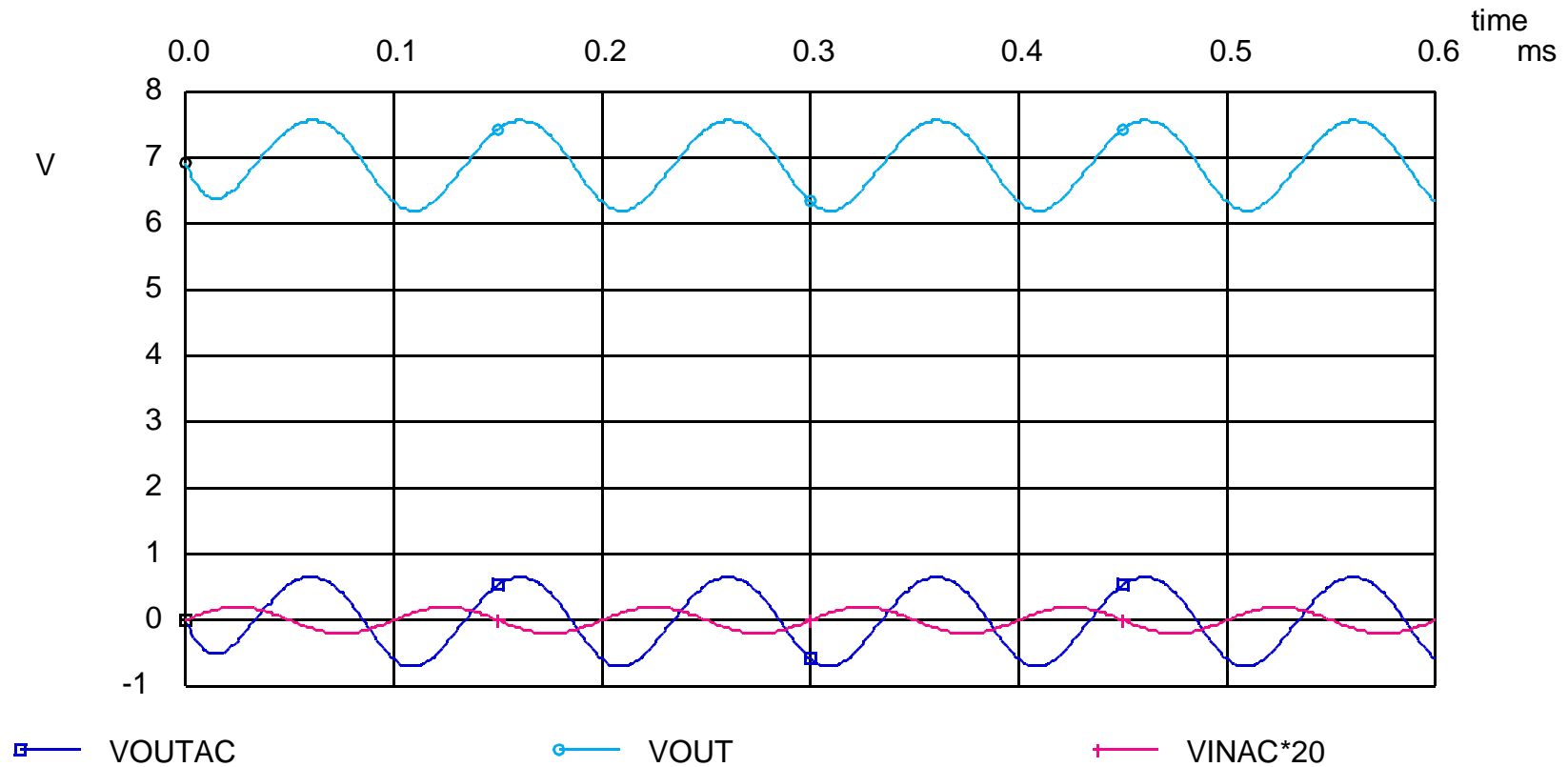- For smaller decoupling C's (10nF) we will see some distortion even at 10kHz



SPICE

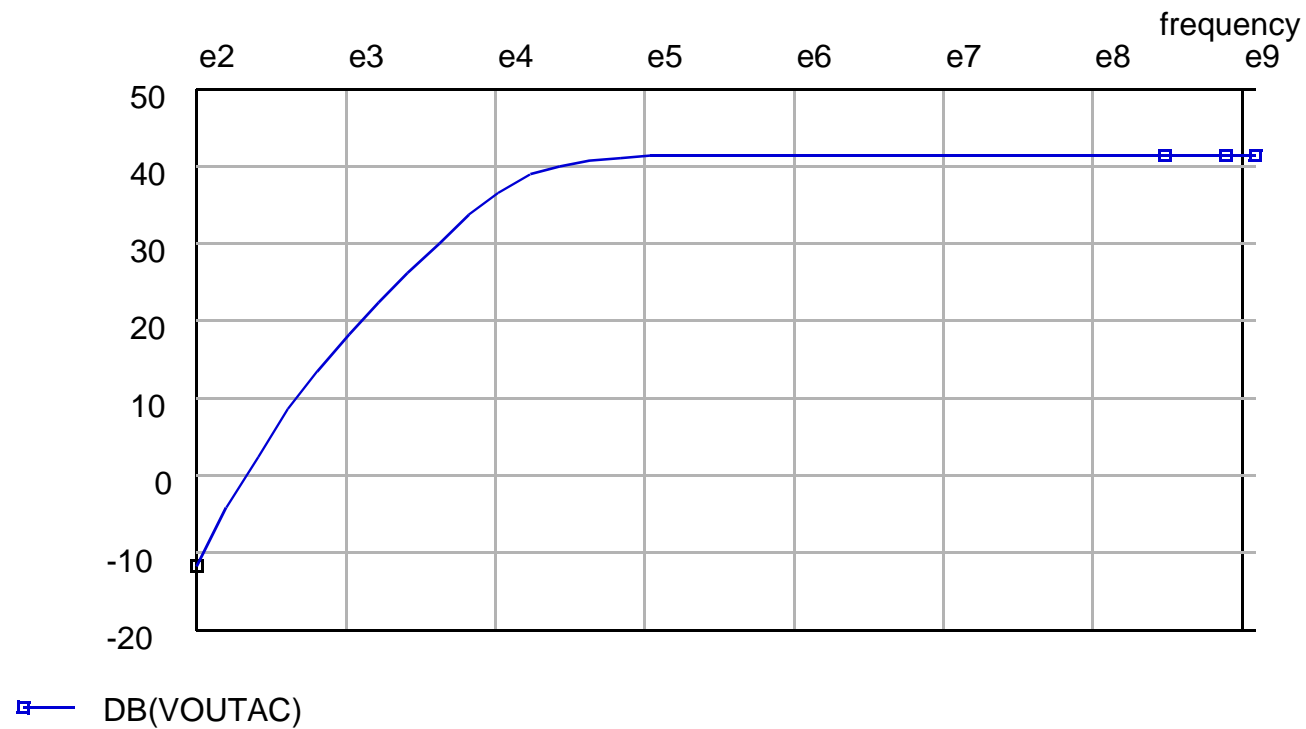- Frequency response with 10nF decoupling C's



Controlling Parameter Variations

- The current gain, β , varies with temperature
 - *Recombination greatly depends on temperature*
- Recombination also depends on the *injection level* (magnitude of current)
- An emitter resistor, R_E is used as negative feedback to reduce the β -variation effect on I_C


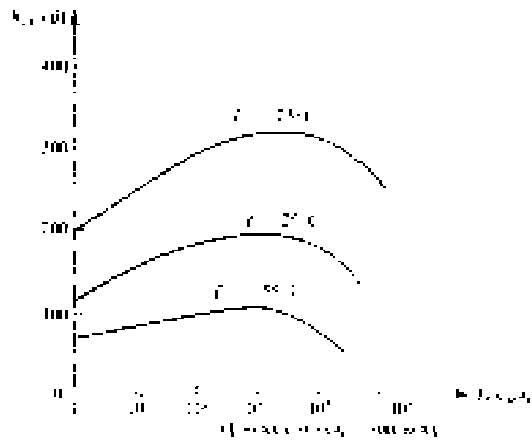



Figure 14-1 Typical dependence of I_C on temperature in a common-emitter amplifier. V_{in} is assumed to be zero and β is assumed to be constant.

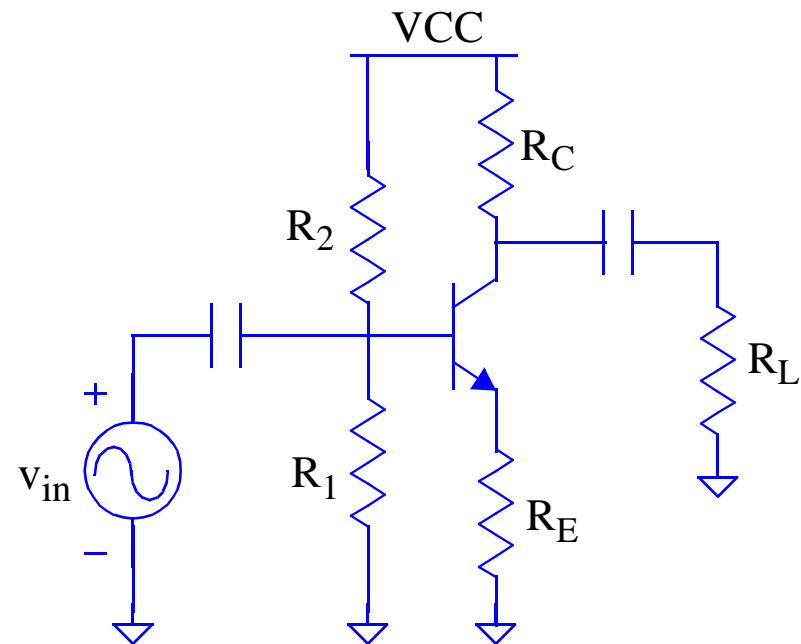

Controlling Parameter Variations


- Make R_{BB} small enough that the base voltage is roughly independent of base current so that R_E feedback can be most effective
 - But why not too small?

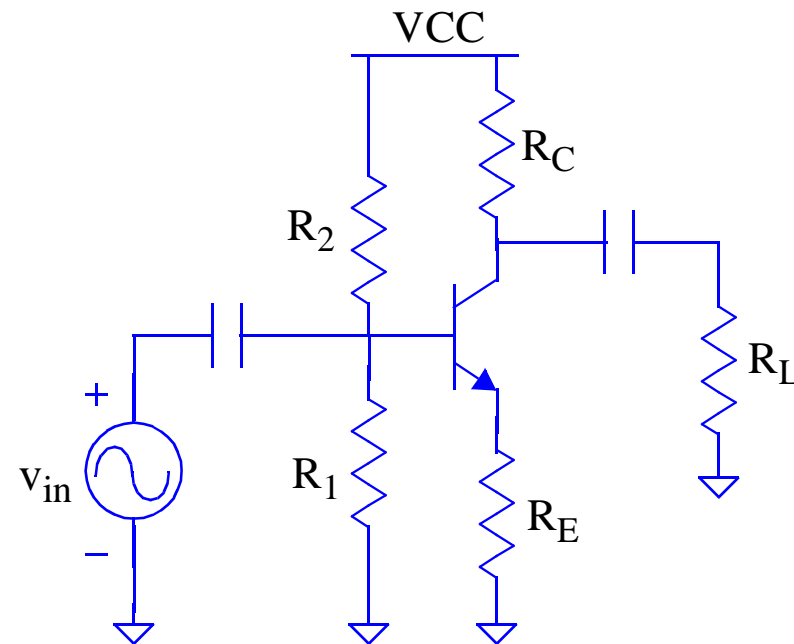- If base voltage is nearly constant, an increase in current due to β -variation will tend to decrease V_{BE} because of R_E



Universal Amplifier Configuration

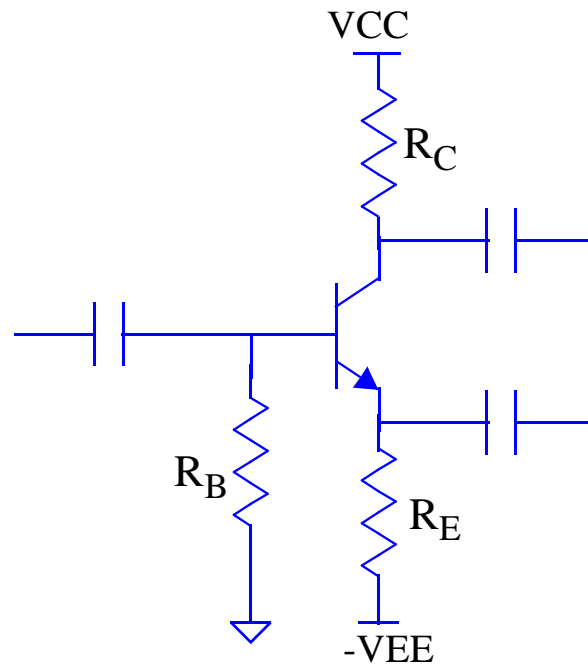
- Dual supplies for generality, makes base biasing simpler



- Use decoupling for input and output signals
- But what does the capacitor at the emitter do?


Decoupling Capacitors

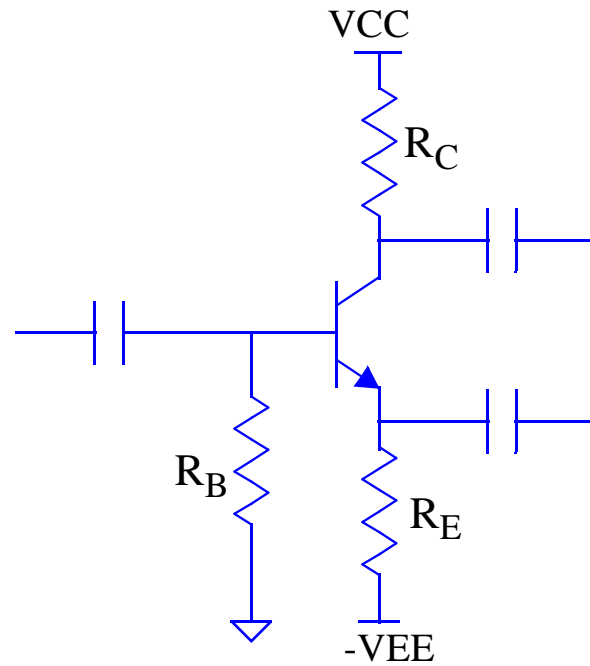- Decoupling C's are generally used only for **discrete design** since it is difficult to build a large capacitor on a chip
- **Direct coupled amplifiers** are generally used on ICs, but they are similar in form to the amplifiers that we will study here




Common Emitter Amplifier

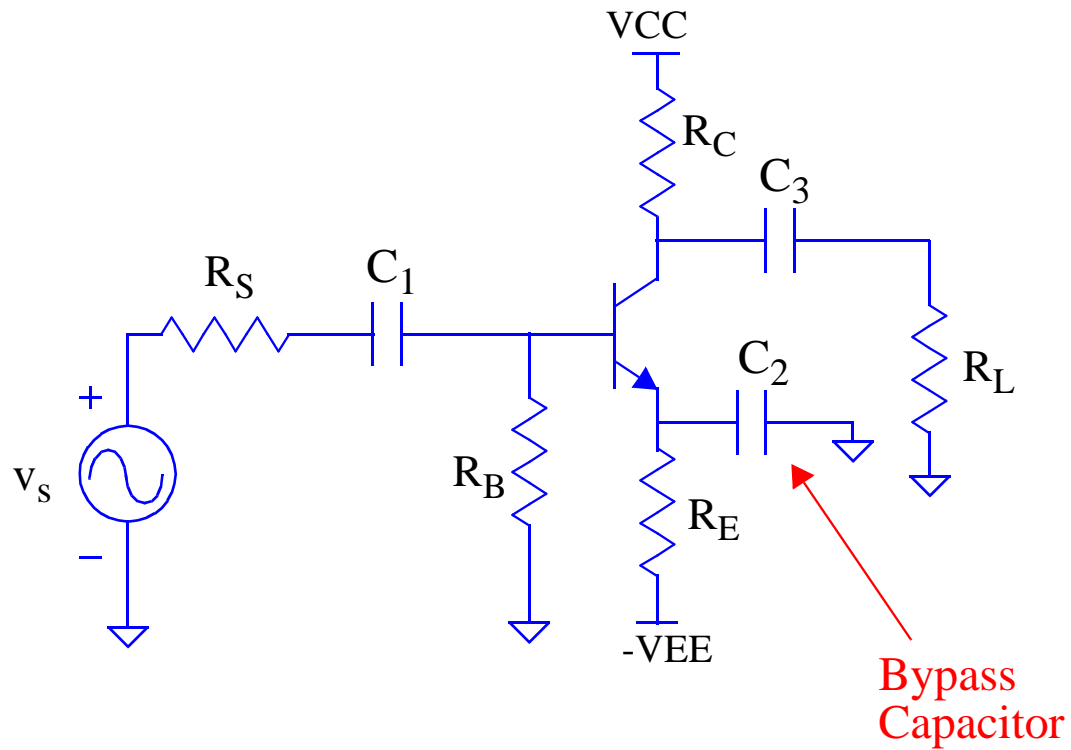- Popular discrete-component amplifier configuration




Common Emitter Design Example

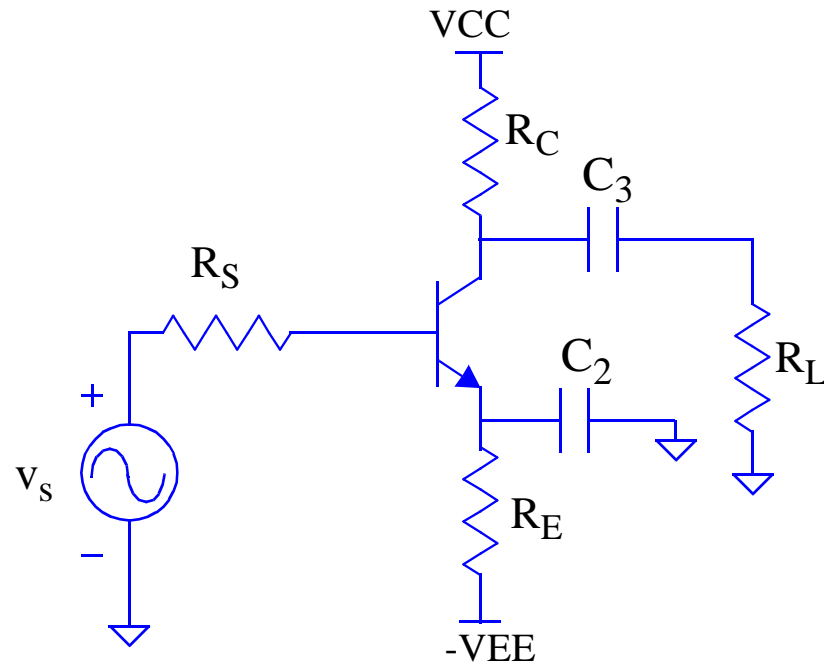- If there is no dc component in v_{in} , then we don't need C_1 or R_B with $-VEE$.




Common Emitter Design Example

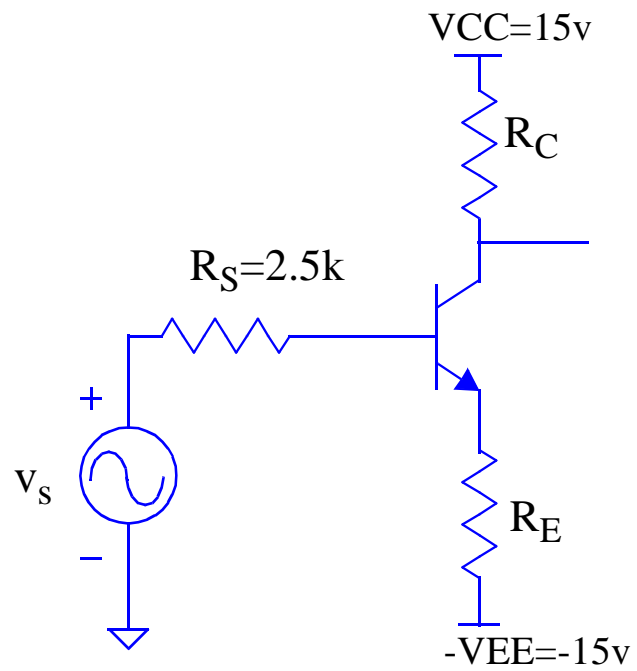

Common Emitter Design Example

Common Emitter Design Example

SPICE dc Analysis

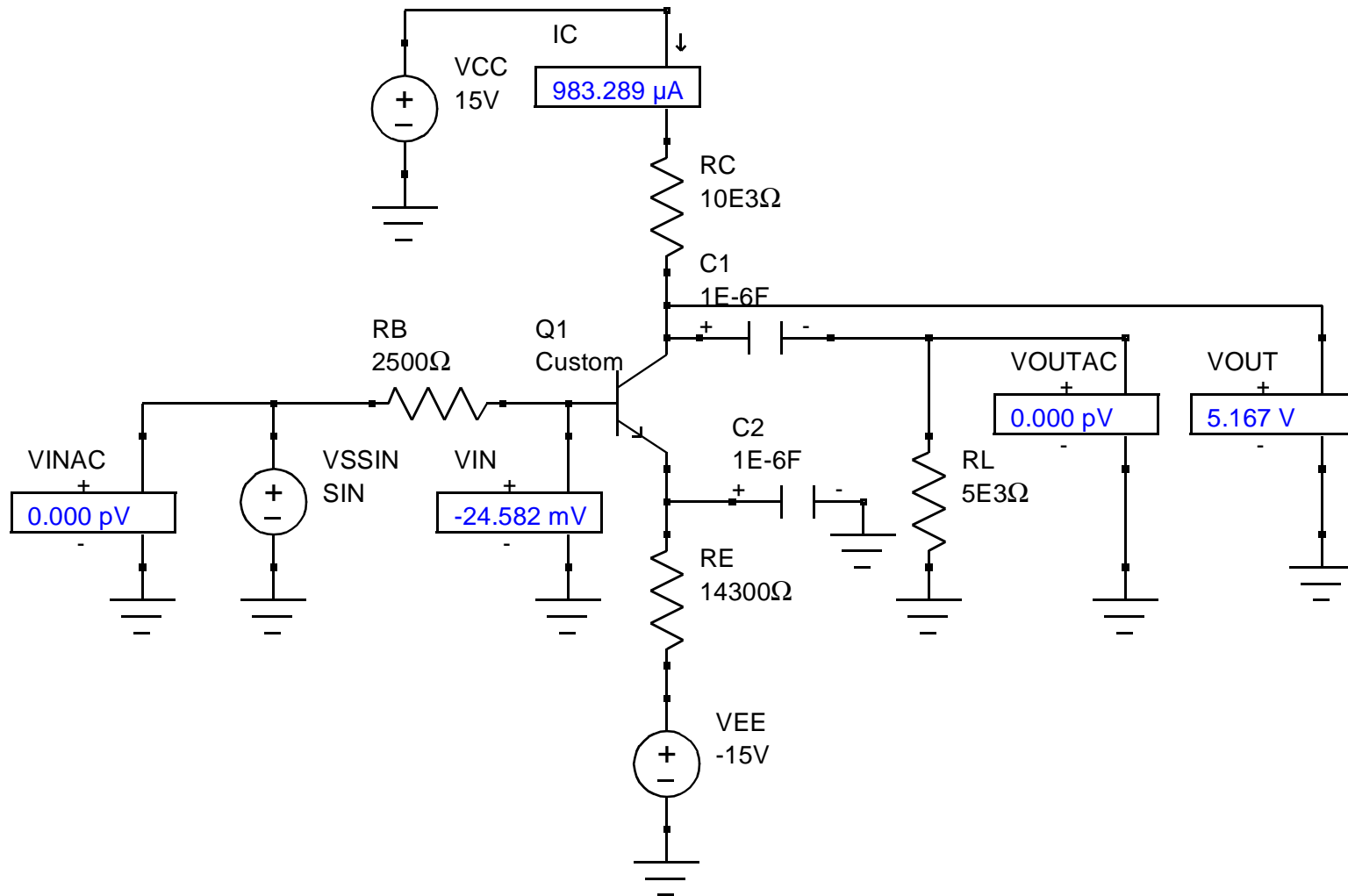

SPICE ac Analysis

