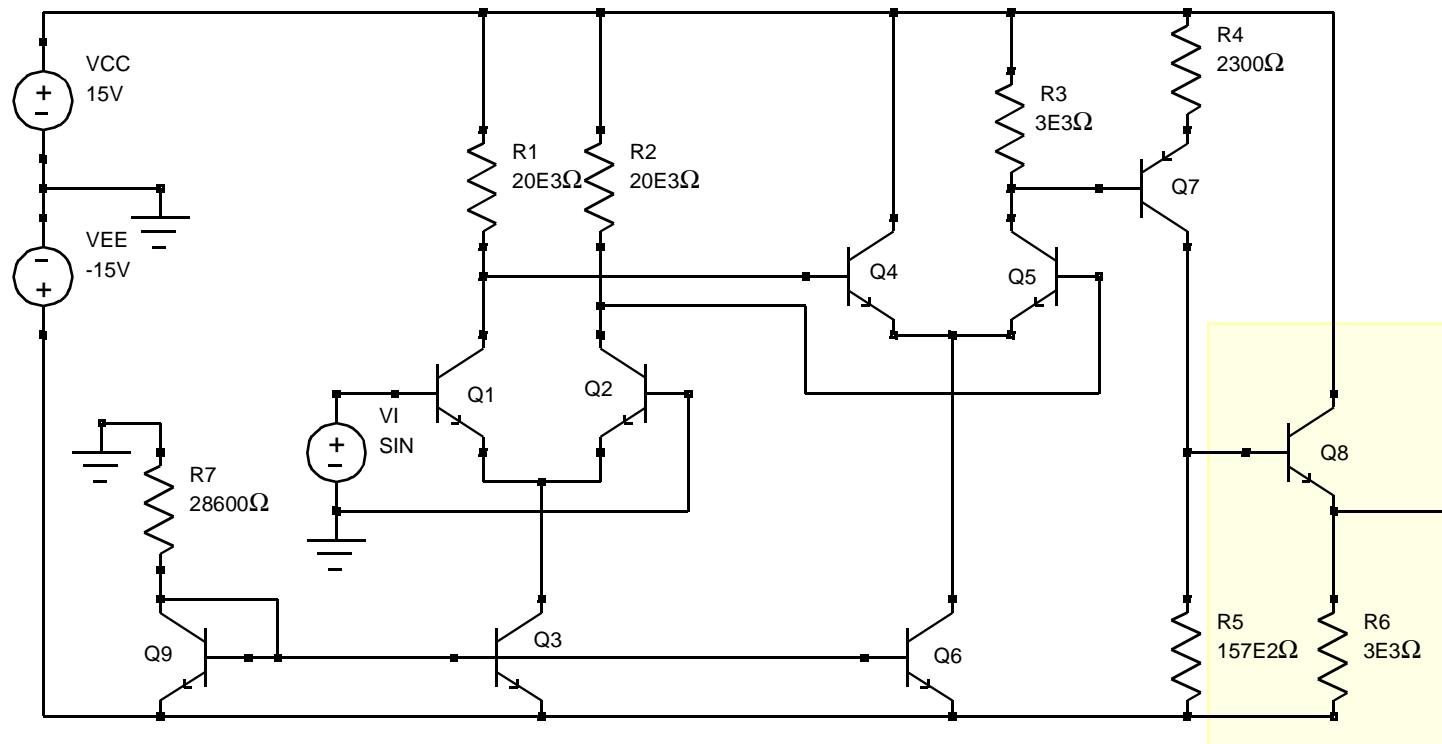


# Output Stages

- Output stage must deal with large signal swings
- Small signal model assumption is not valid, but emitter follower behaves *somewhat linearly*
- Emitter follower is not power efficient



# Output Stages


- The linearity of the output stage is of primary importance
- Minimize output signal distortion
- Design goodness is measured in terms of **total harmonic distortion** (THD)

$$\frac{\text{RMS of output signal harmonics}}{\text{RMS of output signal fundamental frequency}}$$

- THD should be much less than 1% for a good stereo receiver
- Other concern is with delivering a lot of power without wasting power on the output transistors
- Output stages are classified into various types
- We'll look briefly at **class A**, **class B** and **class AB**
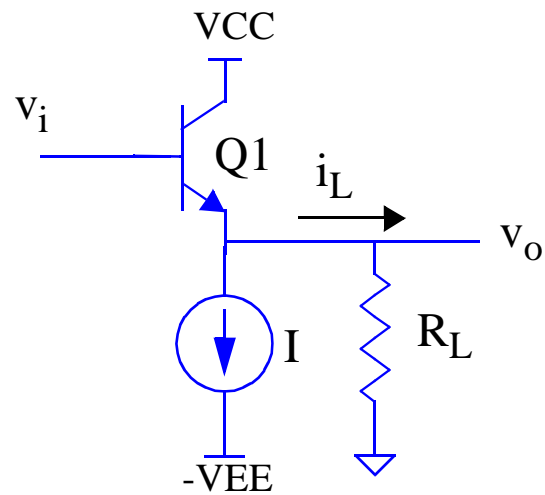
# Class A


- Large signal emitter follower with a current source bias



- “I” must be greater than the largest negative load current

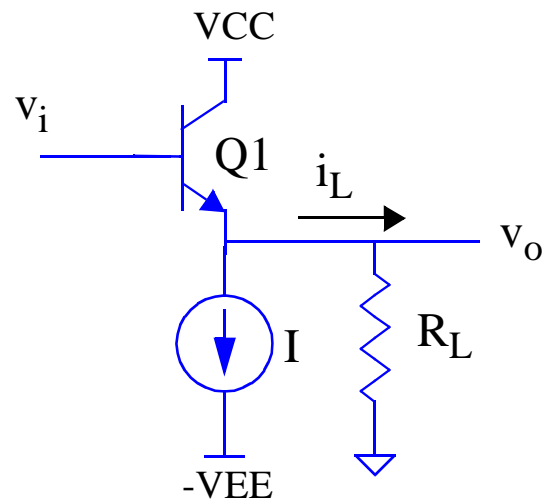
# Class A

- Assuming  $v_{BE}$  is small, it behaves somewhat linearly:



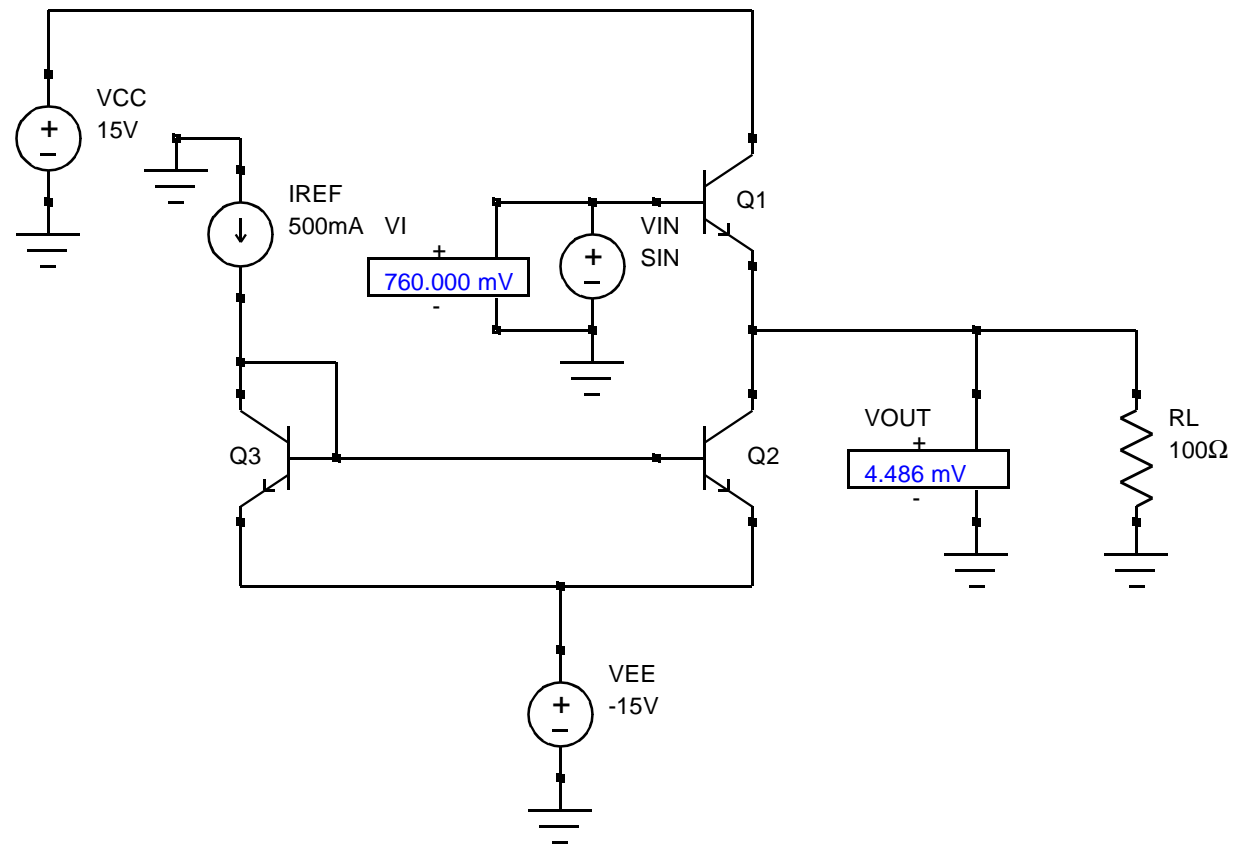
# Class A

- Offset is added to  $V_{IN}$  so that output is zero for zero ac input



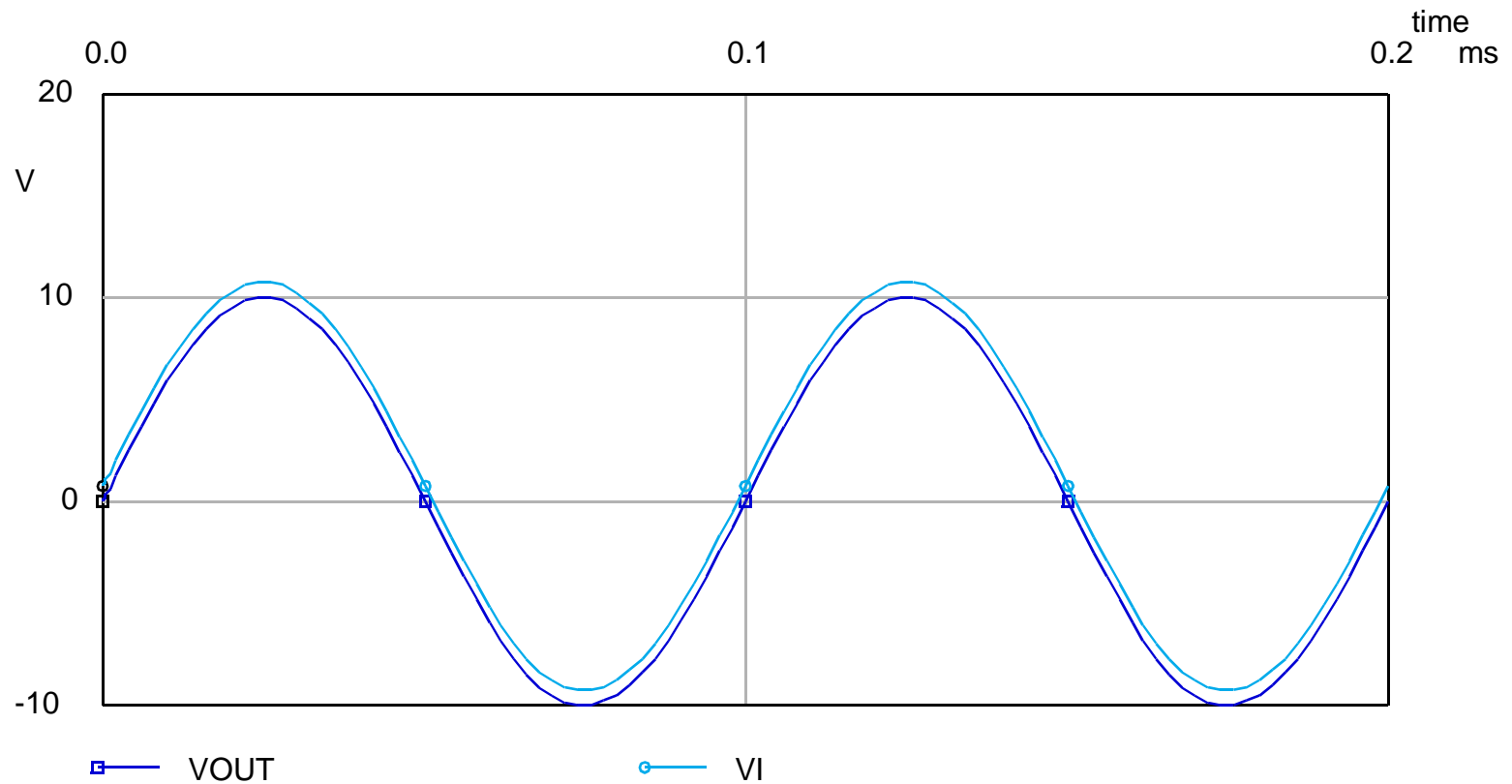
# Class A

- Large signal response is fairly linear, even with large load currents



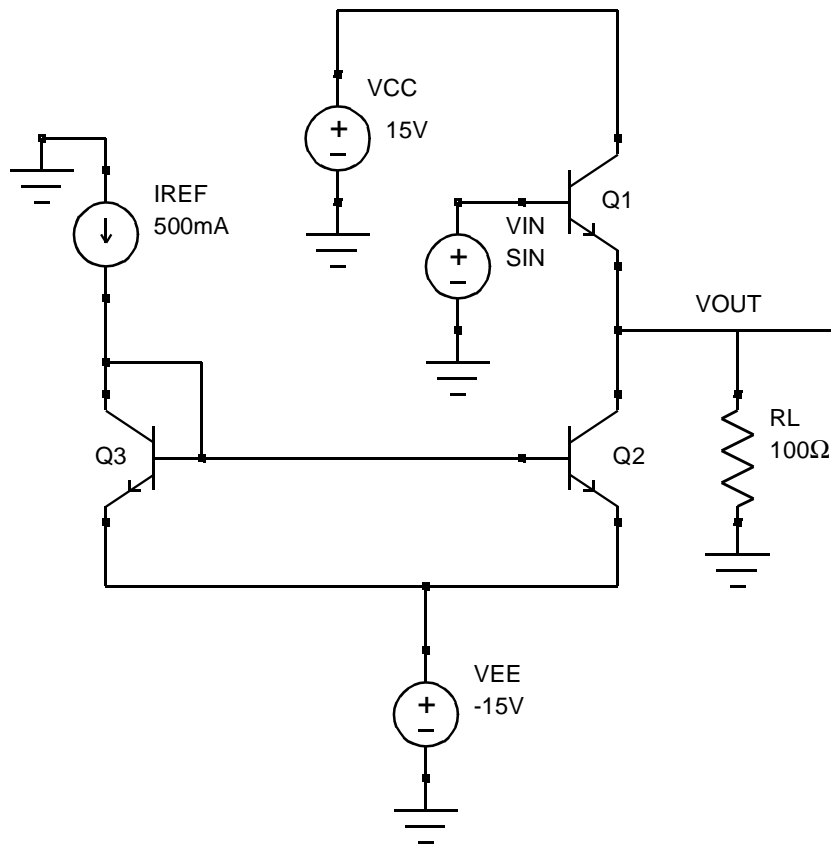
# Class A Power Dissipation

- Power dissipation can be excessive, even with no ac input signal
- For example, when  $v_o=0$ , what is the power dissipation on the transistor?


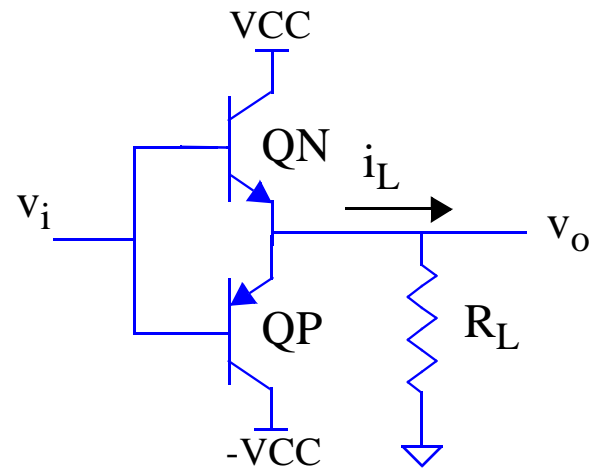
## Class B -- Push-Pull Output Stage


- Designed so that both transistors cannot be conducting at the same time using a pair of emitter followers





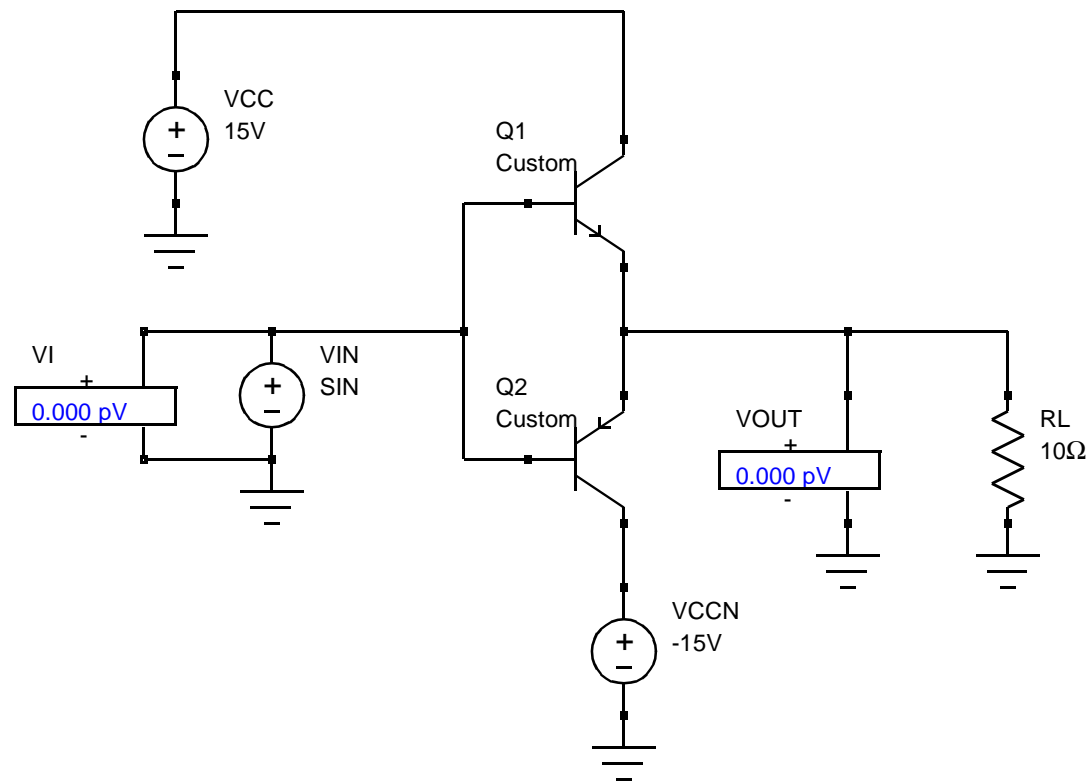
# Class B

- The class B is simpler to design, and no offset is required for  $V_{IN}$



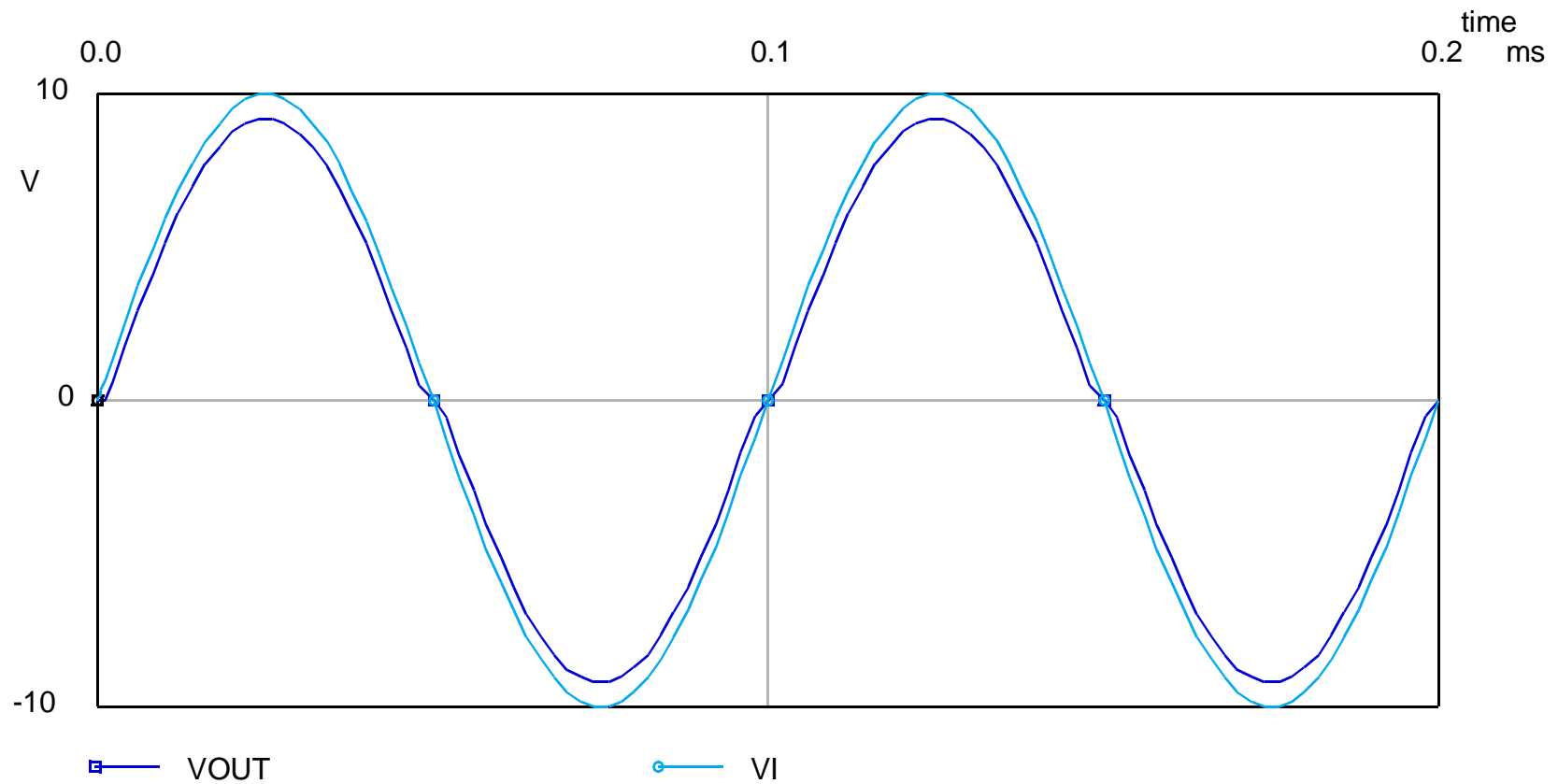
# Class B

- Large signal response is still fairly linear, even with larger load current



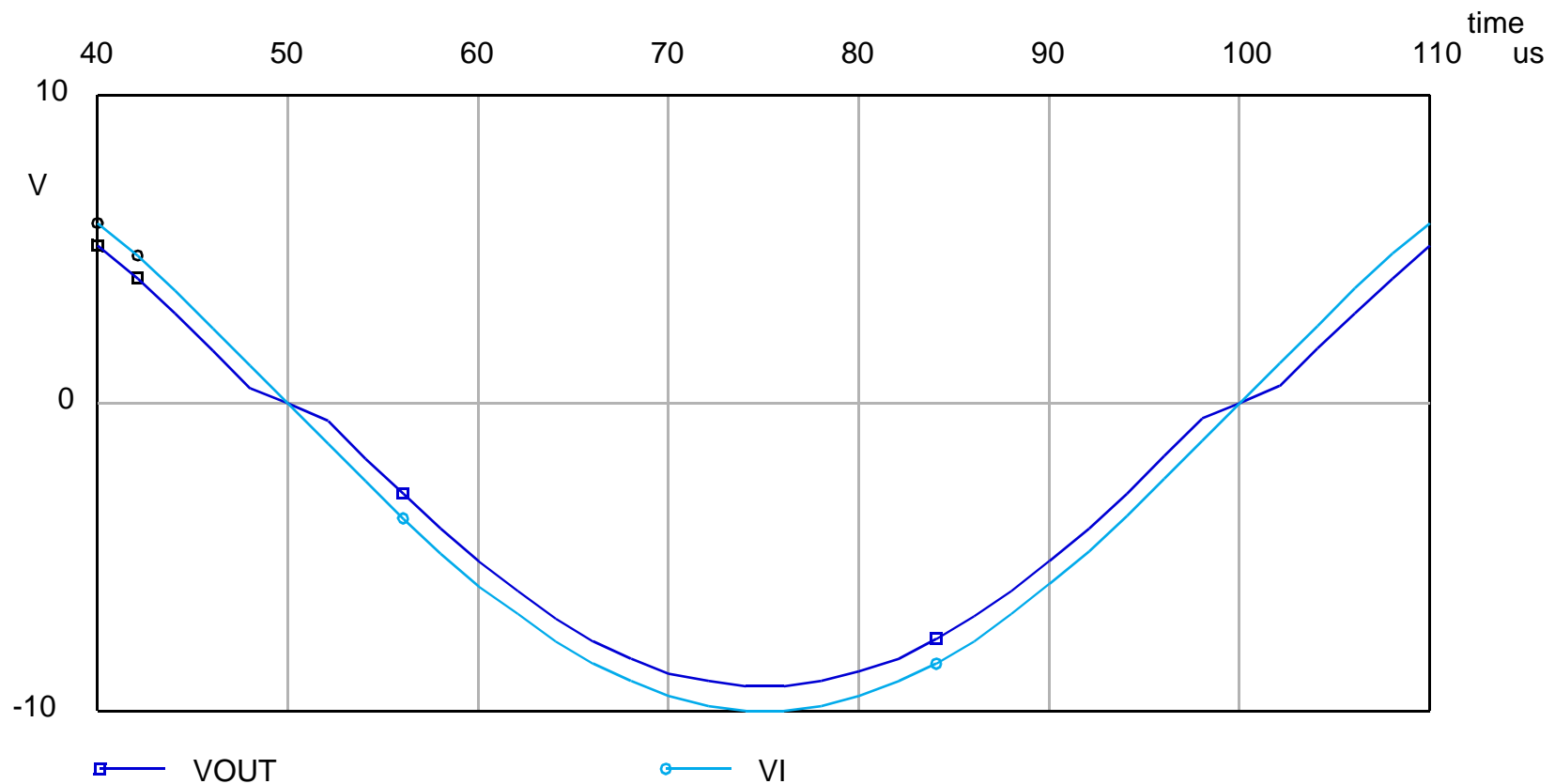
## Class B Crossover Distortion

- The problem is the deadband region for which both QP and QN are off
- Produces unwanted noise for an audio signal



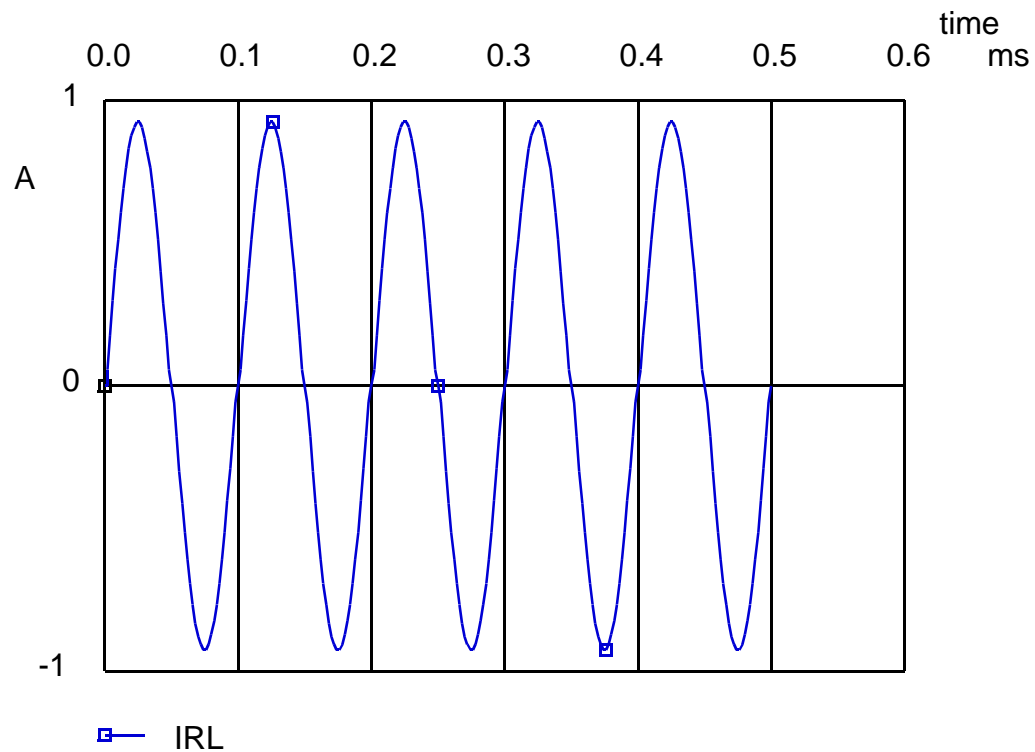
## Class B Power Dissipation

- dc power dissipation is zero
- Avg. power can be calculated for each transistor
- The positive load current is supplied by QN, and the negative is supplied by QP



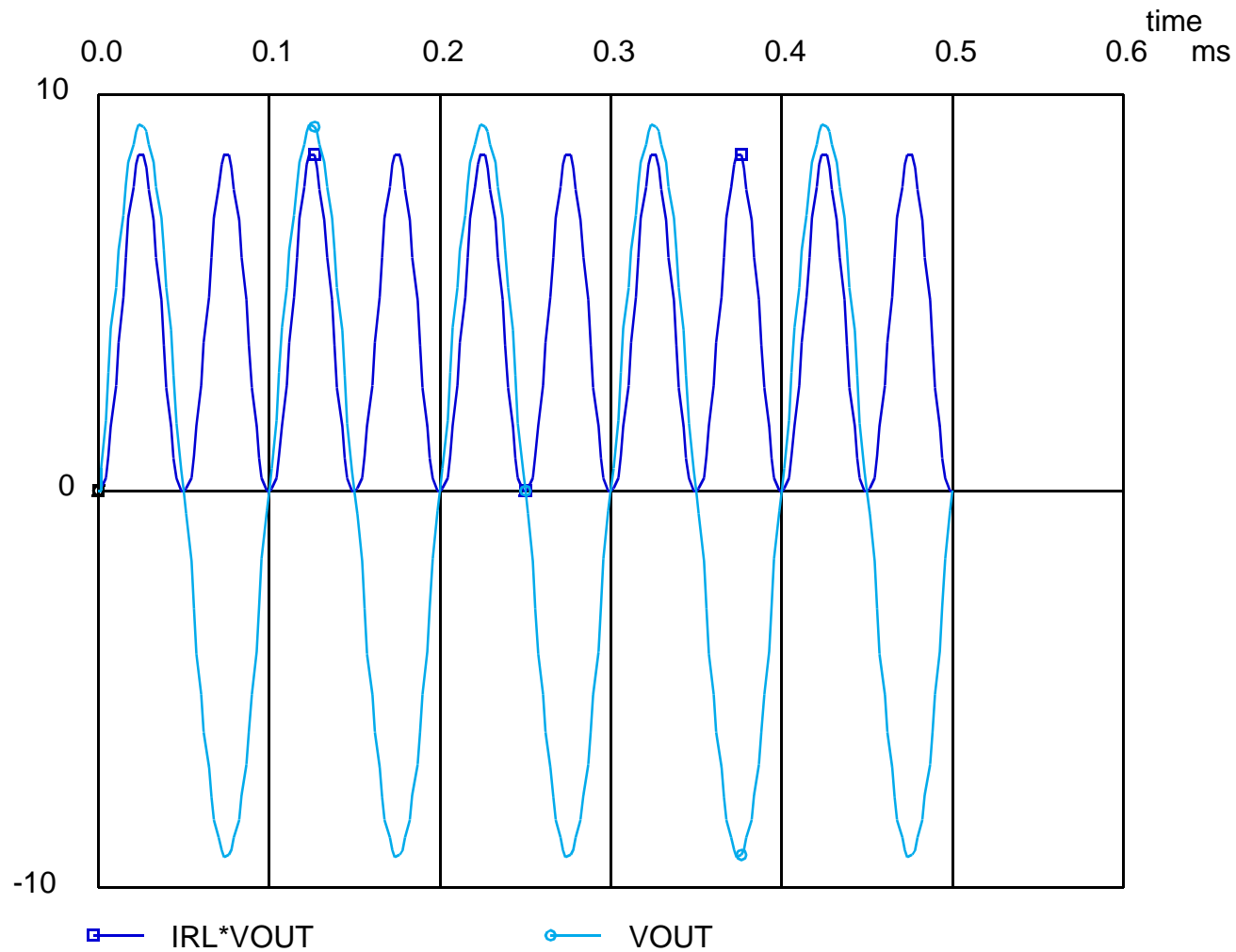
# Class B Power Dissipation

- The instantaneous power is the same for both the push and the pull



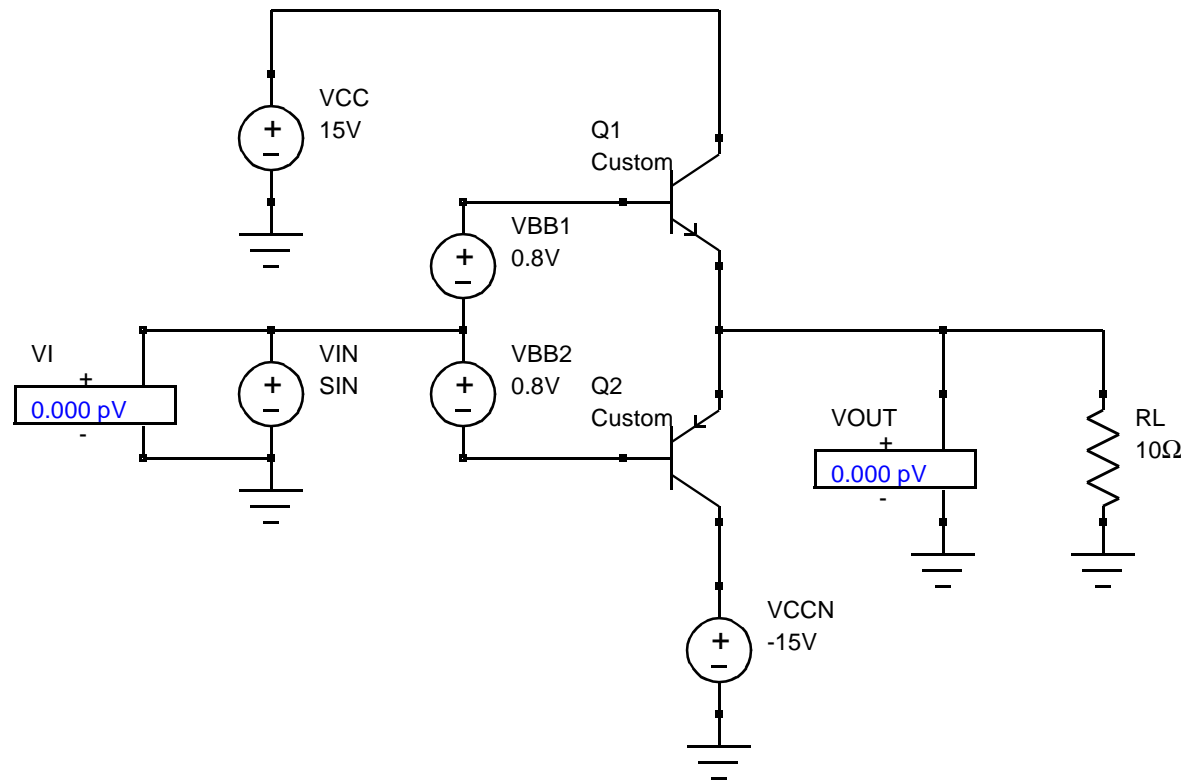
# Class AB

- The most difficult aspect of the class AB design is creating the VBB bias voltages



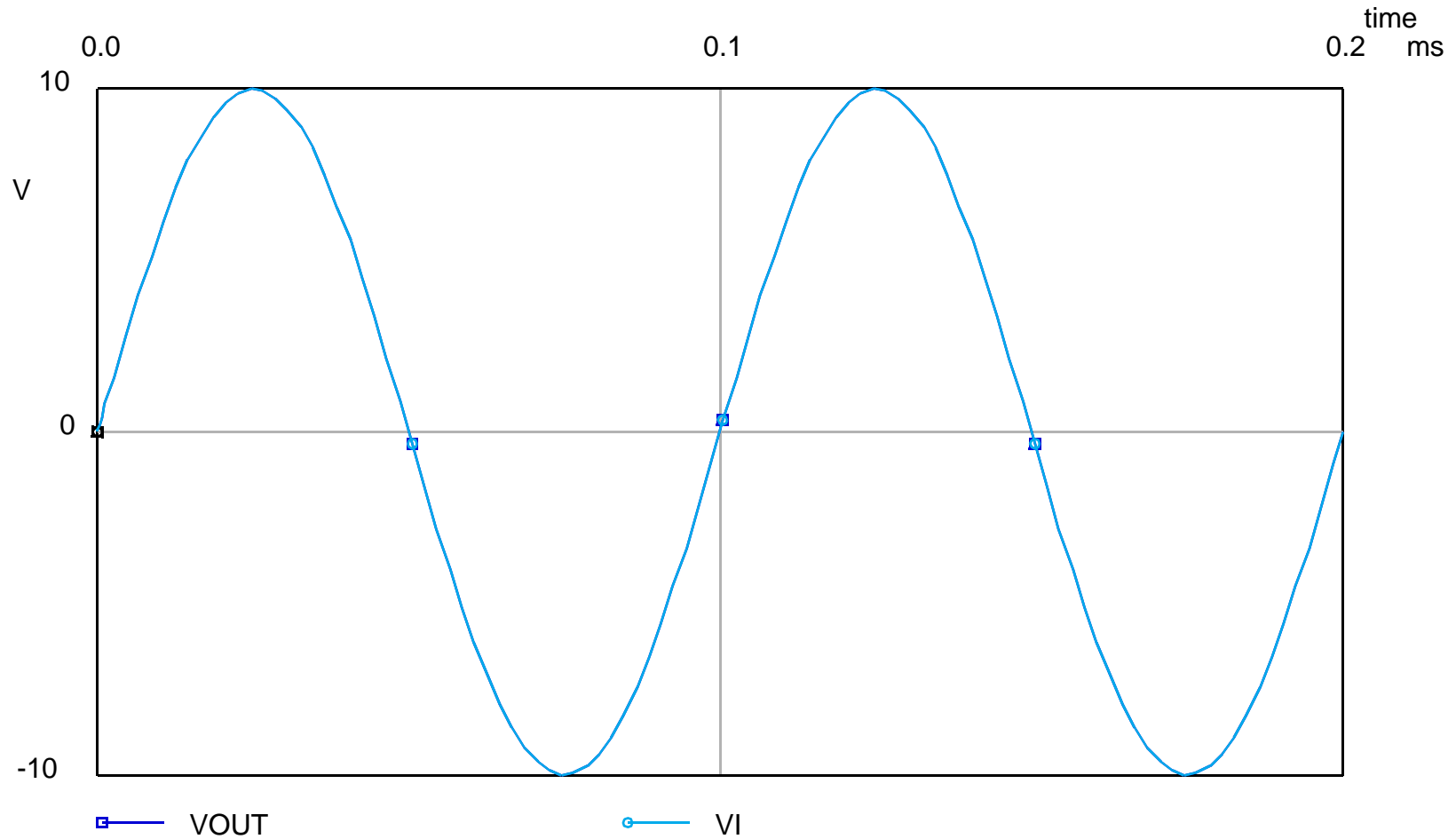
# Class AB

- Input and output are now overlapping, with no cross-over distortion


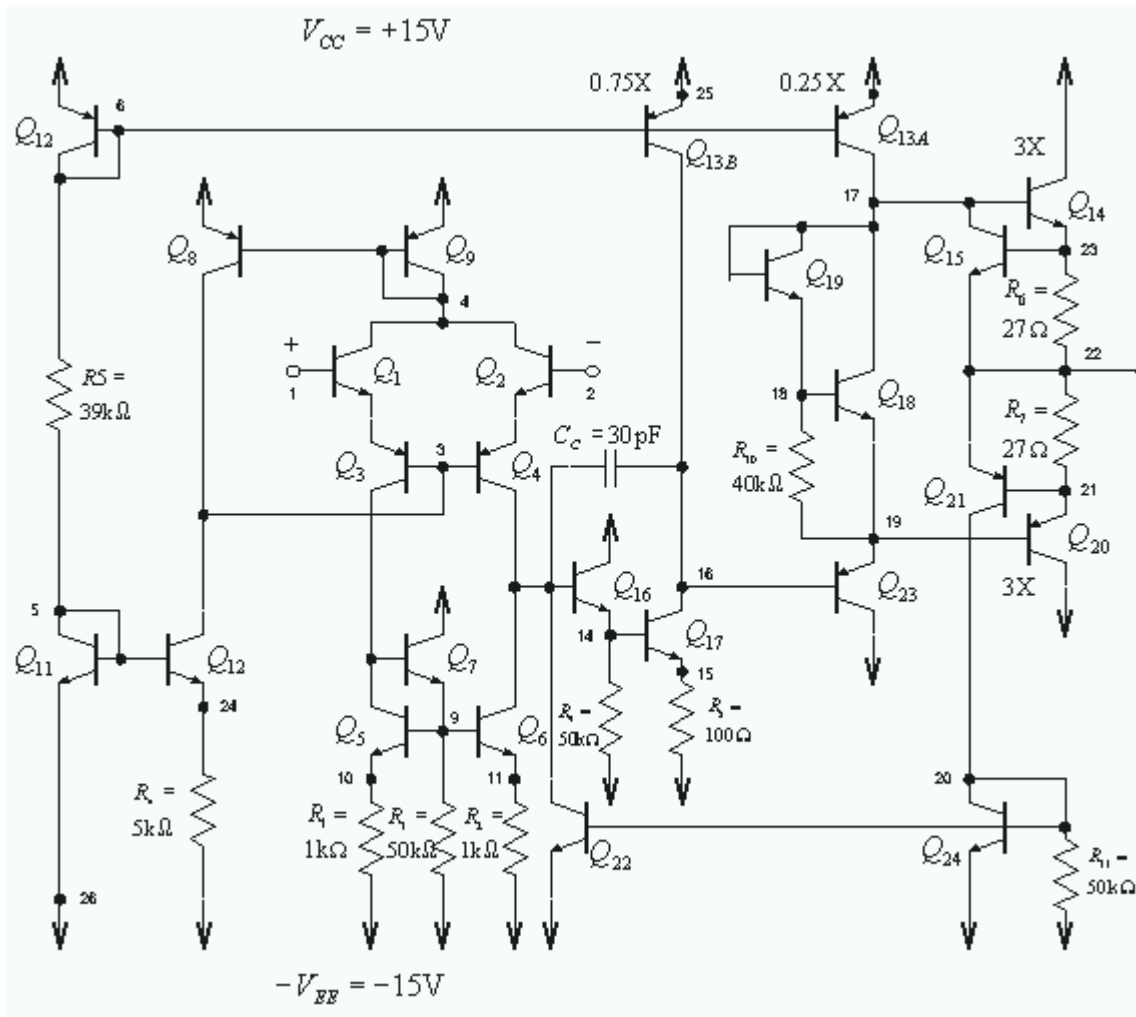
# More Elaborate Multi-Stage Amplifiers


- Now you can “sort of” recognize all of the major portions of a 741 opamp





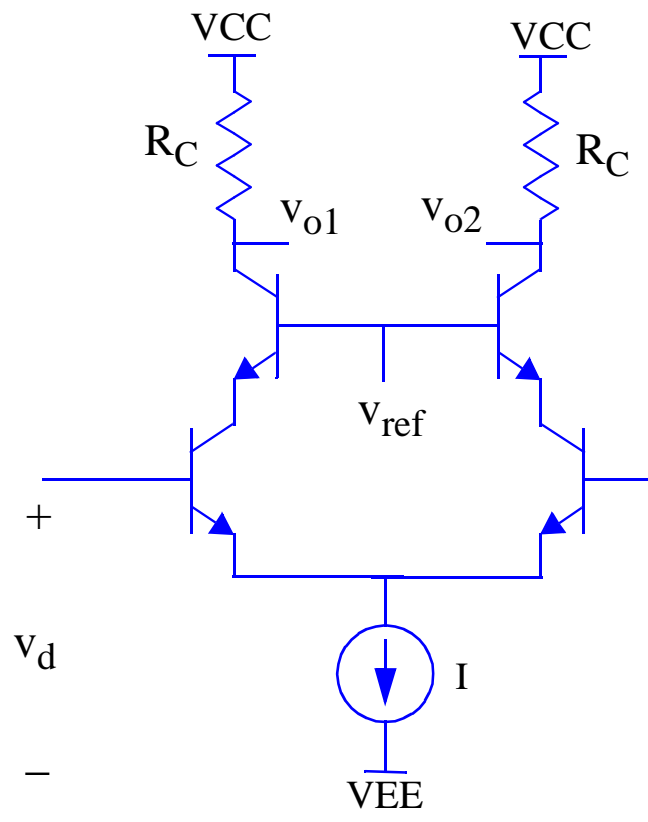
# Cascode Amplifier

- Most differential IC stages will use a cascode stage or something similar to one


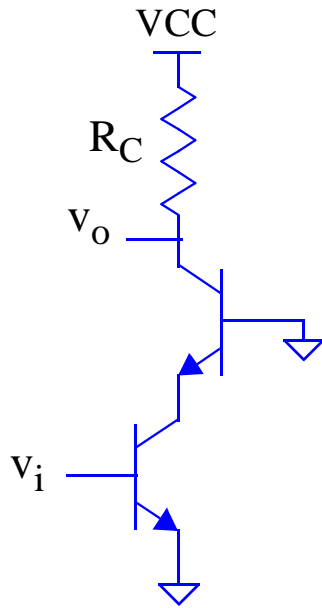
# Cascode Amplifier

- Cascode amplifiers are often used for generating high output impedance and/or high frequency operation



# Cascode Amplifier

