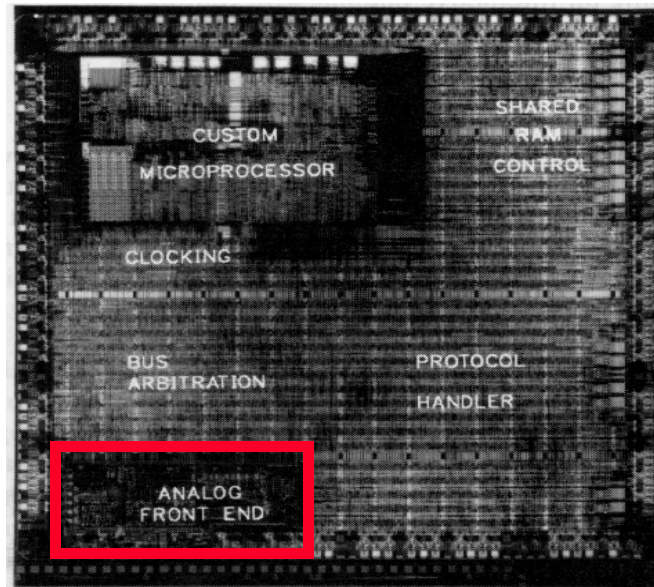


MOS IC Amplifiers


- MOSFETs are inferior to BJTs for analog design in terms of quality per silicon area
- But MOS is the technology of choice for digital applications
- Therefore, most analog portions of mixed-signal designs are MOS
- Most MOS amplifiers will be IC amplifiers with “active” loads
- Resistors and decoupling capacitors are too expensive on ICs



**Token Ring LAN
JSSC 12/89**



NMOS Amplifier --- Active Load

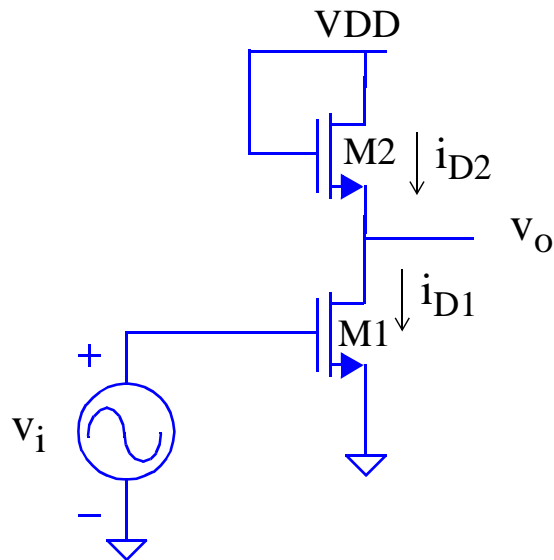- Natural extension of amplifier with resistor pull-up
- Size M2 and bias M1 so that M1 is in saturation
- This is a digital NMOS logic gate when large input signals are applied





Load Line View

- “Load line” is nonlinear

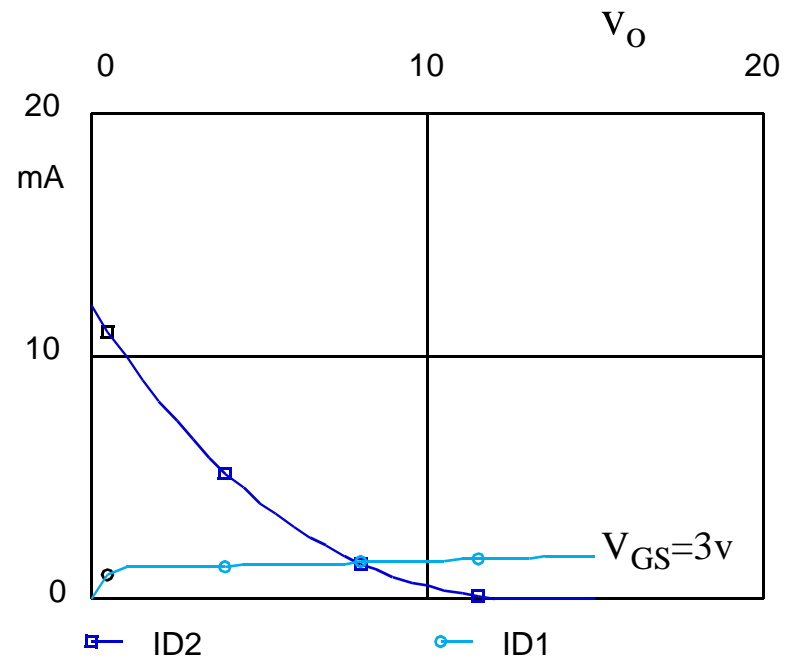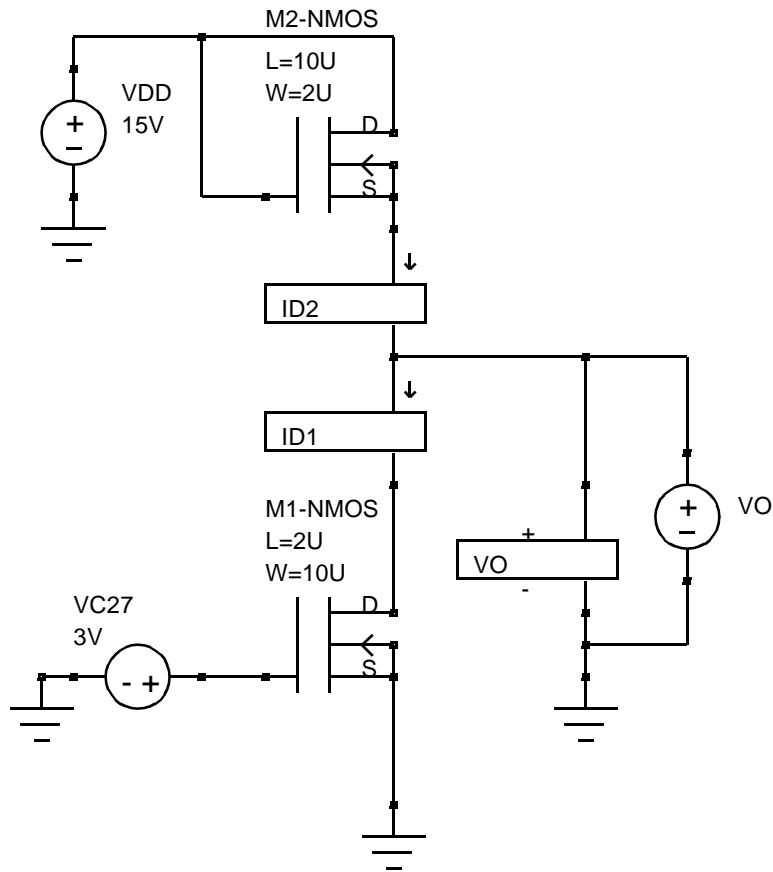


NMOS Amplifier Example

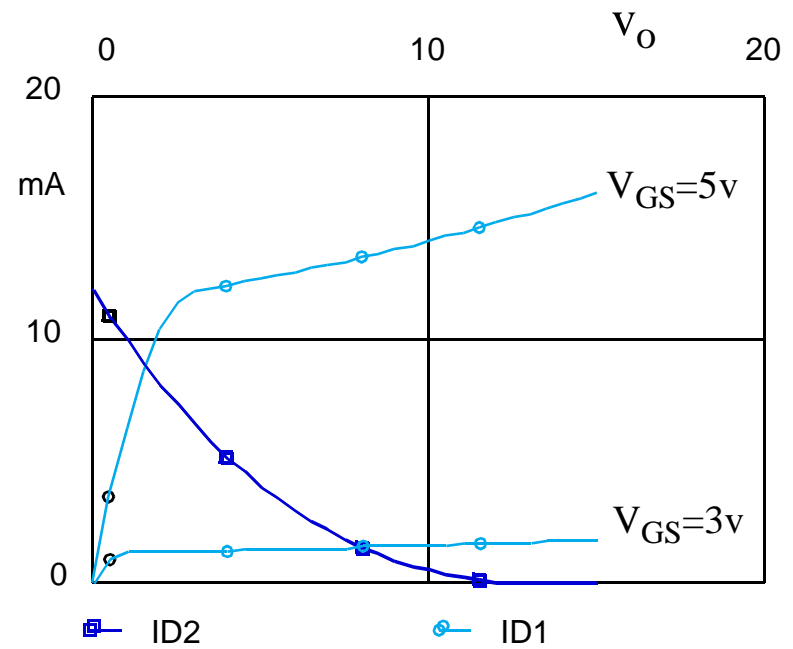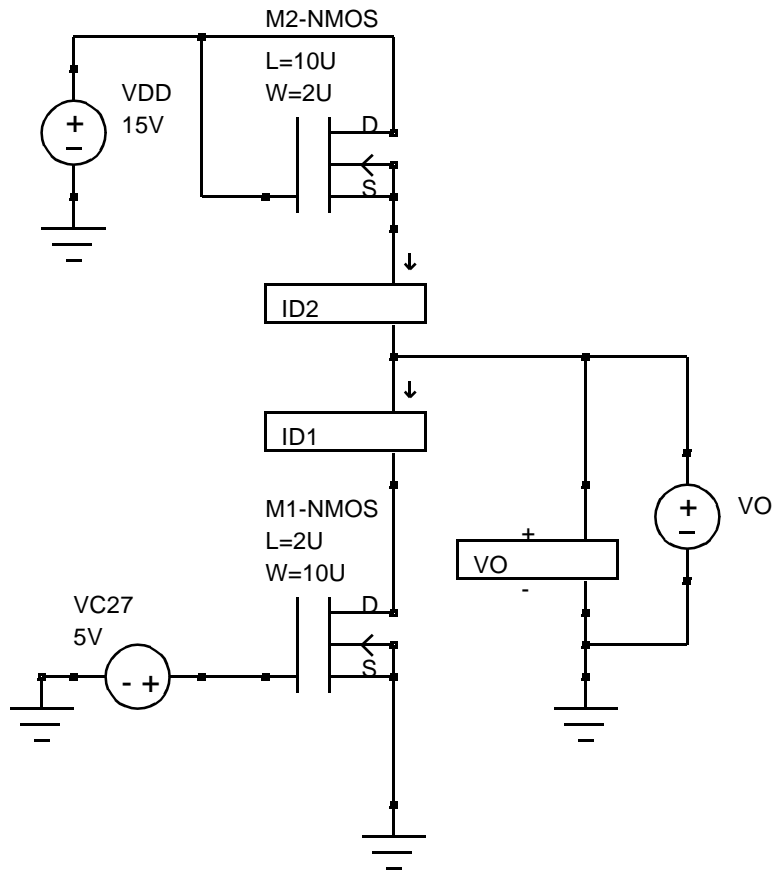- For a larger dc input bias voltage M1 is no longer in saturation




Small Signal Model

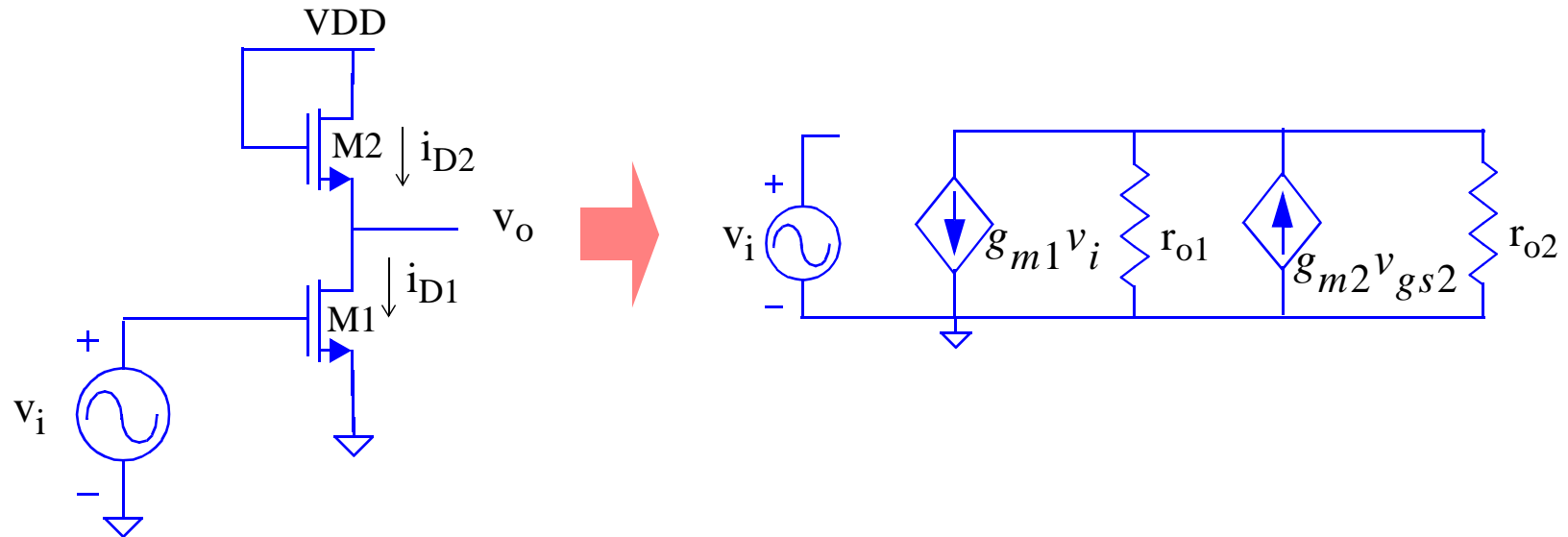- M2 behaves like a resistor in the small signal model
- Why?




Small Signal Model

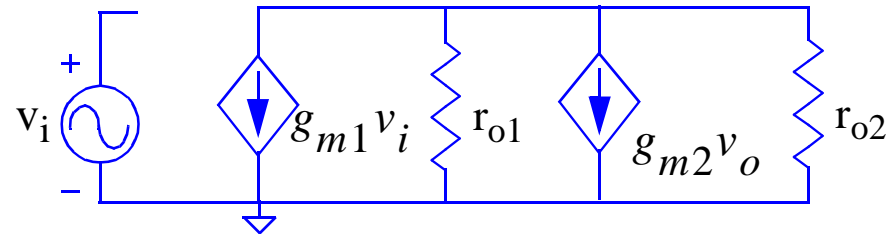



NMOS Amplifier Example

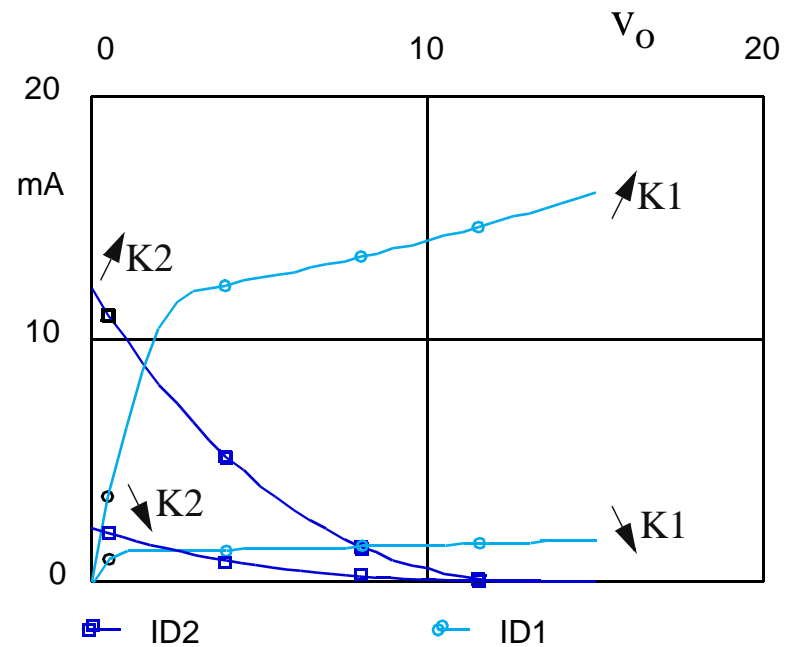- We would tend to lower the “resistance” of the pull-up transistor (increase K_2), or decrease the current levels of the amplifier transistor (decrease K_1) to keep M1 in saturation
- But these changes tend to lower the gain



NMOS Amplifier Example

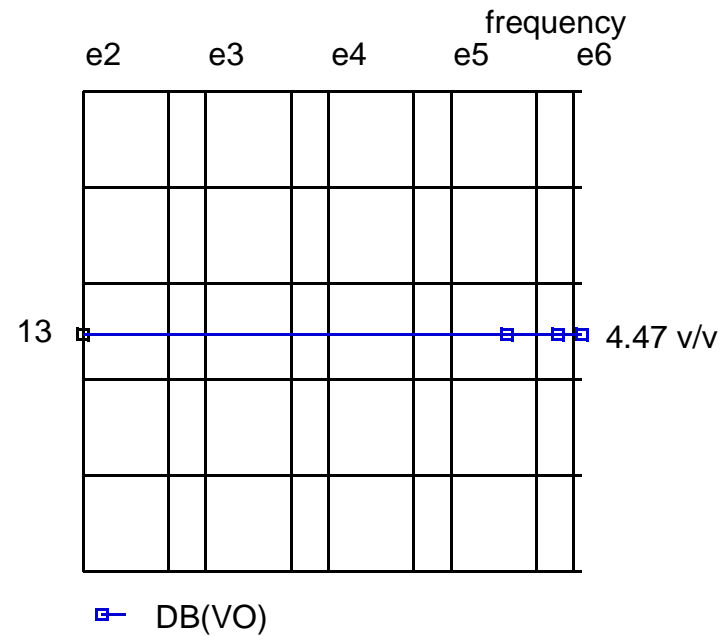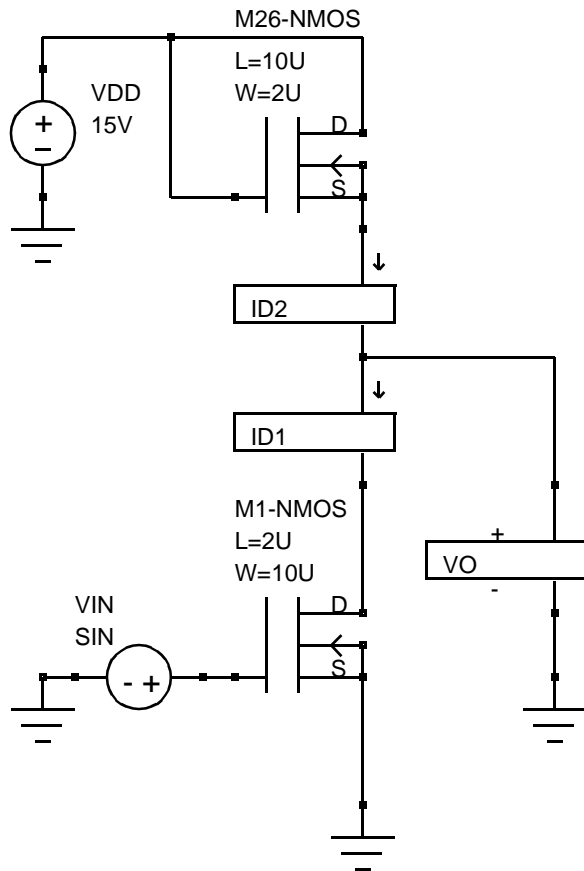
- Design objective is to make K_1 as large as possible, and K_2 as small as possible, to get a reasonable gain



- Why the deviation from ideal gain?

Body Effect

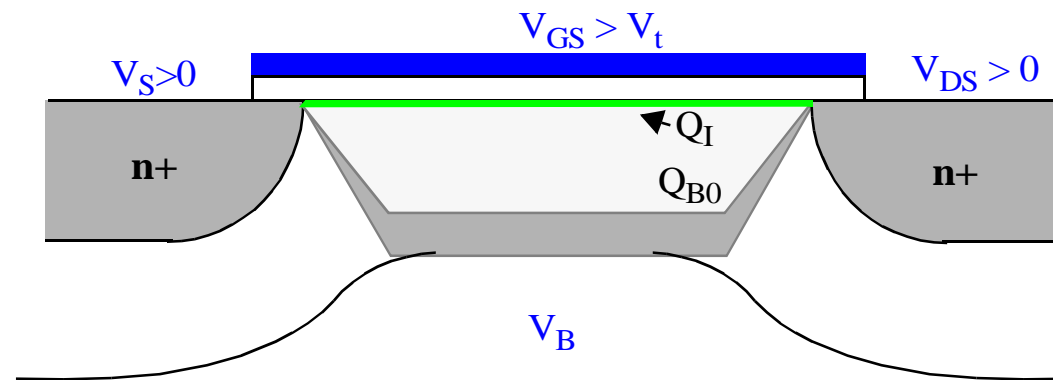- For discrete FETs there is no body effect since the source is tied to the body
- For ICs, all of the NFET body nodes are tied to the lowest potential in the ckt
- The source of our load transistor is not at the same potential as the substrate
- Source voltage partially modulates the channel --- **back gate effect**




- For large signal behavior this is captured by the change in V_t based on the parameter, **gamma**

$$V_t = V_{t0} + \gamma(\sqrt{2\phi_f + V_{SB}} - \sqrt{2\phi_f})$$


Body Effect

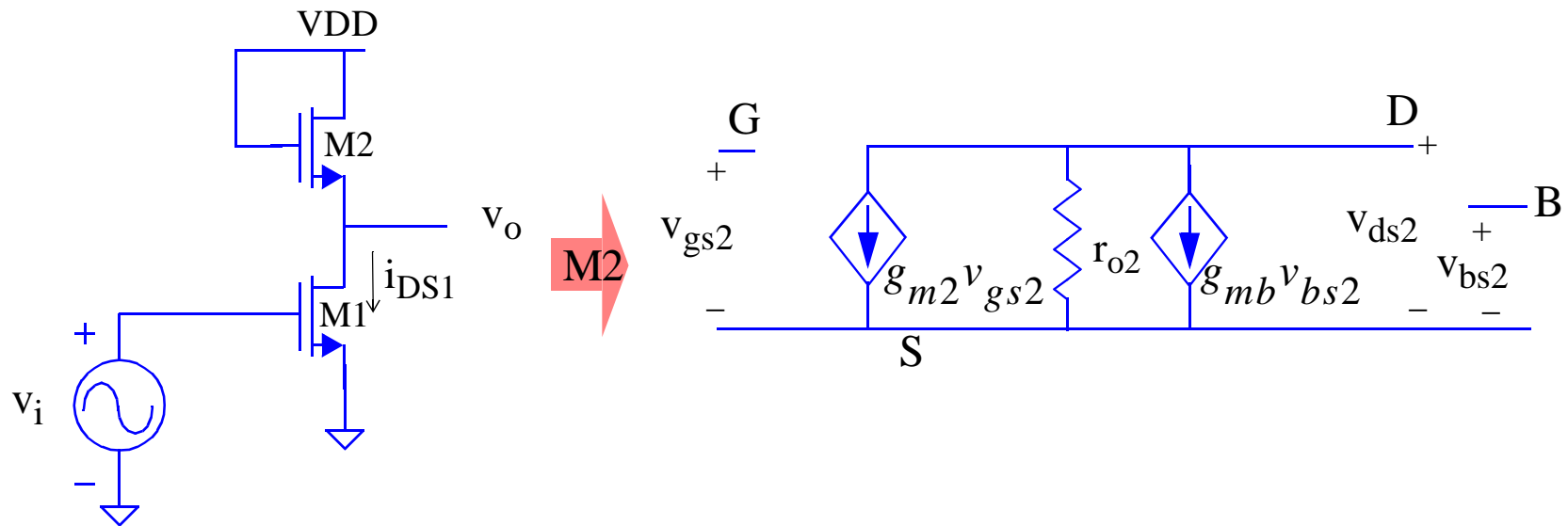- The impact on the small signal model is a function of same parameters
- The change in v_o (which is the source voltage) modulates the **back gate**




Common Source CMOS Amplifier --- Active Load

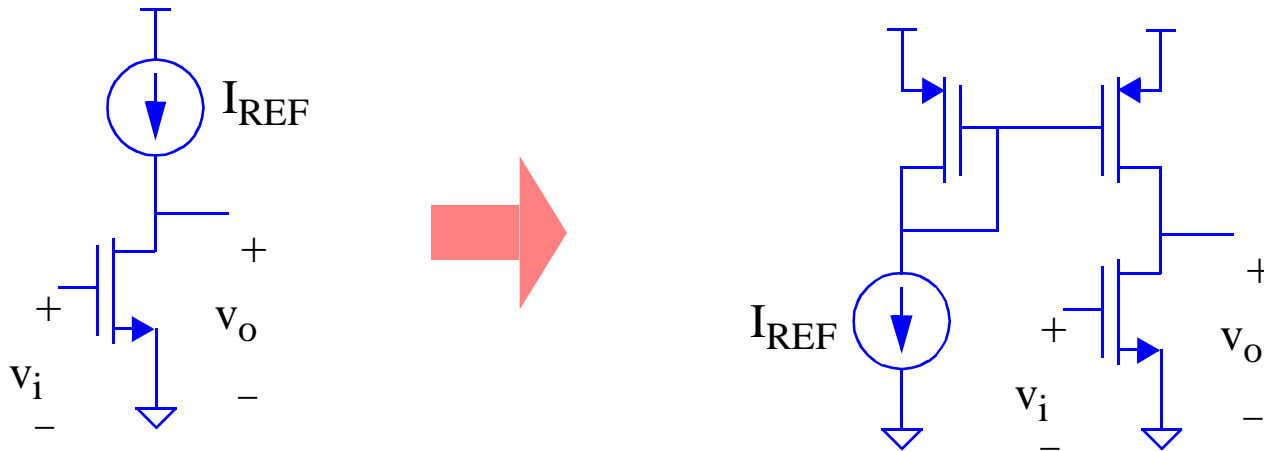- Body effect is not as significant a problem for CMOS
- Current sources are used as pull-ups instead of resistors or load-transistors
- Having complementary types of transistors simplifies the implementation
- Is the body effect a factor for this amplifier?




Common Source Small Signal Model

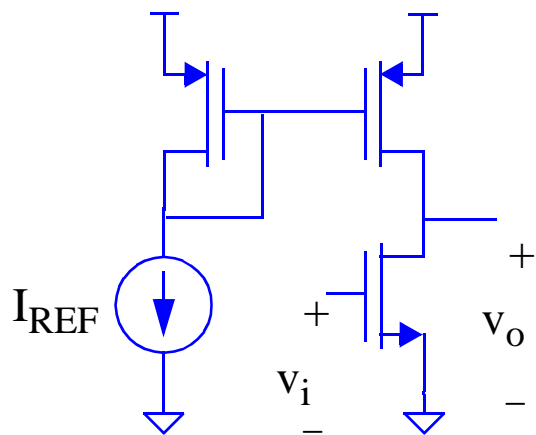- Load line is now nearly a constant current --- huge gain
- What does the small signal model look like?





Common Source Small Signal Model

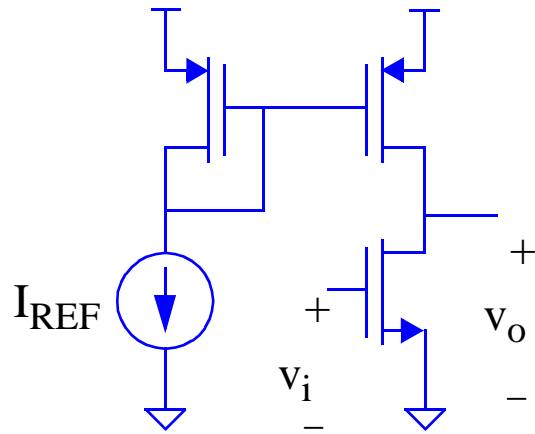

CMOS High Gain Region


- Input-output relation is very similar to a CMOS inverter
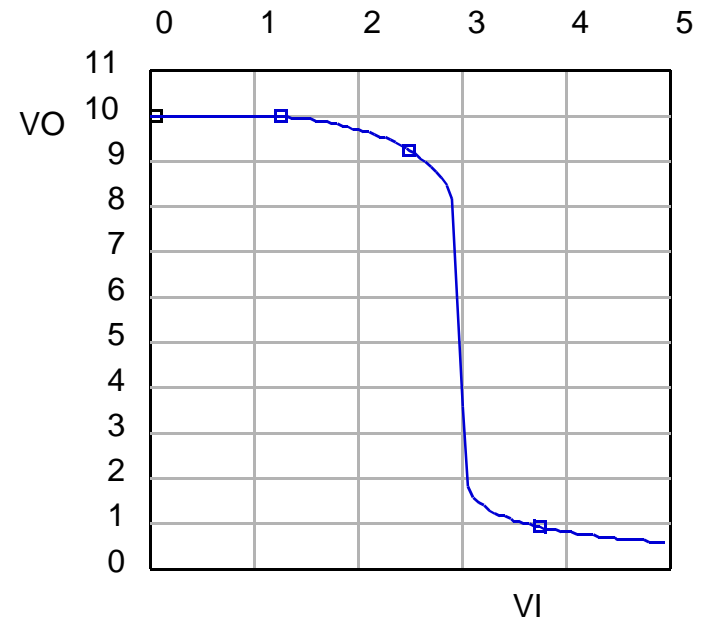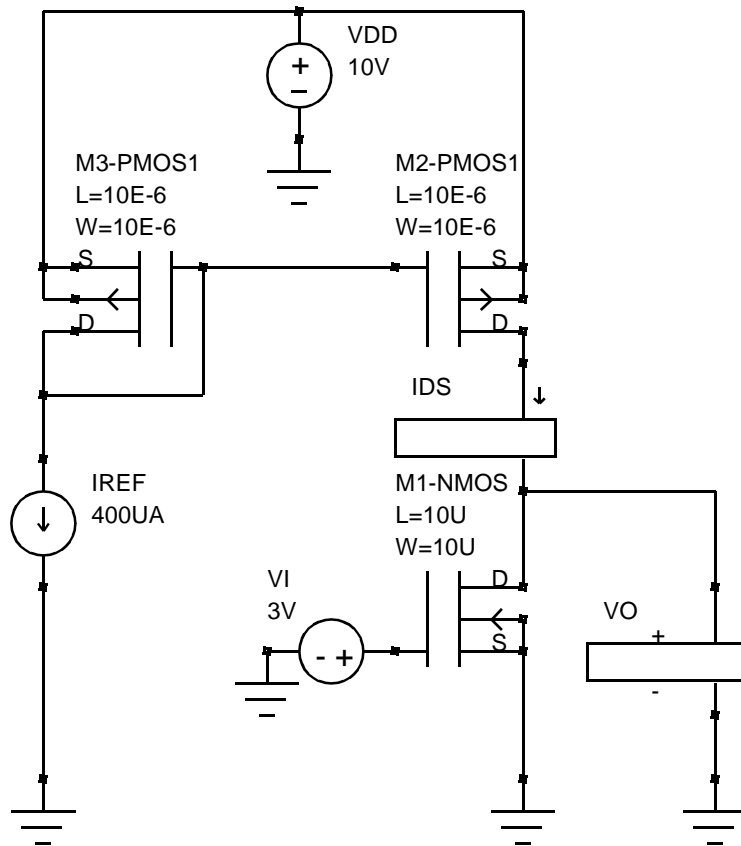
$$V_t = 1\text{V} \quad K = 100\mu\text{A}/\text{V}^2 \quad \lambda = 0.01$$





CMOS High Gain Region

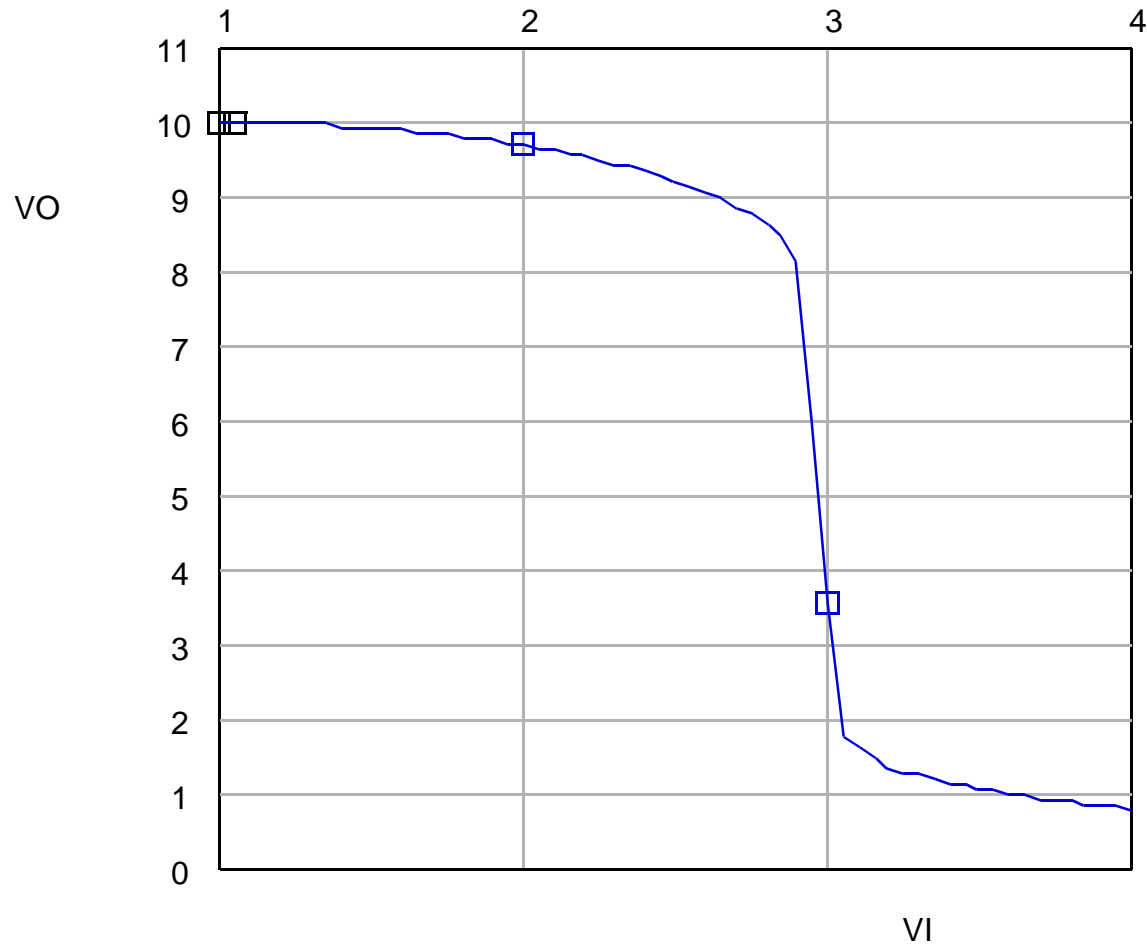- What is the allowable range for v_o and v_i ?




ac Response

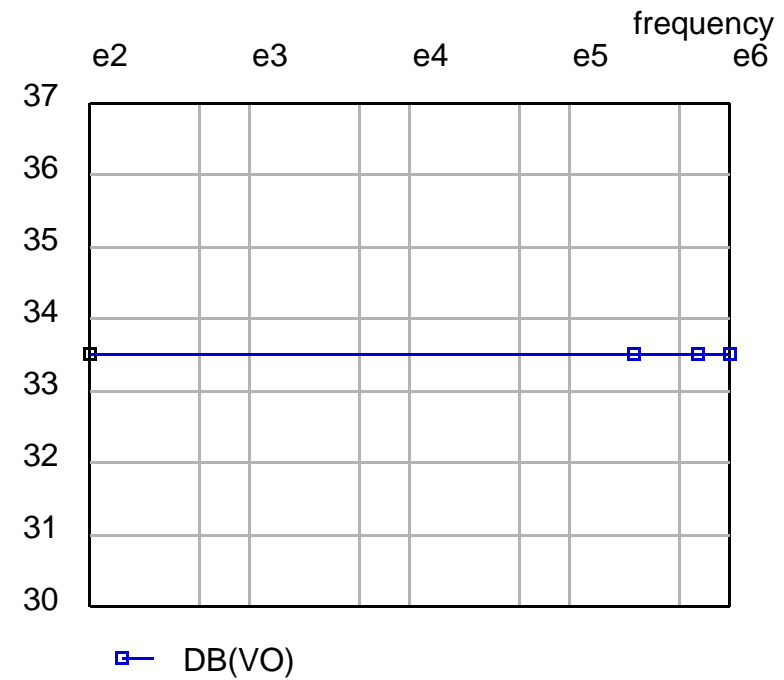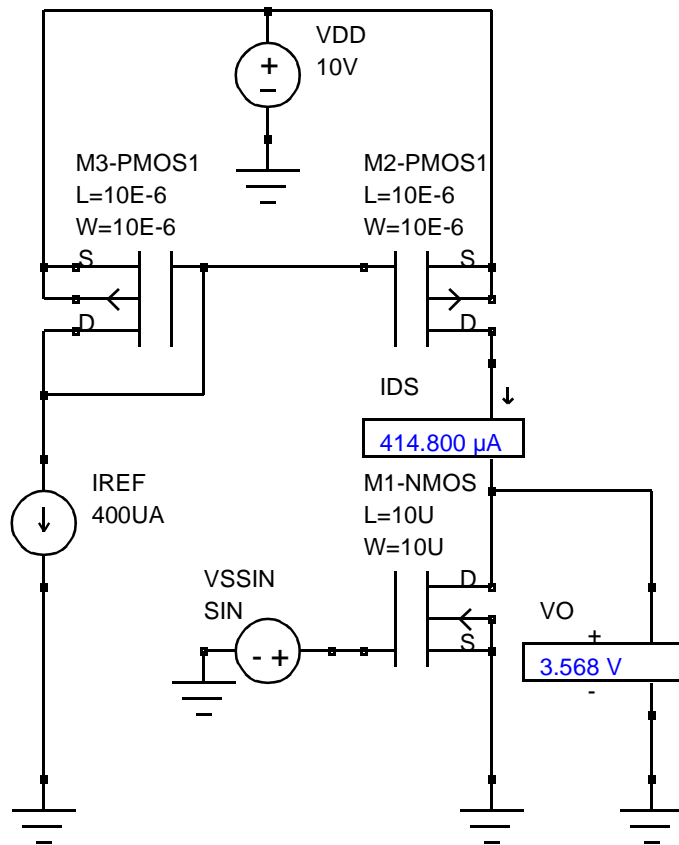- Using an ac input with a 3 volt offset: $V_t = 1\text{v}$ $K=100\mu\text{A}/\text{V}^2$ $\text{lamda}=0.01$




Common Drain (Source Follower) Amplifier

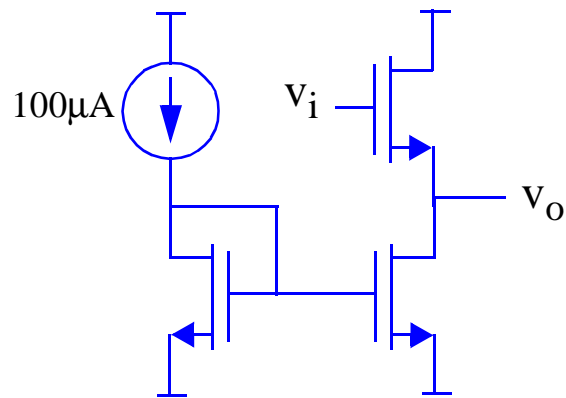- Source Followers are used for output stages
- Gain less than unity, but provides low output resistance to drive loads




Common Drain (Source Follower) Amplifier

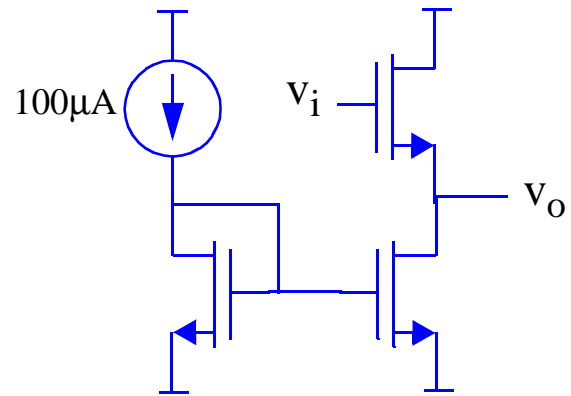

Common Drain (Source Follower) Amplifier

Source Follower

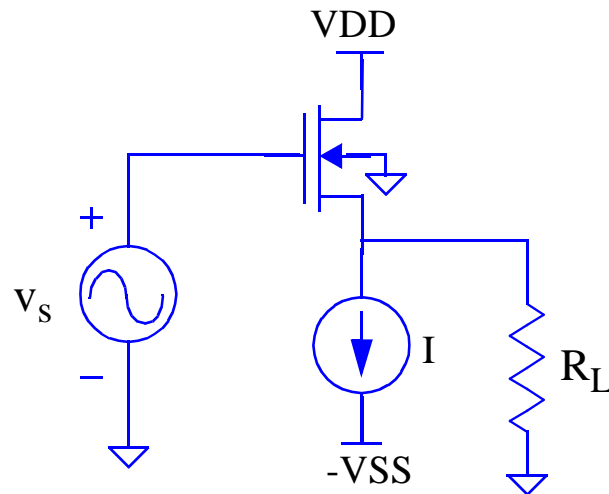- For an emitter follower, the gain is the voltage division of input resistance and emitter resistance
- But the source follower is somewhat different from an impedance reflection standpoint



- Small signal impedance looking into the gate appears as an infinite resistor, while that from the perspective of the source is finite

Small Signal Model

- Assuming that R_L is infinite?