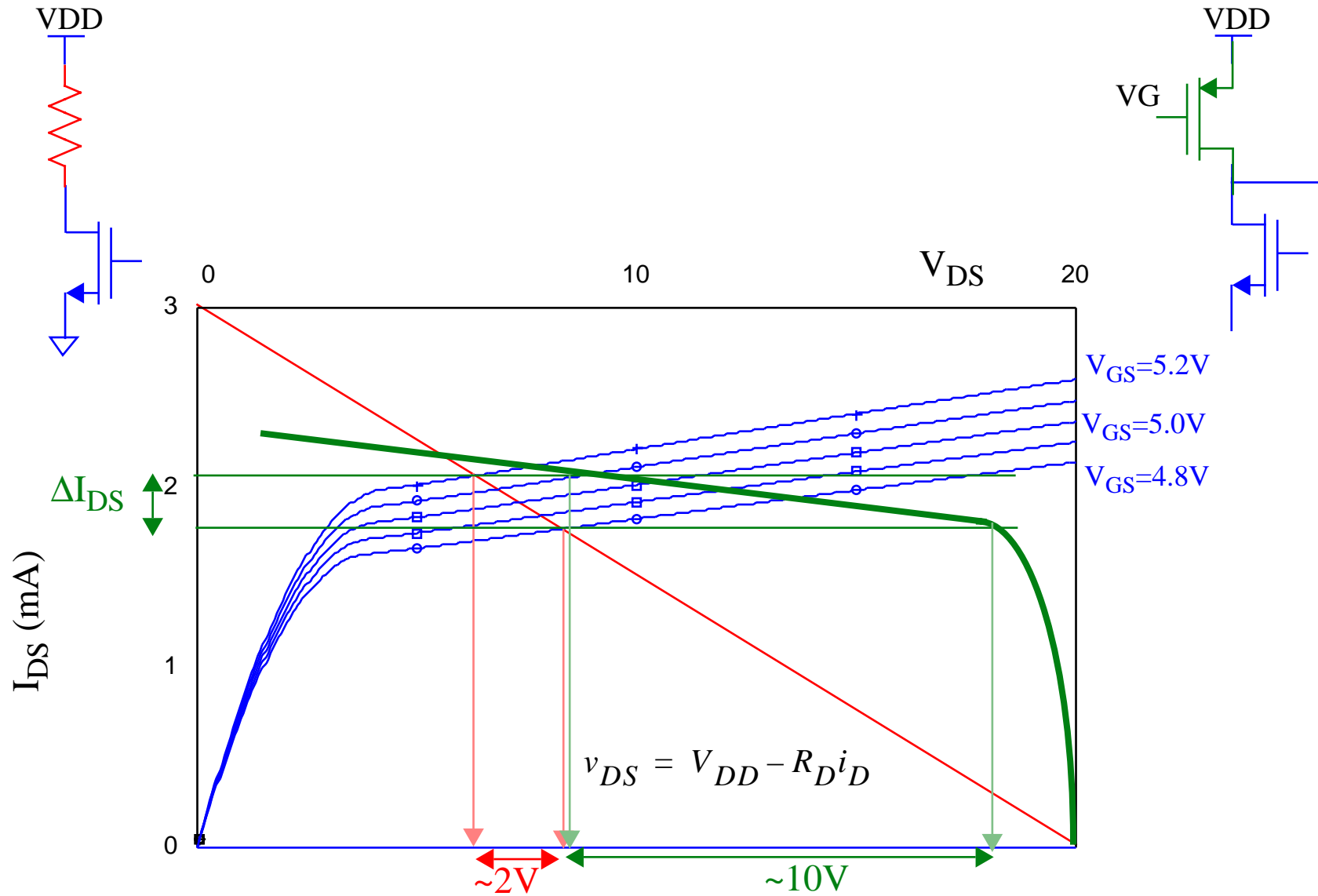



Passive Loads vs Active Loads

- MOS diff amp loads are generally transistors on ICs




Active Loads

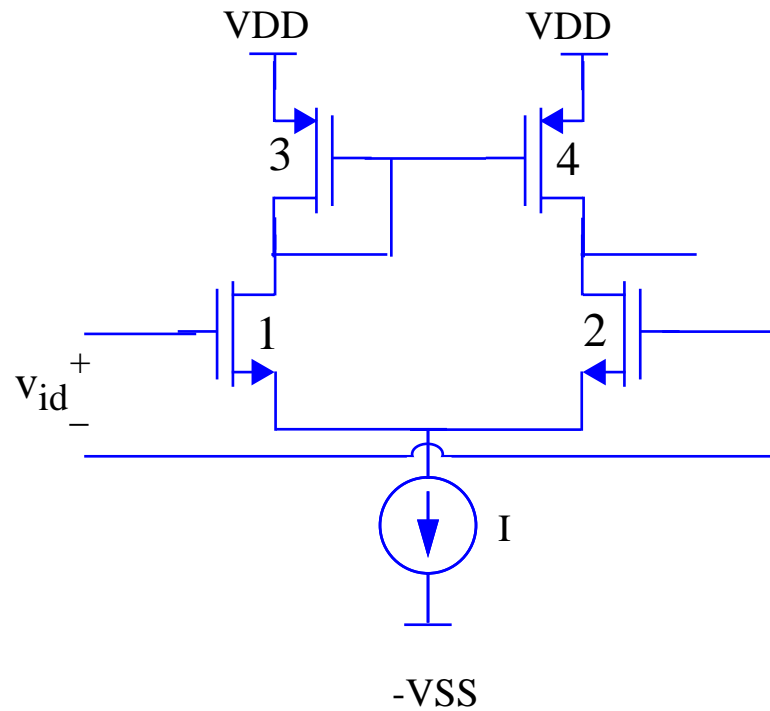
- MOS diff amp loads are generally transistors in ICs



Two Stage OpAmp

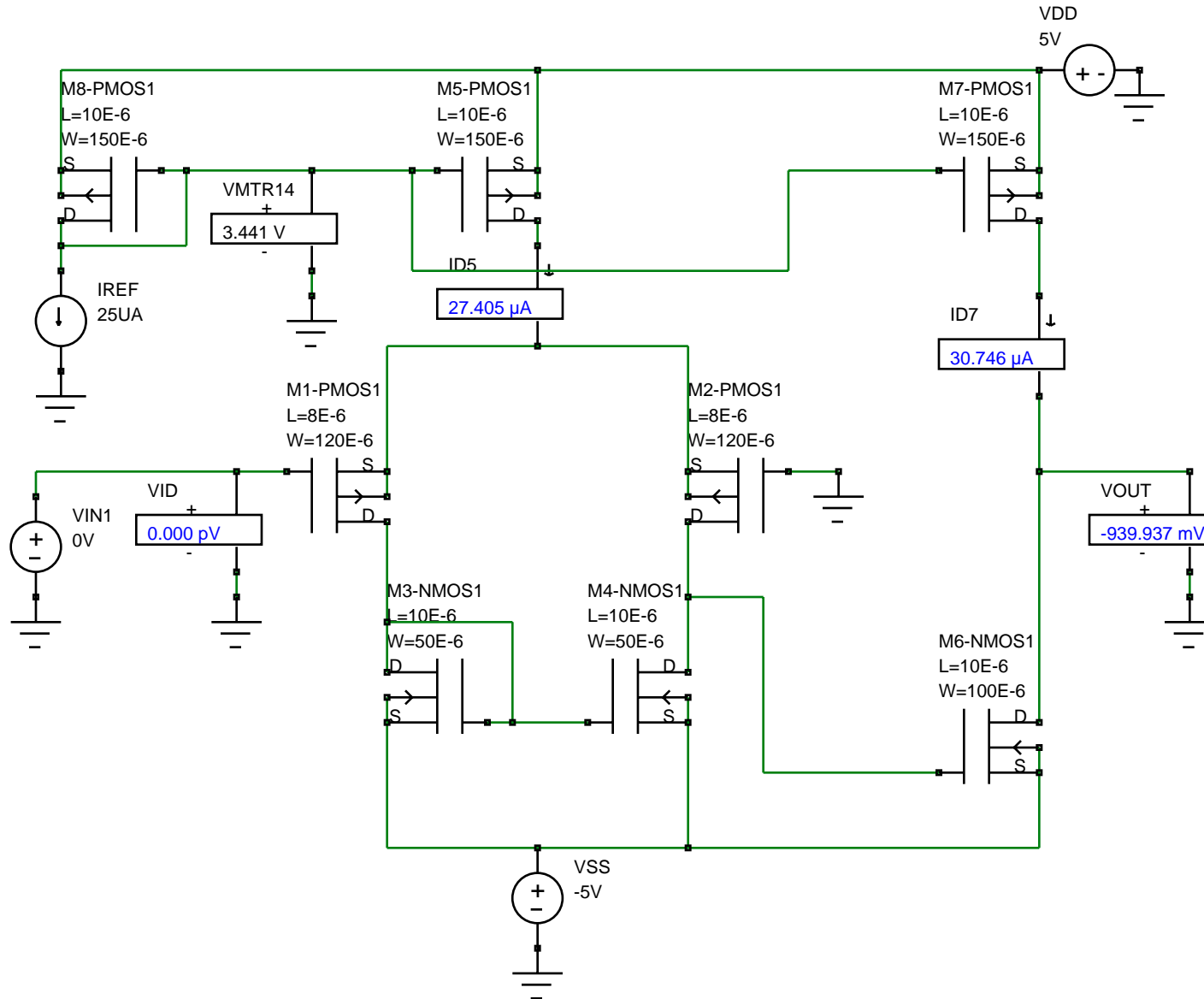


Two Gain Stages

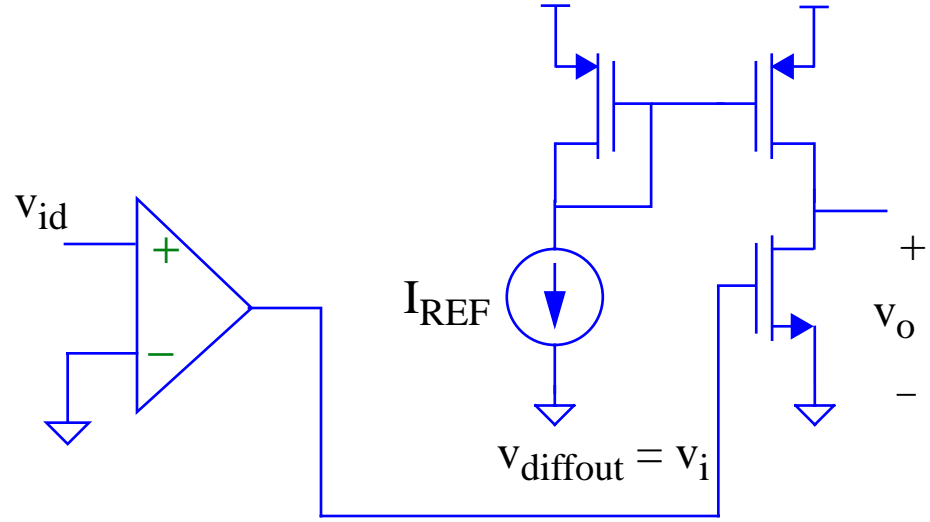


Two Stage OpAmp

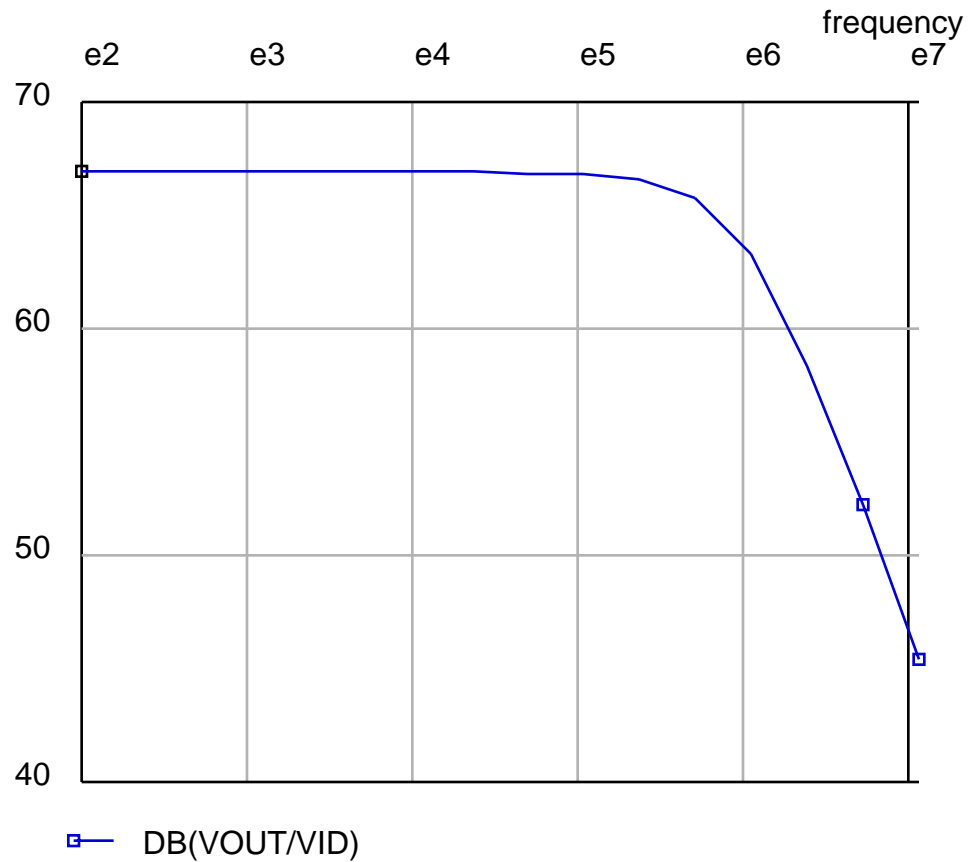
- The overall gain is the product of the two stage gains



Compensation

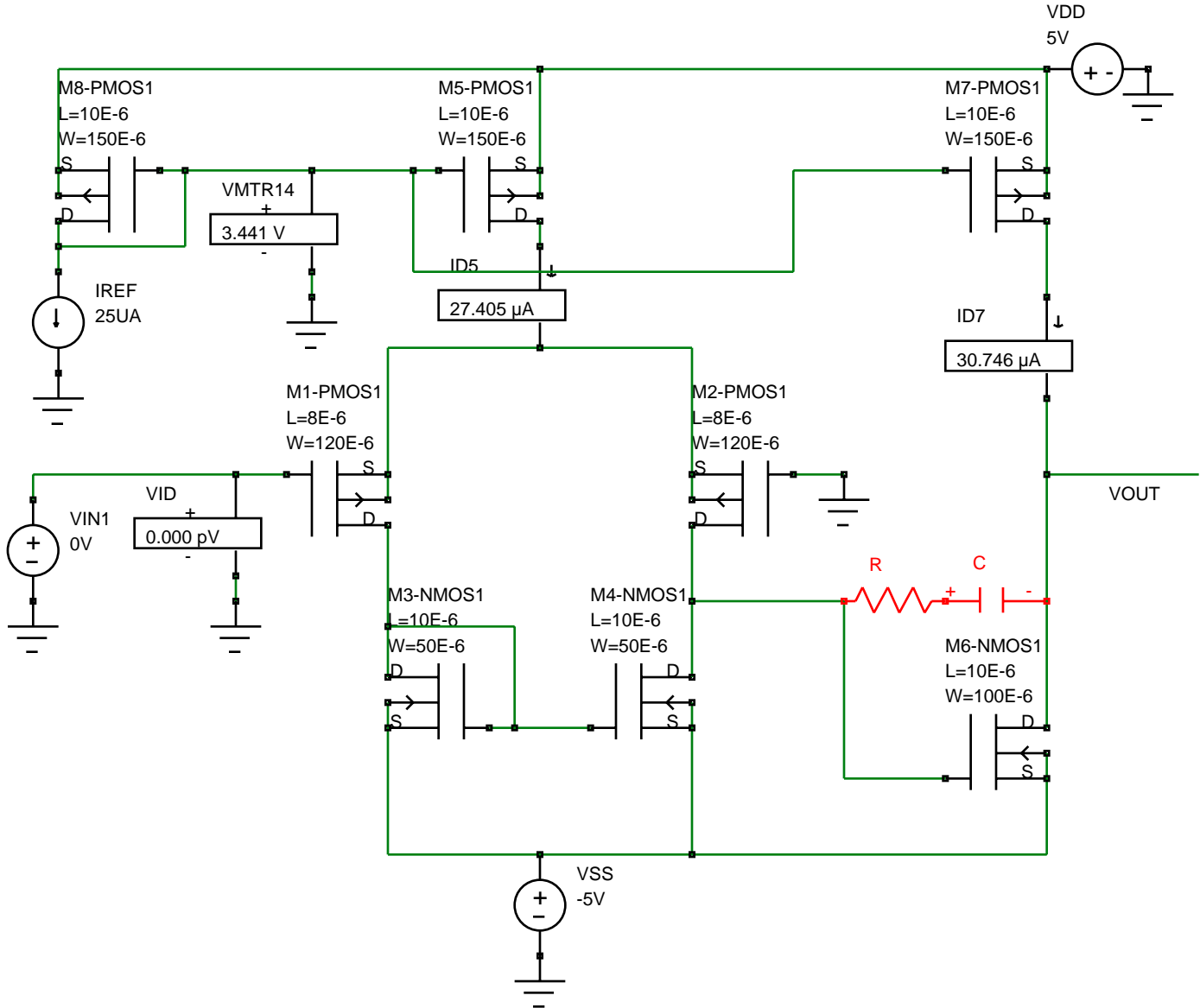


Common Gate Configuration

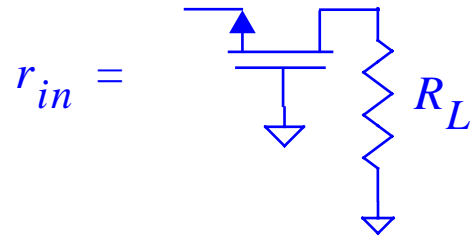


Common Gate Configuration


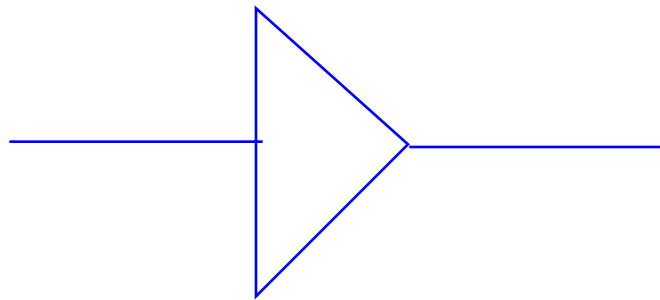
- Common gate configuration acts as a current buffer (just like common base)




Cascode

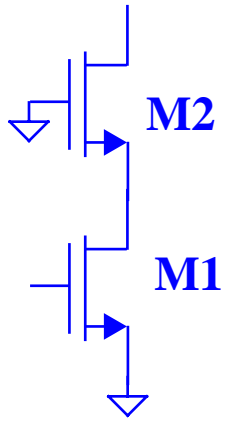

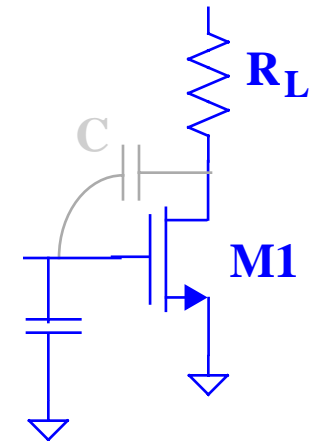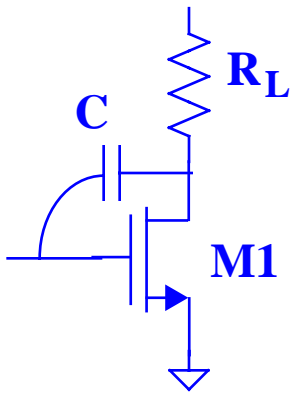
- Cascade of common source and common gate stages.
- Broader frequency band than common source
- Higher output impedance than common source



Cascode - increased output impedance

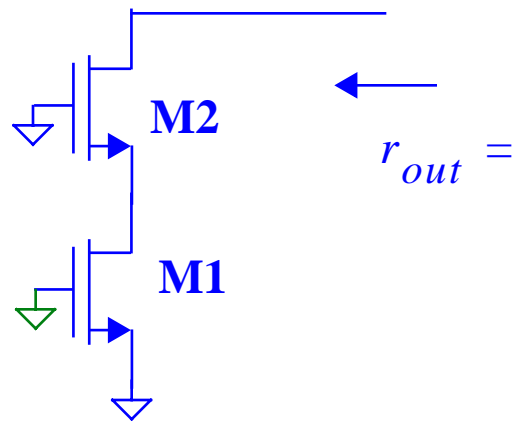

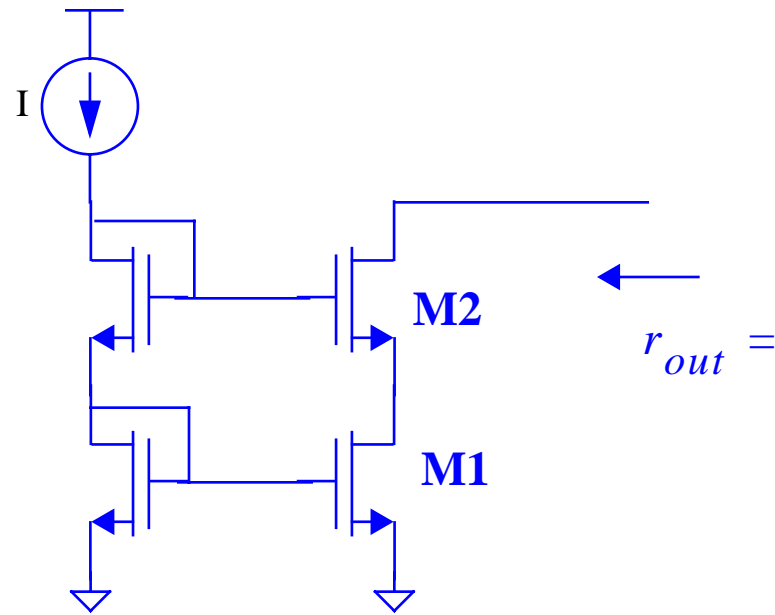
Cascode current source - increased output impedance



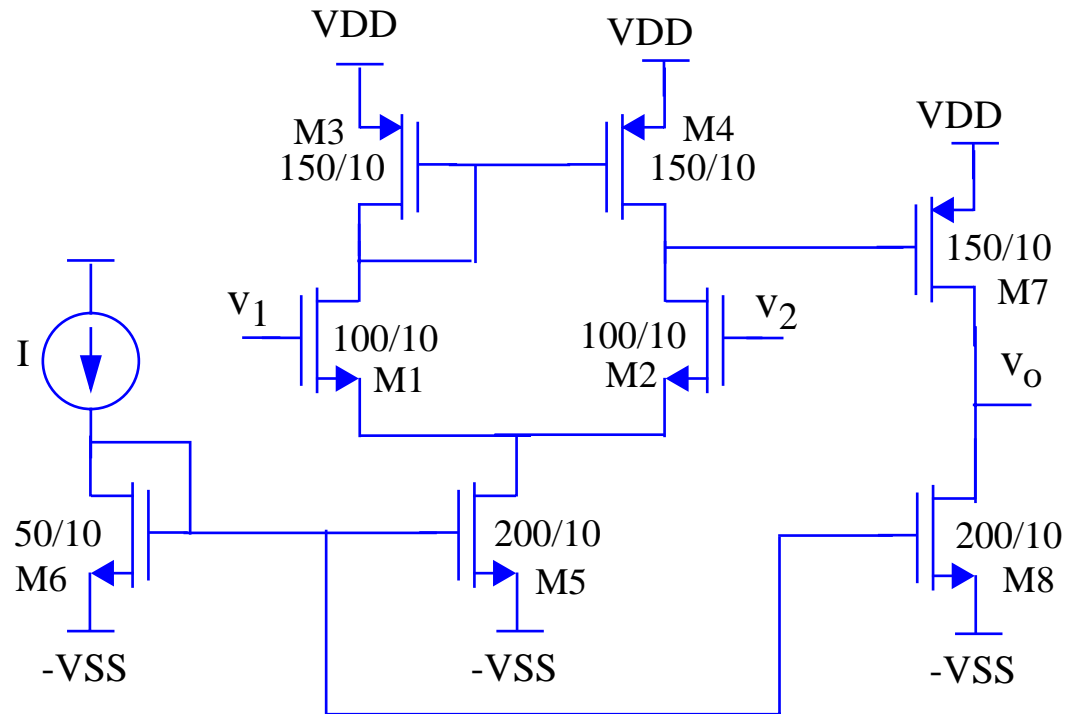Problem from previous year's exam#3

Calculate the midband gain ($v_o/(v_1-v_2)$) as a function of I (the reference current) for the two-stage CMOS opamp shown below. Assume that all of the biasing is working properly. Show all of your work!


$$\begin{aligned}\lambda_p &= 0.02 \\ \lambda_n &= 0.01 \\ \mu_p C_{ox} &= 20\mu\text{A}/\text{V}^2 \\ \mu_n C_{ox} &= 20\mu\text{A}/\text{V}^2\end{aligned}$$



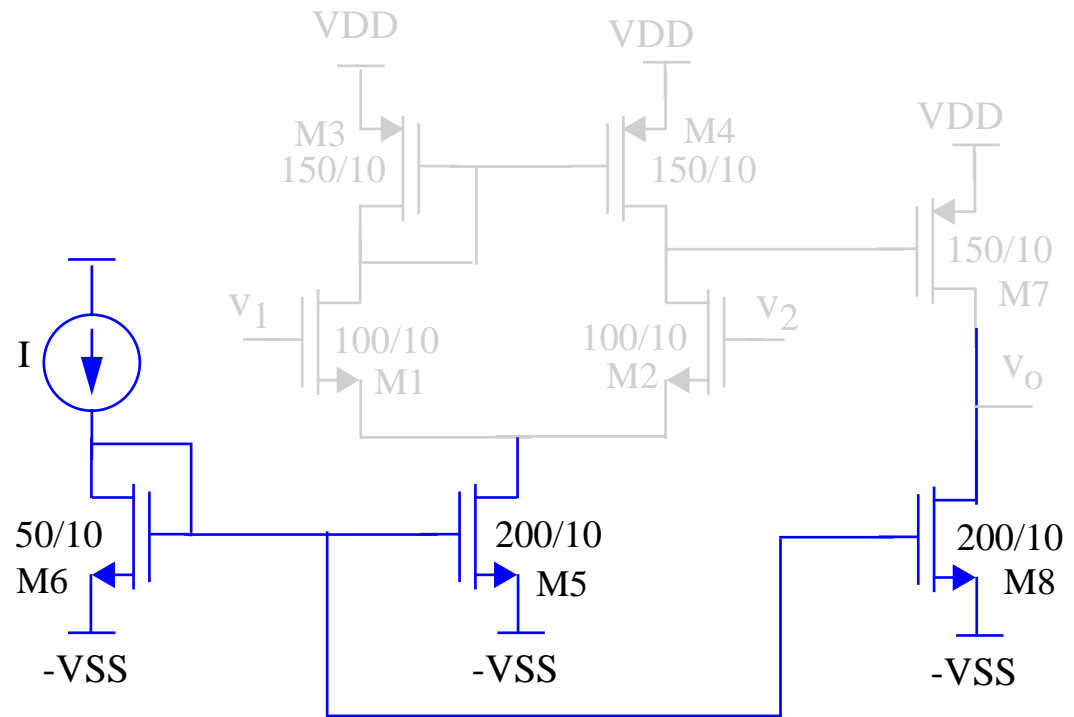1. Calculate currents of M5 and M8

Calculate the midband gain ($v_o/(v_1-v_2)$) as a function of I (the reference current) for the two-stage CMOS opamp shown below. Assume that all of the biasing is working properly. Show all of your work!

$$\begin{aligned}\lambda_p &= 0.02 \\ \lambda_n &= 0.01 \\ \mu_p C_{ox} &= 20 \mu\text{A}/\text{V}^2 \\ \mu_n C_{ox} &= 20 \mu\text{A}/\text{V}^2\end{aligned}$$




2. Calculate gain A_{diff} of the differential stage M5-M1-M2-M3--M4

Calculate the midband gain ($v_o/(v_1-v_2)$) as a function of I (the reference current) for the two-stage CMOS opamp shown below. Assume that all of the biasing is working properly. Show all of your work!

$$\begin{aligned}\lambda_p &= 0.02 \\ \lambda_n &= 0.01 \\ \mu_p C_{ox} &= 20 \mu\text{A}/\text{V}^2 \\ \mu_n C_{ox} &= 20 \mu\text{A}/\text{V}^2\end{aligned}$$

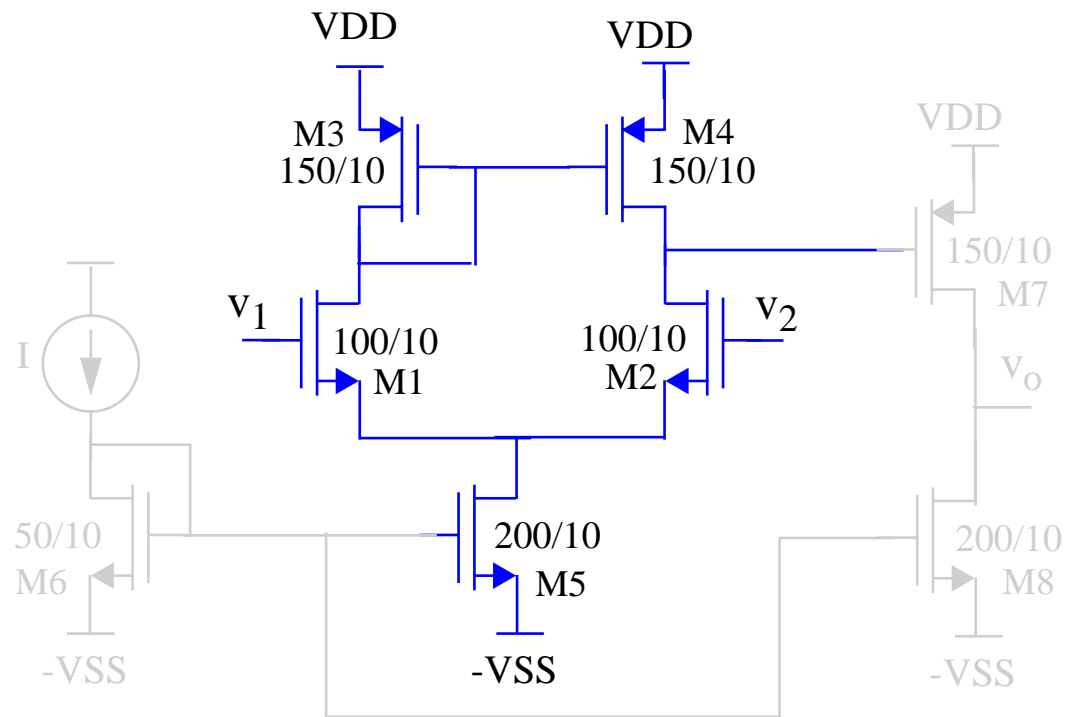
$$g_m = \sqrt{2\mu_n C_{ox}} \sqrt{\frac{W}{L}} \sqrt{I_D}$$



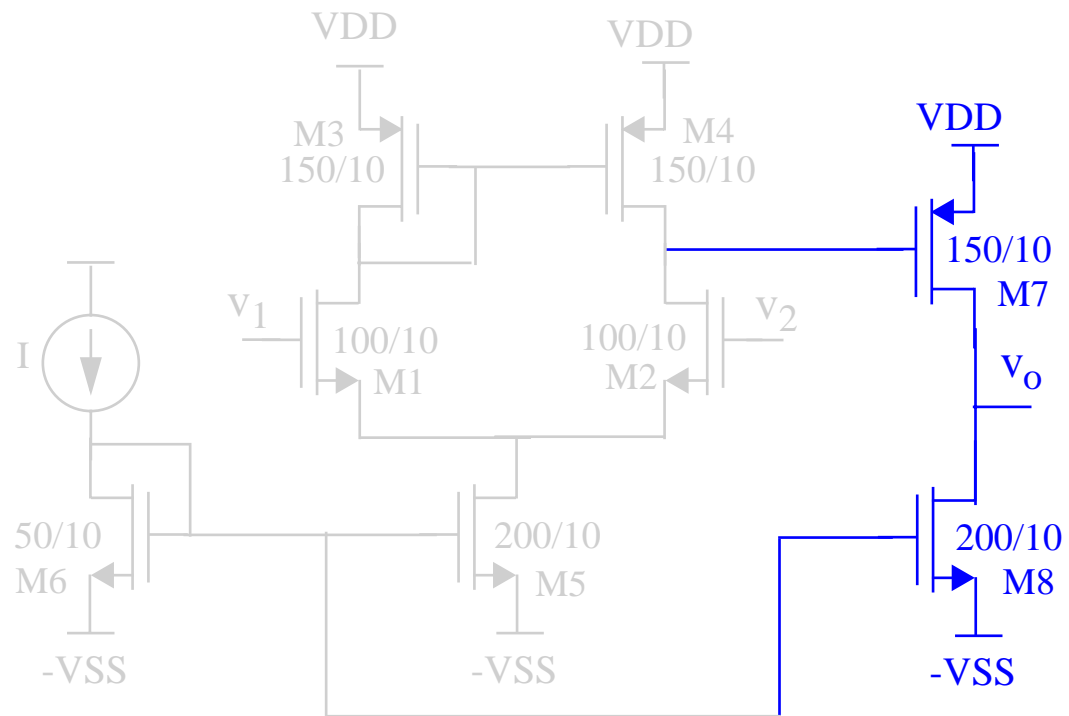3. Calculate gain of the second stage

Calculate the midband gain ($v_o/(v_1-v_2)$) as a function of I (the reference current) for the two-stage CMOS opamp shown below. Assume that all of the biasing is working properly. Show all of your work!

$$\begin{aligned}\lambda_p &= 0.02 \\ \lambda_n &= 0.01 \\ \mu_p C_{ox} &= 20\mu\text{A}/\text{V}^2 \\ \mu_n C_{ox} &= 20\mu\text{A}/\text{V}^2\end{aligned}$$



4. Combine gain of both stages

Calculate the midband gain ($v_o/(v_1-v_2)$) as a function of I (the reference current) for the two-stage CMOS opamp shown below. Assume that all of the biasing is working properly. Show all of your work!

$$\begin{aligned}\lambda_p &= 0.02 \\ \lambda_n &= 0.01 \\ \mu_p C_{ox} &= 20\mu\text{A}/\text{V}^2 \\ \mu_n C_{ox} &= 20\mu\text{A}/\text{V}^2\end{aligned}$$

