



# Frequency Response

- Sometimes we will design analog circuits to attenuate certain frequencies while amplifying others --- **Filters** and **decoupling circuits**
- In all cases there will be some finite bandwidth due to the nonidealities associated with the transistors and other components
- The output signal **phase** will also be shifted differently (relative to the input signal) as a function of frequency
- For analog design we generally view **plots** of the **magnitude** and **phase** as a function of frequency,  $\omega$ , radians/sec to understand these behaviors

- If we consider only frequency responses to design the circuit, how do we know what is happening in terms of the transient response? And do we care?

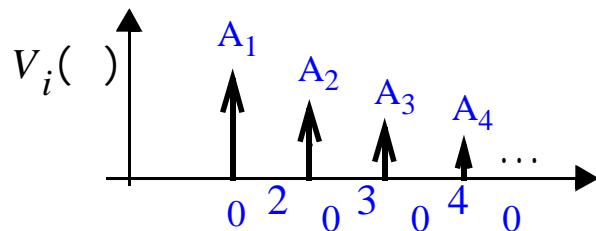
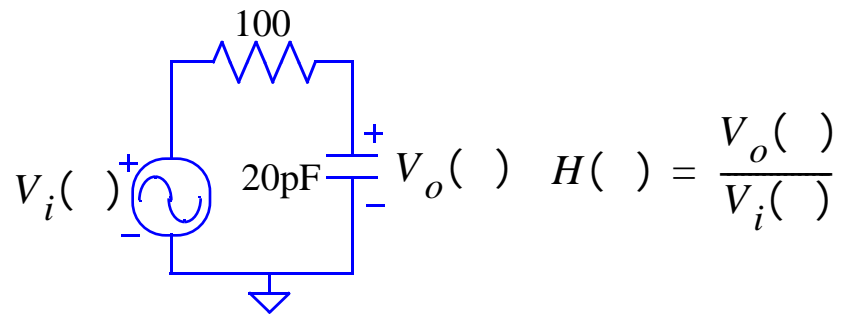
## Simple RC Circuit Example

- For analog design we generally view **plots** of the **magnitude** and **phase** as a function of frequency,  $\omega$ , radians/sec




$$V_i(t) = a_{avg} + \sum_{n=1} A_n \cos(n \omega t - \phi_n)$$

# Transfer Function Magnitude and Phase

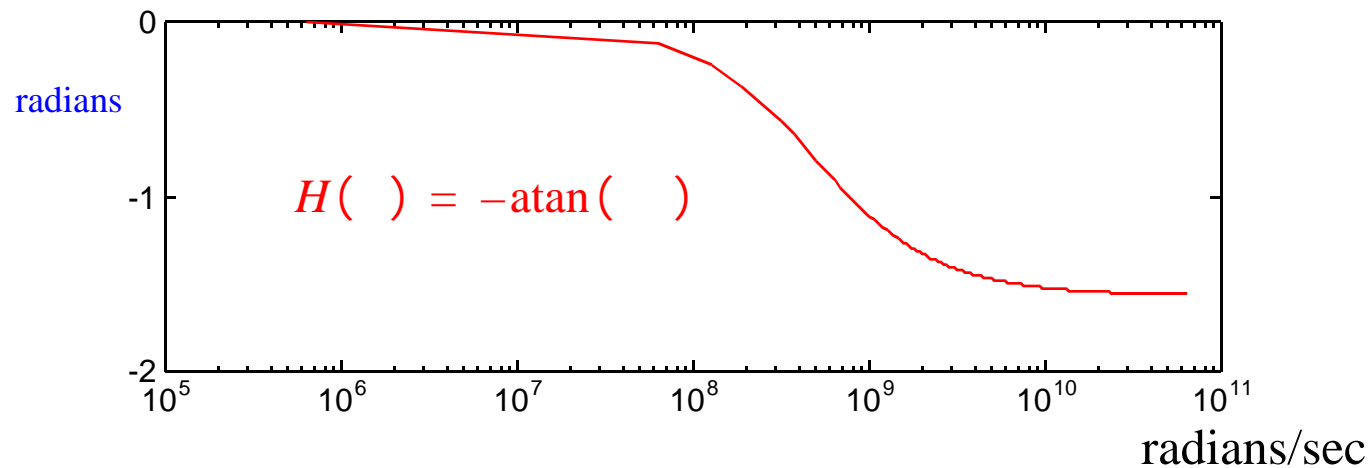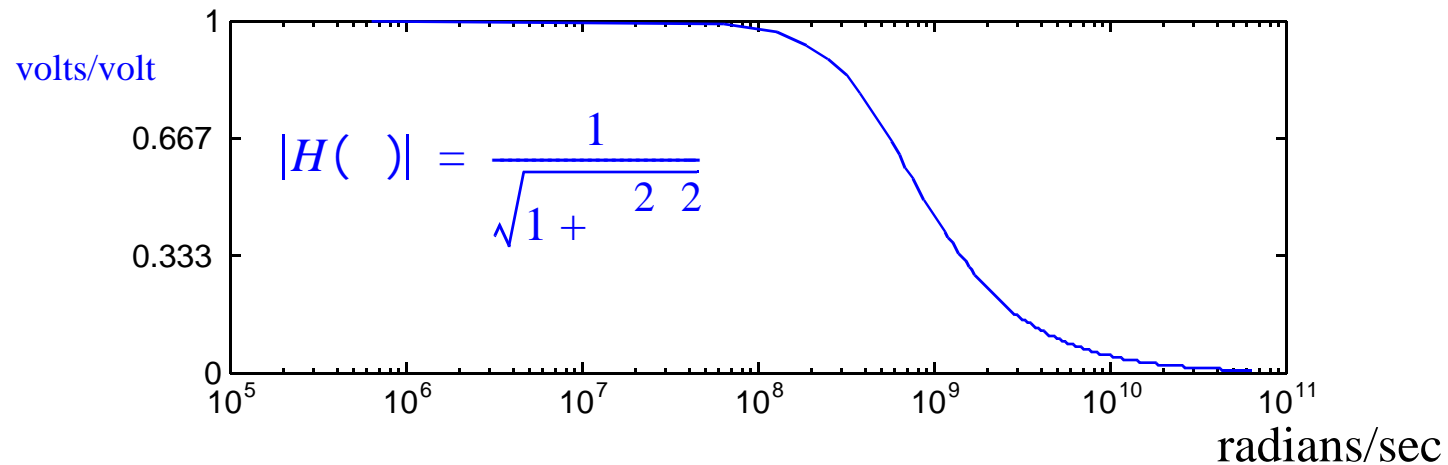


- The steady state response of a cosine input signal is modified in terms of phase and magnitude as displayed on the plots

# Steady State Response

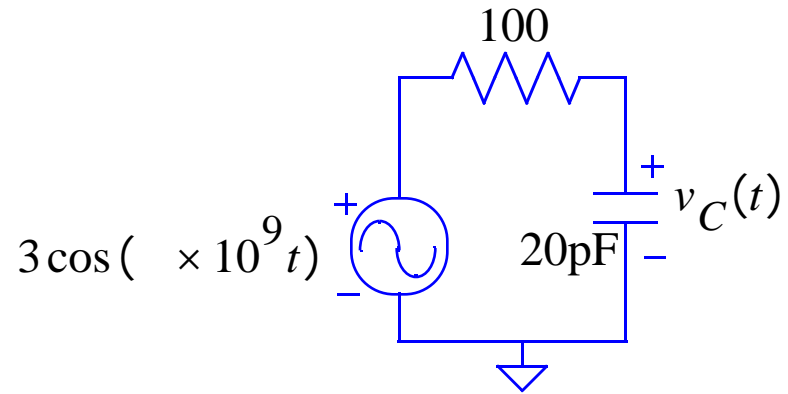

$$v_{in} = 3 \cos(\times 10^9 t)$$


steady state  
response

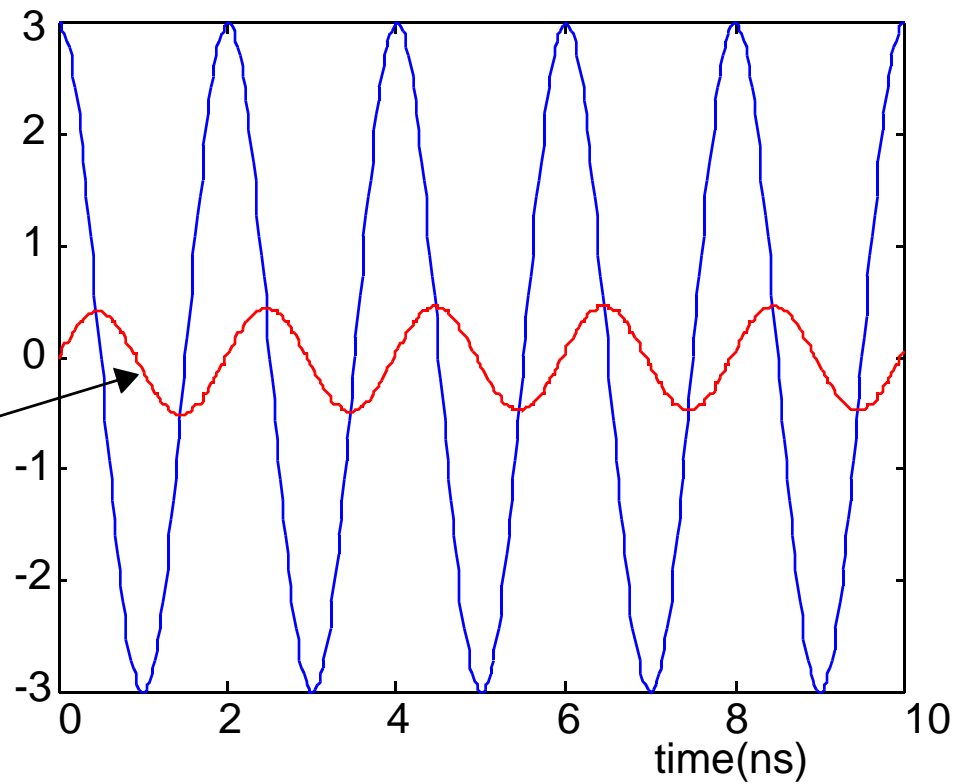

## Change in SS Response as Frequency is Varied

- Note that lower frequency signals have less attenuation of magnitude and less phase shift, as can be seen from the frequency domain plots


$$v_{in} = 3 \cos(\times 10^8 t)$$

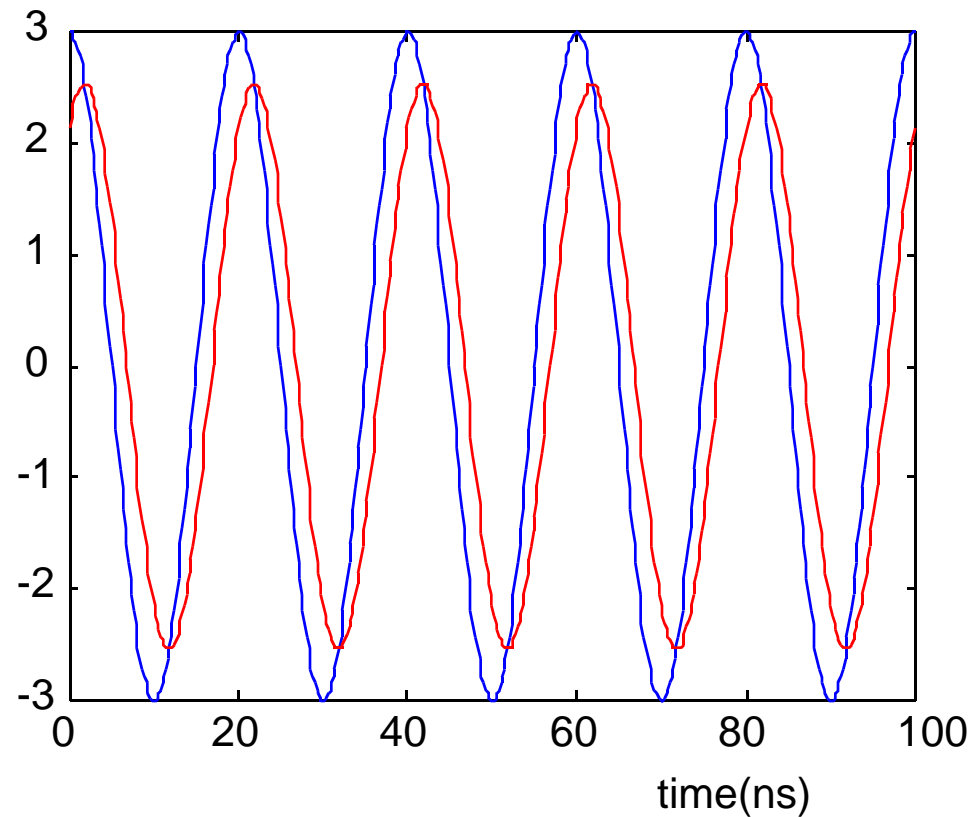

# High Frequency Response

- For frequencies significantly beyond the breakpoint in the magnitude plot, the response will start to vanish


$$v_{in} = 3 \cos(\times 10^{10} t)$$

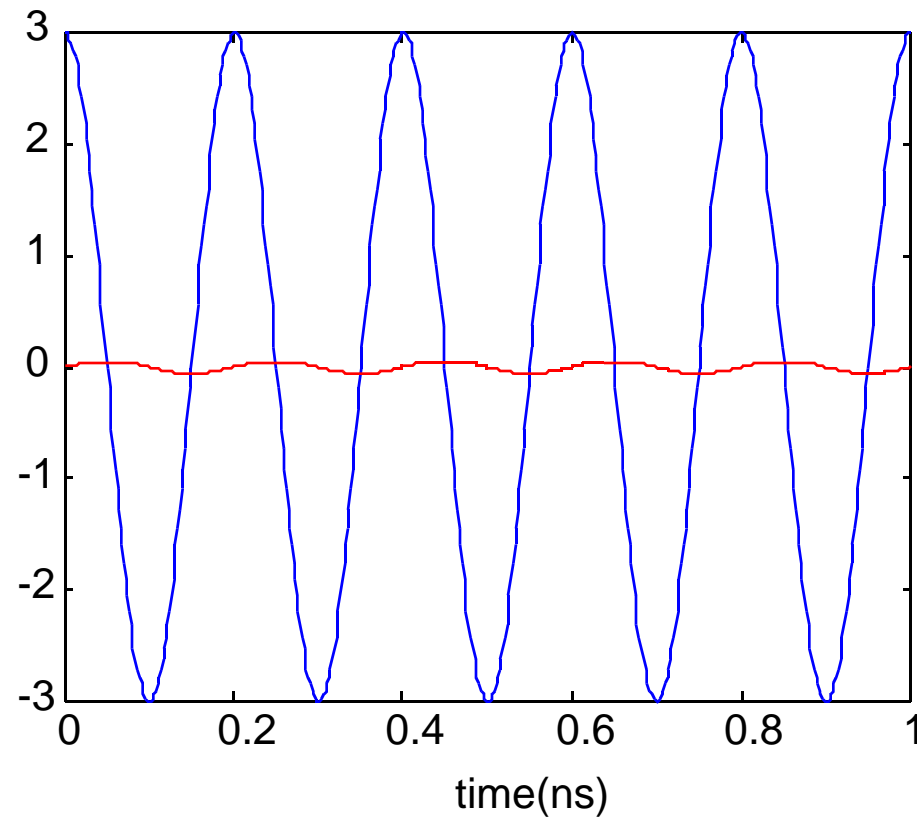
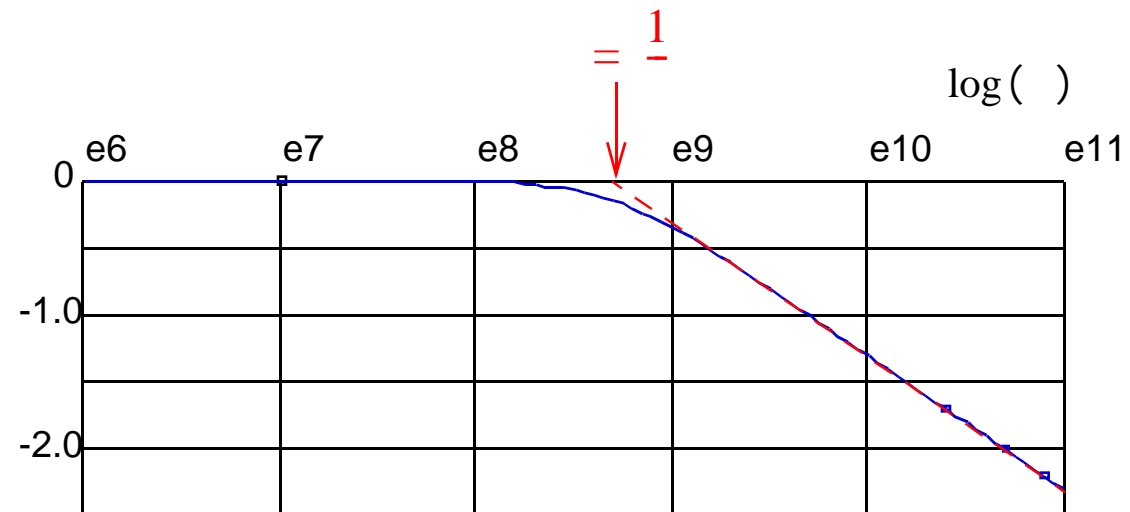
## Magnitude on a log Scale

- The breakpoints in these frequency domain characteristics are related to the **natural frequencies** of the circuit
- Plotting the magnitude on a log-log scale we can see this relationship
- For our RC example, the time constant,  $\tau$ , is 2ns, therefore the natural frequency is  $5e8$ .


$$\log \frac{1}{\sqrt{1 + \omega^2 \tau^2}}$$


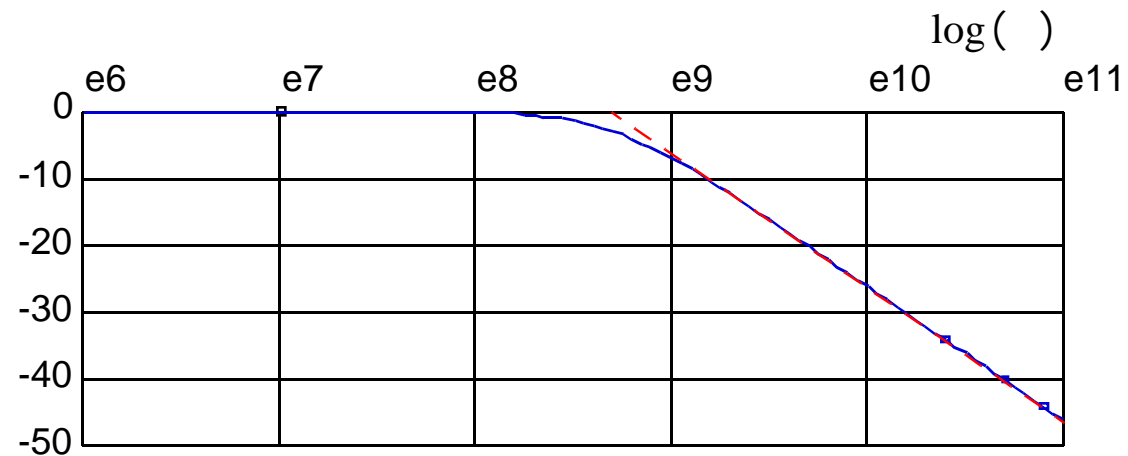
## Magnitude on a decibel (dB) Scale

- Magnitudes are generally plotted on a dB scale:

$$20 \log \frac{1}{\sqrt{1 + \omega^2 \tau^2}}$$




- Magnitude (for this single time constant example) falls off at asymptotic rate of 20dB/decade, or 6dB/octave (an octave is a 2x change in frequency)
- This relation to circuit natural frequencies also holds for higher order circuits
- Allows us to quickly estimate (visualize) the frequency response based on the natural frequencies



# Natural Frequencies

- You may not have seen Laplace Transforms yet, but like phasors they represent a transformation to the (complex) frequency domain that makes it easy to solve for natural frequencies,  $s$ 's, or reciprocal time constants, 's

$s$   $j$

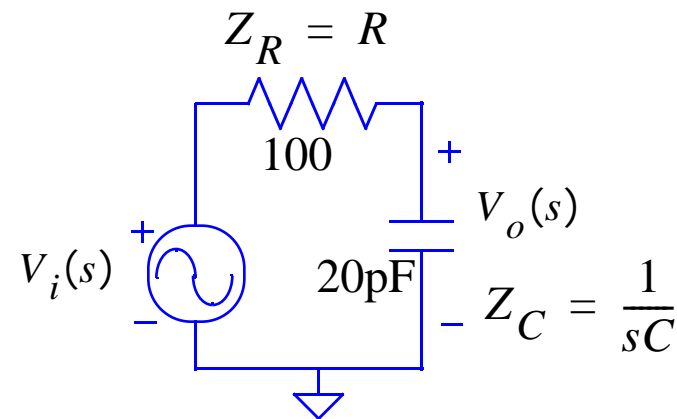

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{\frac{1}{sC}}{\frac{1}{sC} + R}$$

# Poles

- With Laplace transform terminology there is a pole at  $-1/RC$  for this RC circuit
- A pole represents a value for  $s$  for which  $H(s)$  is infinite.

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{1}{1 + sRC} = \frac{\frac{1}{RC}}{\frac{1}{RC} + s}$$

- However, the transfer function is *not* infinite at the real frequency,

$$H(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{1}{1 + j\omega RC}$$

## Poles and Natural Frequencies

- It is important to note that natural frequencies and time constants have positive magnitude, while poles are negative (negative real parts for RLC)

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{1}{1 + sRC} = \frac{1}{1 + \frac{s}{p}}$$

- $p$  is equal to  $1/RC$  and can be thought of as the natural frequency
- The pole which makes  $H(s)$  infinite, however, is  $s=-p$
- We know that if we solved for the time domain response, that the  $s$  term in the assumed solution form would have to be a negative value:

$$Ae^{st}$$

## Bode Plot

- Once we know the magnitude of the pole,  $p$ , for this transfer function, we can use straight line estimates (on the log-log scale) to approximate the frequency response plot

$$H(\omega) = \frac{V_o(\omega)}{V_i(\omega)} = \frac{1}{1 + j\omega RC} = \frac{1}{1 + \frac{j\omega}{p}}$$

$$|H(\omega)| = \frac{|1|}{\left|1 + \frac{j\omega}{p}\right|} \quad 20\log(|1|) - 20\log\left|1 + \frac{j\omega}{p}\right| \quad \text{in dB}$$

- We calculate the asymptotes for the magnitude of this function


$$\text{For } \omega \ll p \quad |H(\omega)| \approx 0\text{dB}$$

$$\text{For } \omega \gg p \quad |H(\omega)| \approx -20\log\frac{\omega}{p} = -[20\log(\omega) - 20\log(p)]\text{(dB)}$$

- Where do these asymptotes intersect?
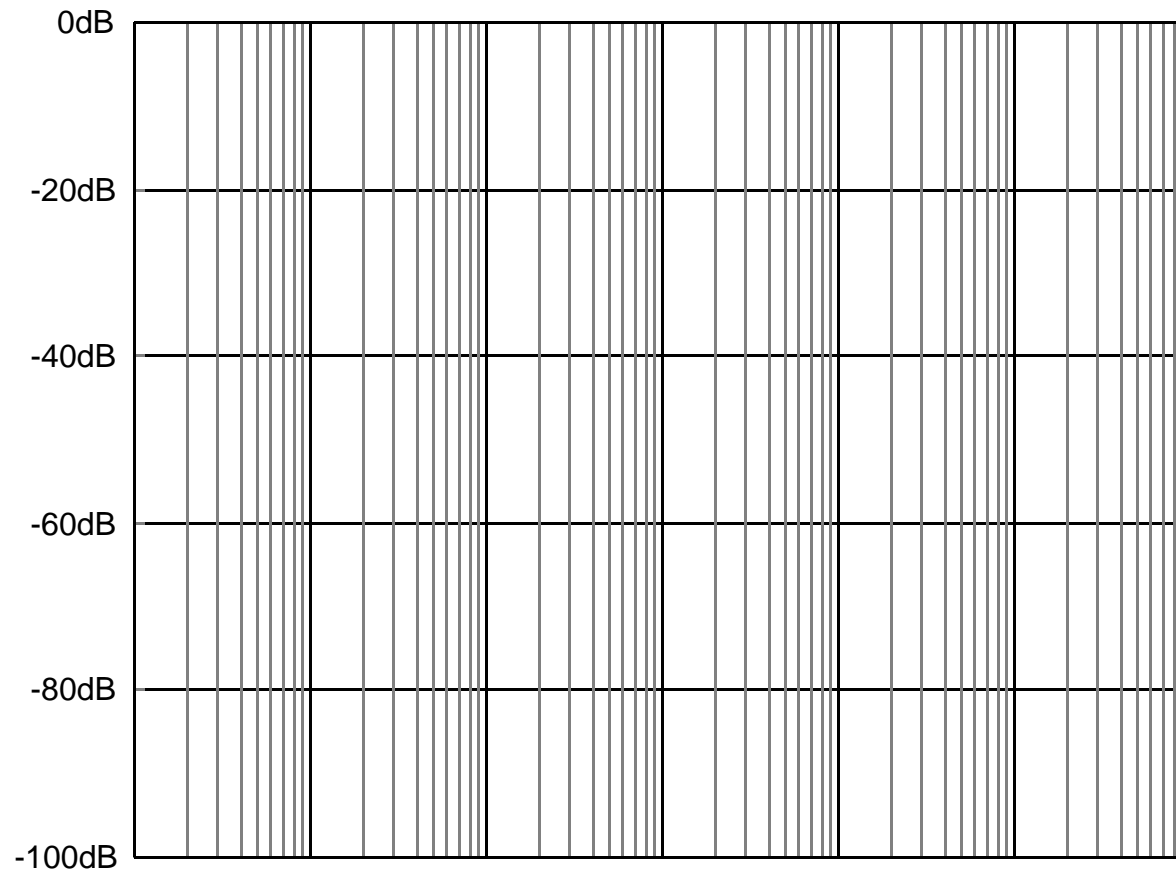
# Bode Plot

- With frequency plotted on a log scale, we can quickly sketch the asymptotes
- The maximum error at the breakpoint in the curve is known to be 3dB



## Bode Plot: Phase


- The phase plot (for this single pole) can be sketched in a similar way

$$H(s) = \frac{1}{1 + \frac{j}{p}} \quad \angle H(s) = -\text{atan} \frac{1}{p}$$

For  $\ll p$   $\angle H(s) \approx 0$  (radians)  $\approx 0$  degrees


For  $\gg p$   $\angle H(s) \approx -\frac{\pi}{2}$  (radians)  $\approx -90$  degrees

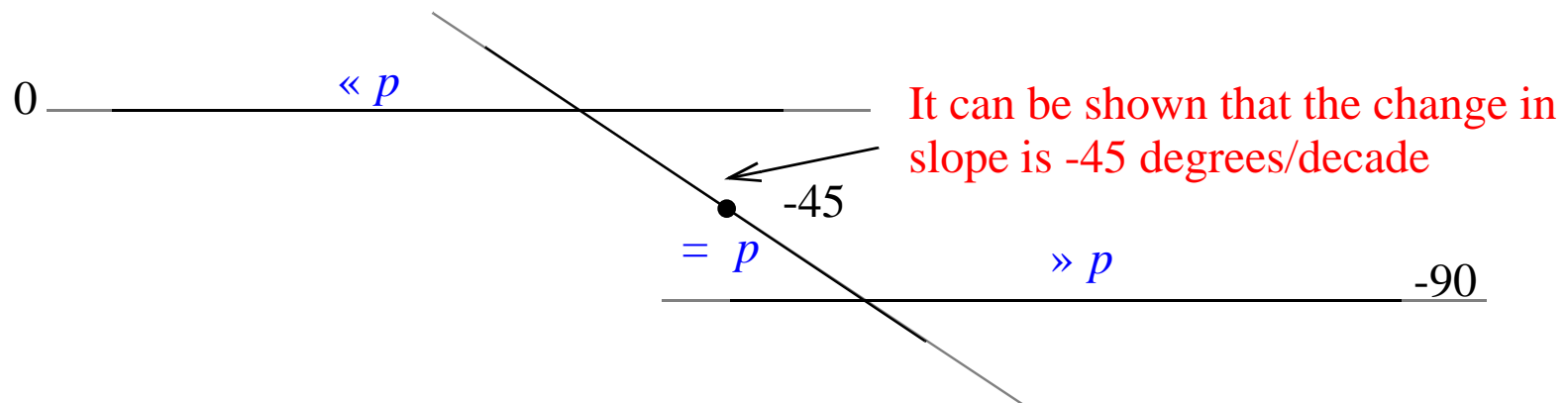For  $= p$   $\angle H(s) \approx -\frac{\pi}{4}$  (radians)  $\approx -45$  degrees



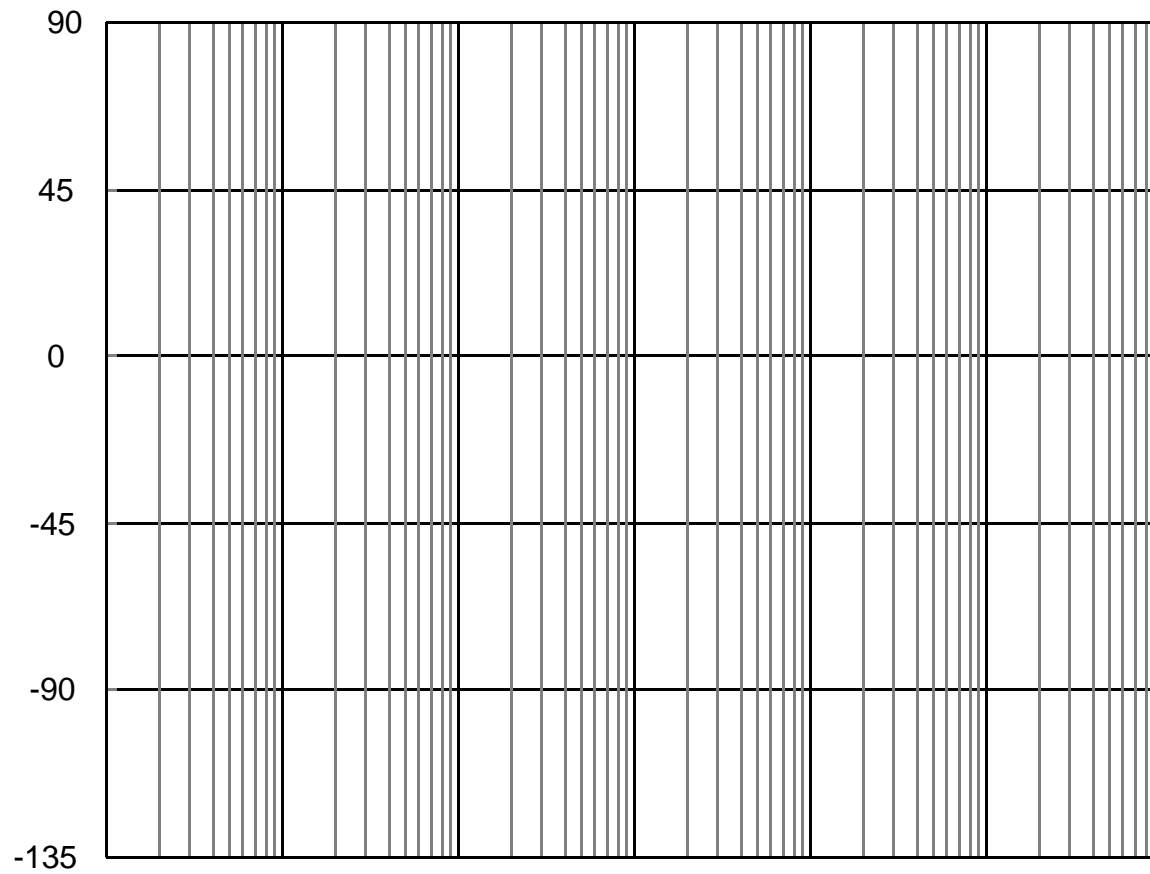
# Phase Plot

- Maximum error at the breakpoint is 5.7 degrees


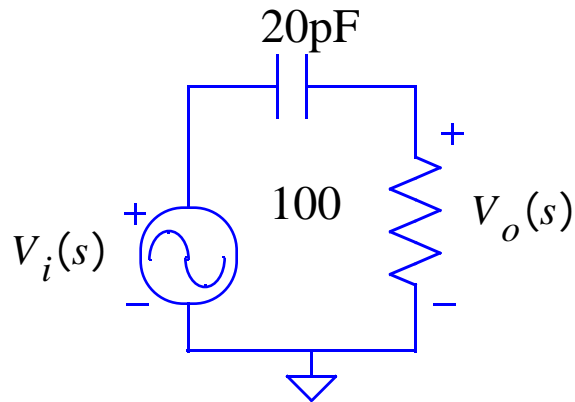
## Poles and Zeros

- We'll solve circuits in terms of  $s$ , just like the book
- But we'll only consider sinusoidal steady state problems, therefore,  $s = j\omega$
- We'll also use the terminology of **pole** to refer to the natural frequency magnitude
- A related term is a **zero**
- Example of a circuit with a zero at  $s=0$  --- Actually a transmission zero at  $s=0$  in this case:




$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{R}{\frac{1}{sC} + R} = \frac{sRC}{1 + sRC}$$


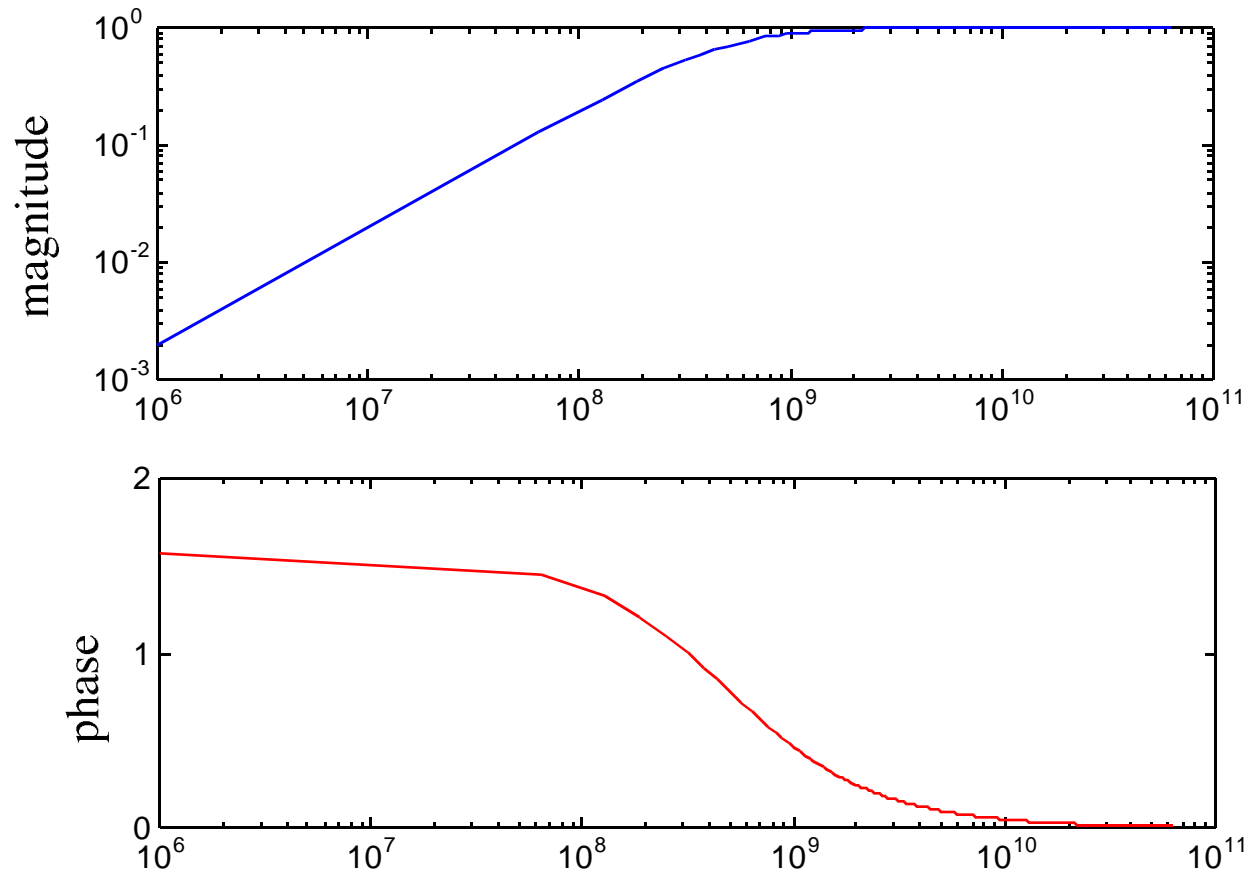
## Magnitude on a decibel (dB) Scale

- Swapping the R and C changes a low-pass filter into a high-pass filter



- The values of the zeros and poles signify the breakpoints and direction

## Bode Plot


- Once we know the pole and zero values we can apply a Bode approximation

$$H(\omega) = \frac{V_o(\omega)}{V_i(\omega)} = \frac{j\omega RC}{1 + j\omega RC} = \frac{j\omega p}{1 + j\omega p}$$
$$|H(\omega)| = \frac{\left| \frac{j\omega p}{1 + j\omega p} \right|}{\left| 1 + j\omega p \right|} = 20\log \left| \frac{j\omega p}{1 + j\omega p} \right| = 20\log \left| j\omega p \right| - 20\log \left| 1 + j\omega p \right|$$

- Pole term is the same as before
- Zero term is 0dB at breakpoint, and increasing at a rate of 20dB/decade otherwise
- Note that zeros create asymptotes that are increasing with frequency, while poles create asymptotes that are decreasing with frequency
- We add all of the asymptotes together to get the overall response
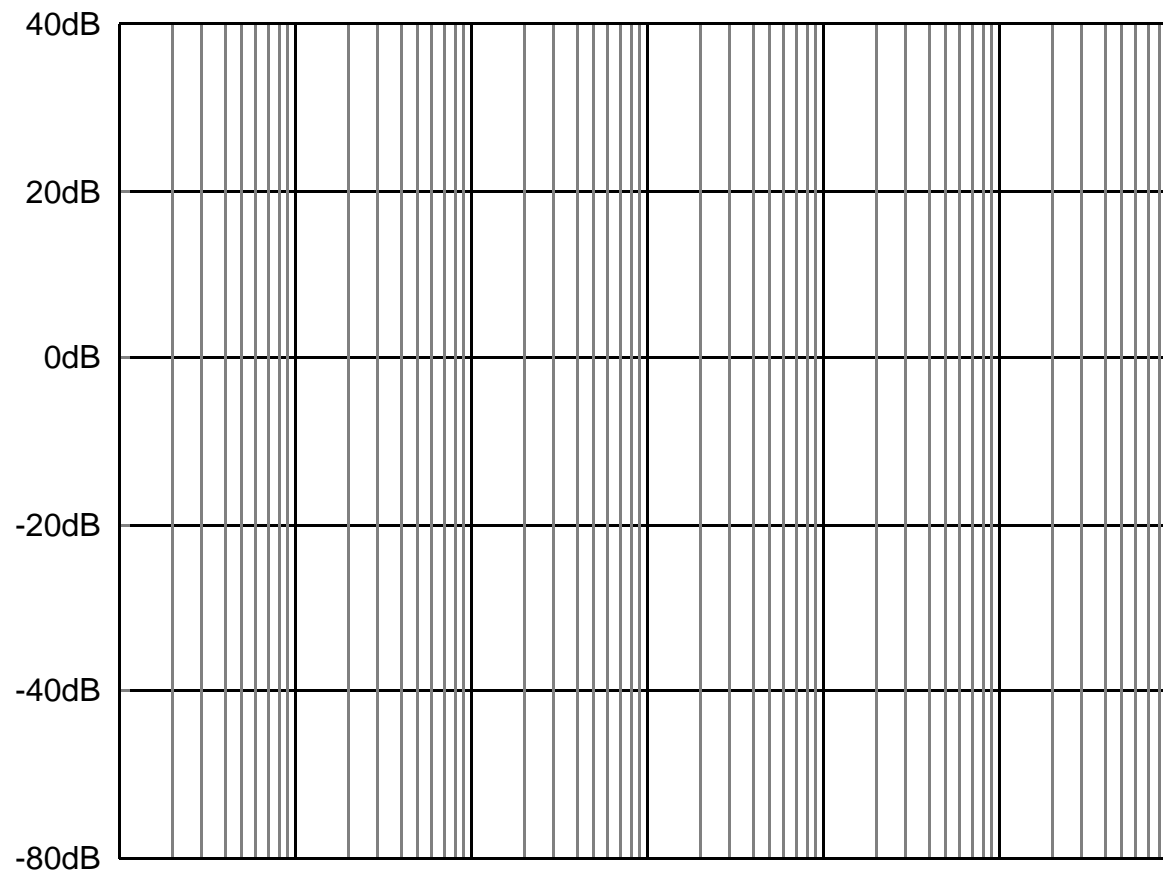
# Bode Plot

- For each term in the transfer function expression:
  1. Find the direction and slope of the asymptote
  2. Find one point through which the asymptote passes



## Poles and Zeros of Larger Circuits


- Bode plots can be used for higher-order circuits too
- But higher order circuits will have more poles and zeros, and transfer functions of the form:

$$H(s) = K \frac{\left(1 + \frac{j\omega}{z_1}\right) \left(1 + \frac{j\omega}{z_2}\right) \dots \left(1 + \frac{j\omega}{z_m}\right)}{\left(1 + \frac{j\omega}{p_1}\right) \left(1 + \frac{j\omega}{p_2}\right) \dots \left(1 + \frac{j\omega}{p_n}\right)}$$

- We would expect that there will always be more finite poles than zeros, why?
  
- What does the K-term represent?

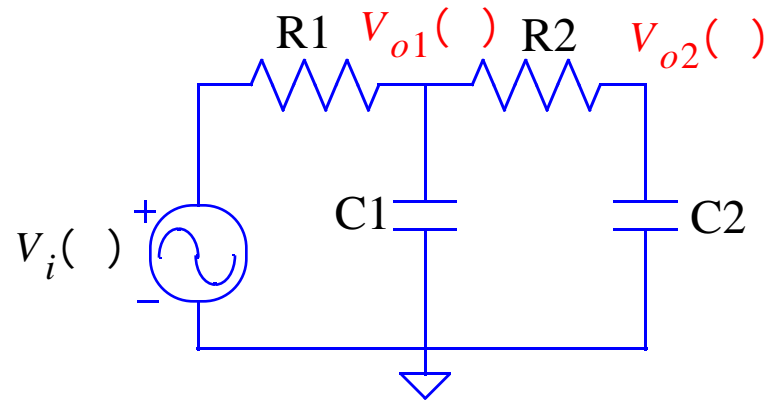
## 2nd Order Example

- The following RC circuit will have 2 poles and 1 zero for the transfer function from the input to node 1 or 2:



$$H_i(\omega) = K \frac{1 + \frac{j}{z_1}}{1 + \frac{j}{p_1} \quad 1 + \frac{j}{p_2}}$$

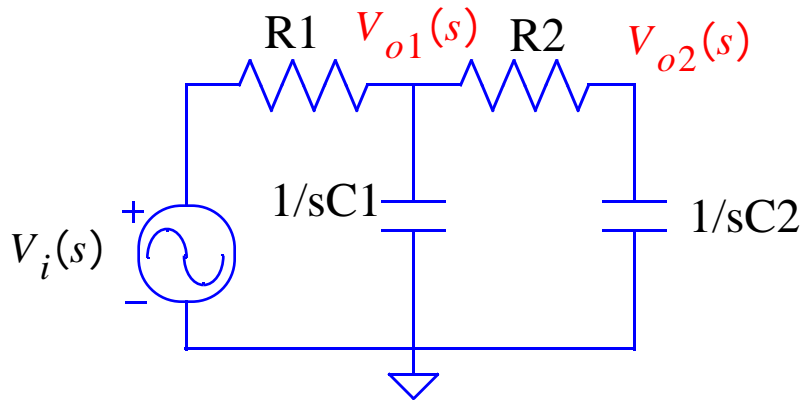
- You may know how to solve for the poles (natural frequencies) of a circuit by formulating the differential equations and using an assumed solution of:  $Ae^{st}$
- An easier way is to use the following circuit to solve for the poles and zeros:



$$H_i(s) = \frac{V_o(s)}{V_i(s)}$$
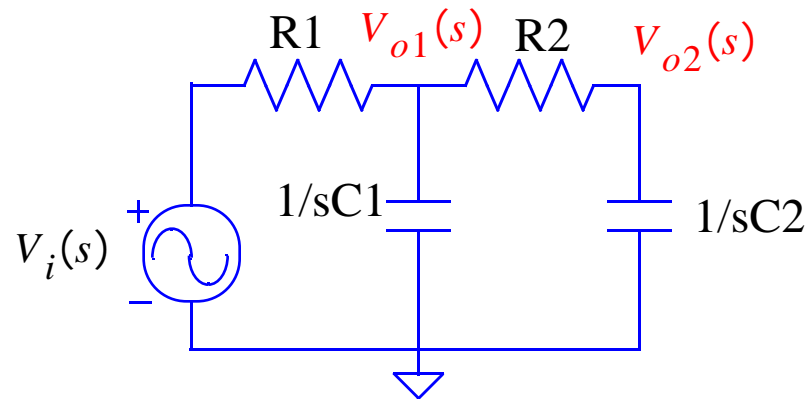
## 2nd Order Example

- Write the nodal equations just like you would for phasors




- Transfer functions to nodes 1 and 2 are:

$$H_1(s) = \frac{V_o(s)}{V_i(s)} = \frac{\frac{1}{R_1 R_2 C_1 C_2} (1 + s R_2 C_2)}{s^2 + s \left( \frac{1}{R_2 C_2} + \frac{1}{R_2 C_1} + \frac{1}{R_1 C_1} \right) + \frac{1}{R_1 R_2 C_1 C_2}}$$

$$H_2(s) = \frac{V_o(s)}{V_i(s)} = \frac{\frac{1}{R_1 R_2 C_1 C_2}}{s^2 + s \left( \frac{1}{R_2 C_2} + \frac{1}{R_2 C_1} + \frac{1}{R_1 C_1} \right) + \frac{1}{R_1 R_2 C_1 C_2}}$$

## Numerical Example

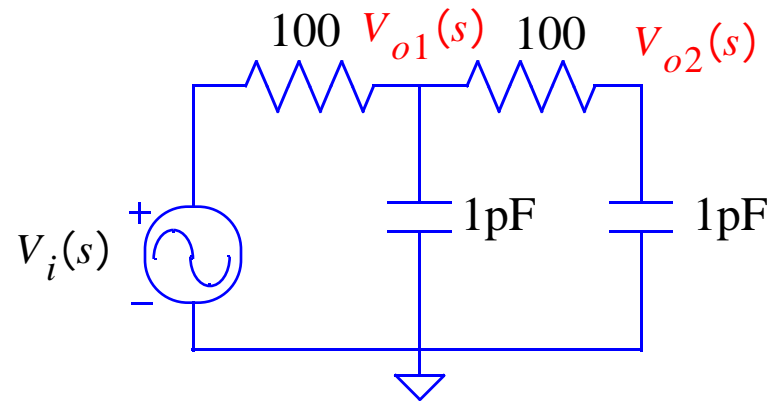

$$H_1(s) = \frac{\frac{(1 + 10^{-10} s)}{10^{-20}}}{s^2 + s(0.03 \times 10^{12}) + 10^{20}} = 10^{20} \frac{1 + \frac{s}{10^{10}}}{s^2 + s(0.03 \times 10^{12}) + 10^{20}}$$

- What is the dc gain?
- What is the zero? Does it represent a transmission zero?

## Numerical Example

- Rearrange the terms to recognize the poles

$$H_1(s) = 10^{20} \frac{1 + \frac{s}{z}}{s^2 + s(0.03 \times 10^{12}) + 10^{20}} = 10^{20} \frac{1 + \frac{s}{z}}{(s + p_1)(s + p_2)}$$

- Where:  $p_{1,2} = -(-1.5 \times 10^{10} \pm 1.118 \times 10^{10})$

$$H_1(s) = \frac{10^{20}}{p_1 p_2} \frac{1 + \frac{s}{z}}{\frac{s}{p_1} + 1 \quad \frac{s}{p_2} + 1}$$

1.0

- So we can write the sinusoidal steady state transfer function as:

$$H_1(j\omega) = \frac{1 + \frac{j\omega}{z}}{\frac{j\omega}{p_1} + 1 \quad \frac{j\omega}{p_2} + 1}$$



## Numerical Example

- Transfer function can be expressed as the product of the pole and zero terms:

$$H_1(j\omega) = \frac{1 + \frac{j\omega}{z}}{\frac{j\omega}{p_1} + 1} \frac{1}{\frac{j\omega}{p_2} + 1} = \left(1 + \frac{j\omega}{z}\right) \frac{1}{\frac{j\omega}{p_1} + 1} \frac{1}{\frac{j\omega}{p_2} + 1}$$


- If we measure the magnitude in dB, then all of the terms can be separated:

$$|H_1(j\omega)|_{dB} = 20 \log \left[ \left(1 + \frac{j\omega}{z}\right) \frac{1}{\frac{j\omega}{p_1} + 1} \frac{1}{\frac{j\omega}{p_2} + 1} \right] =$$

$$20 \log \left[ 1 + \frac{j\omega}{z} \right] + 20 \log \left[ \frac{1}{\frac{j\omega}{p_1} + 1} \right] + 20 \log \left[ \frac{1}{\frac{j\omega}{p_2} + 1} \right]$$
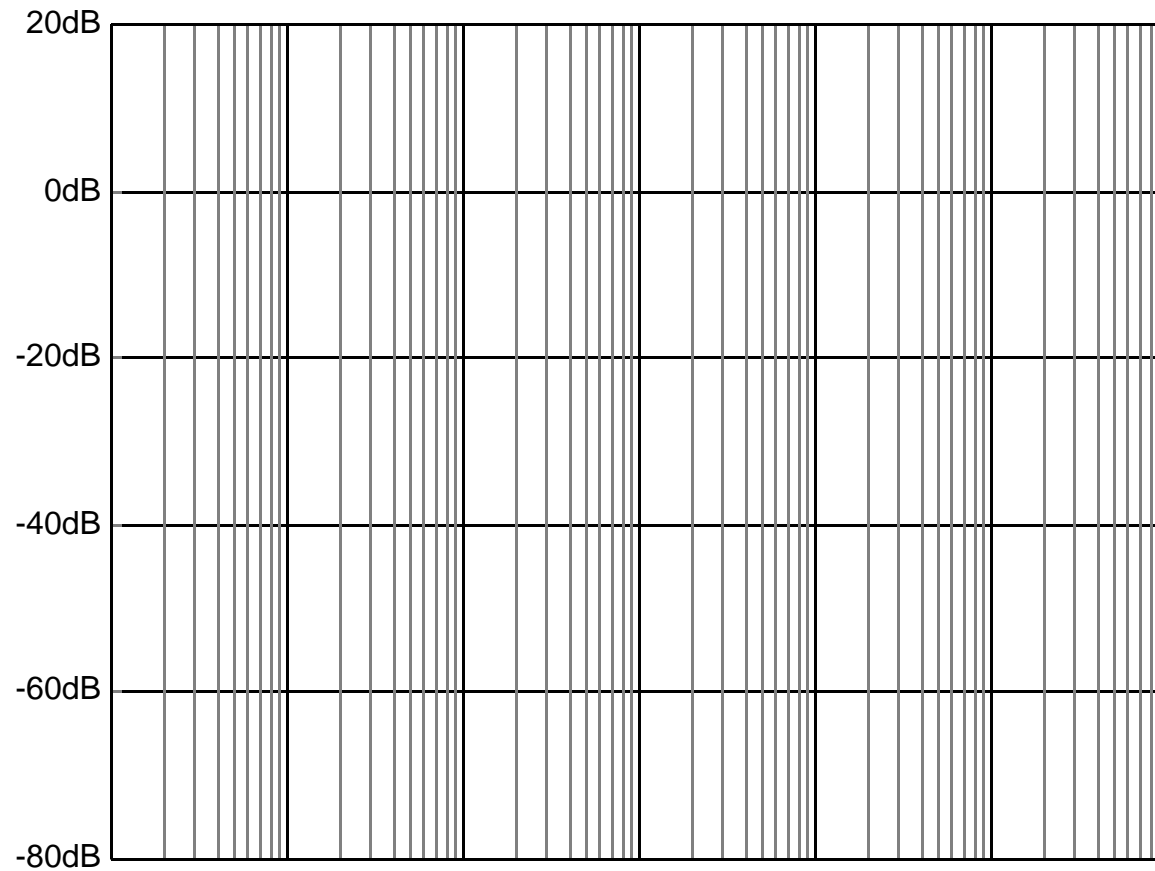
# Bode Plot

- Add the asymptotes for each of the individual pole and zero contributions



## Phase Numerical Example

- Starting again with the transfer function in product form:


$$H_1(j\omega) = \left(1 + \frac{j\omega}{z}\right) \frac{1}{\frac{j\omega}{p_1} + 1} \frac{1}{\frac{j\omega}{p_2} + 1}$$

- Each term represents a complex number which can be expressed in polar coordinate form

$$H_1(j\omega) = H_z \angle \text{atan} \frac{\omega}{z} \cdot H_{p1} \angle -\text{atan} \frac{\omega}{p_1} \cdot H_{p2} \angle -\text{atan} \frac{\omega}{p_2}$$

- From which it is apparent that all of the phase angle terms add
- So we can add the phase-shift asymptotes too


# Phase Plot

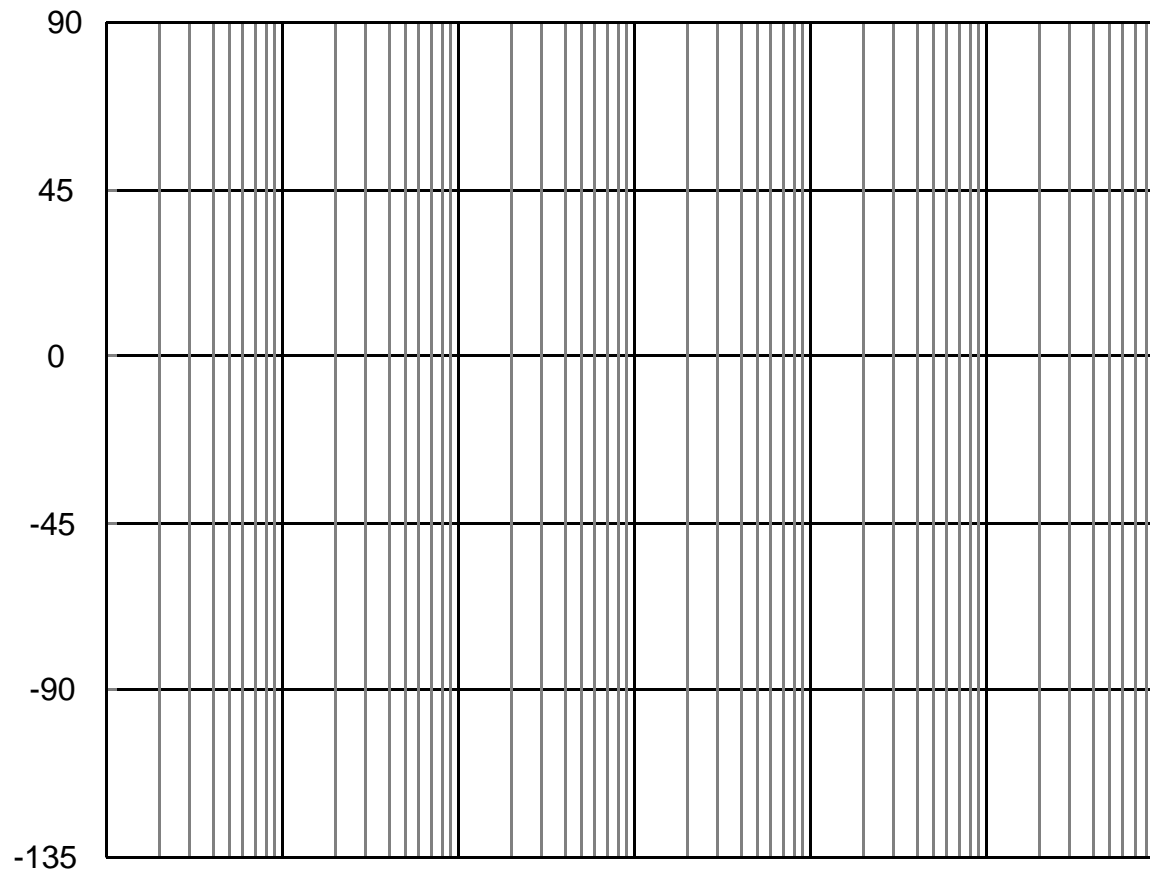
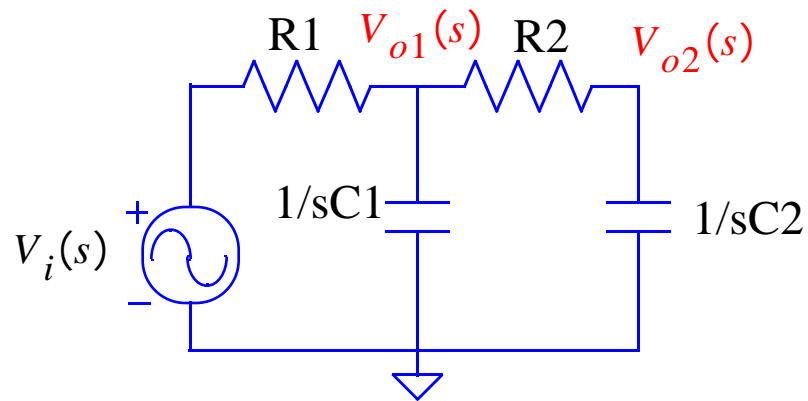
## Zeros at Node 2


$$H_2(j\omega) = \frac{1}{\frac{j\omega}{p_1} + 1} \frac{1}{\frac{j\omega}{p_2} + 1}$$

- The zero at node 1 is  $1/R_2C_2$ , but the response at node 2 does not have any **finite zeros** --- does this make sense?


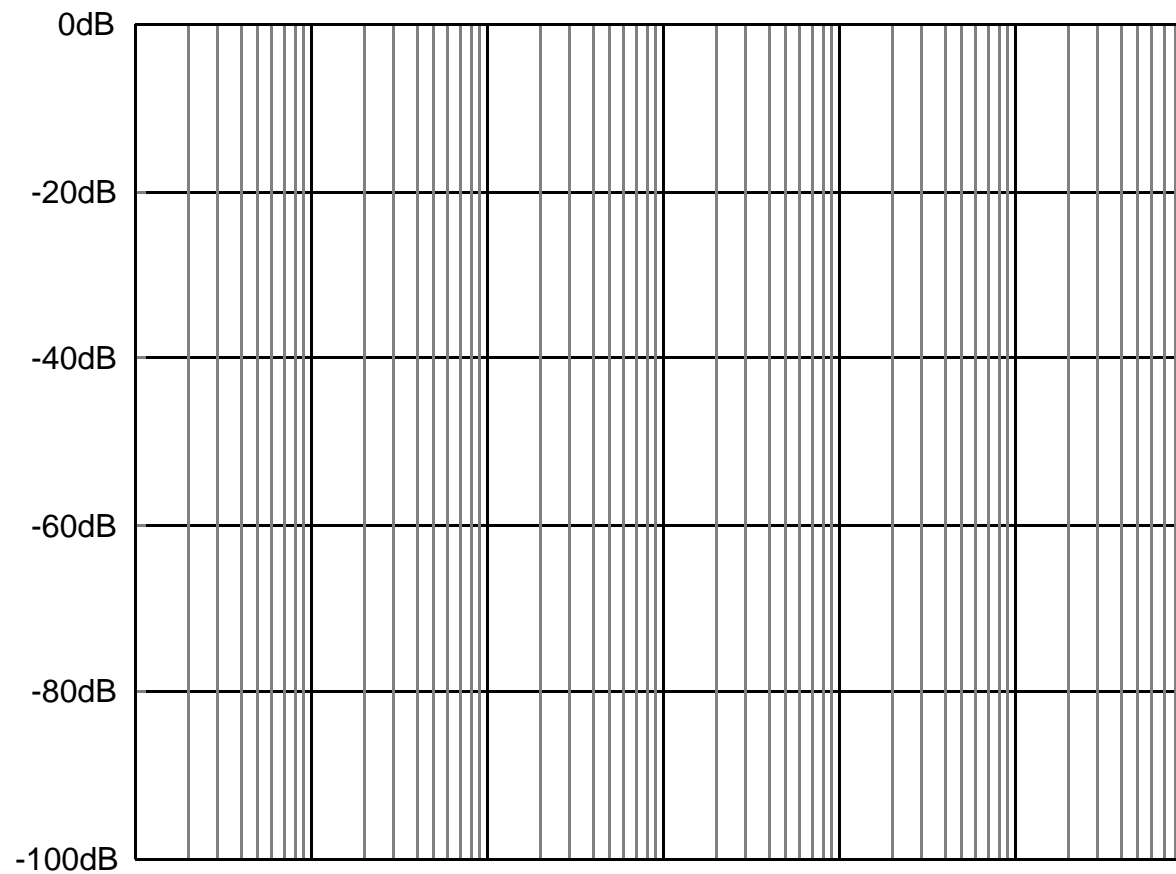
# Bode Plot

- The transfer functions share the same two poles, their responses are different due to the zero



# Phase Plot

