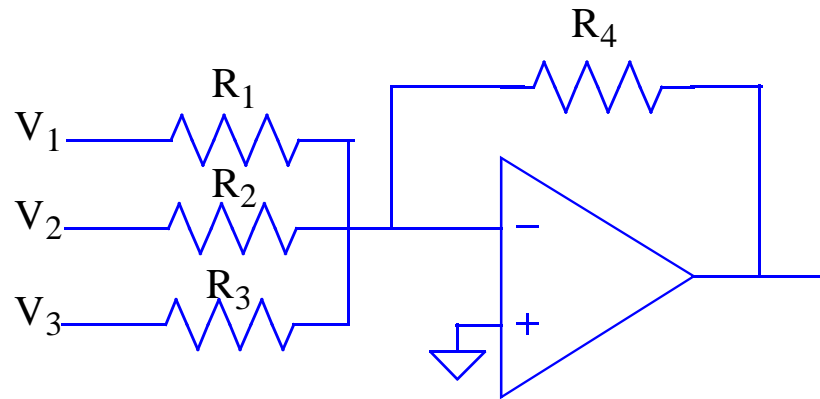



## Summing Amplifier Revisited

- Superposition can be used to easily evaluate summing amplifiers with infinite open loop gain


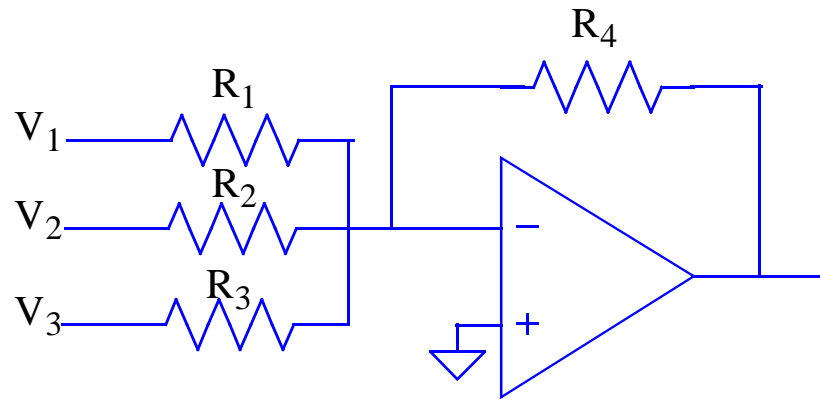
## Summing Amplifier Revisited

- Can we solve for the summing amplifier gain the same way when the open loop gain is finite?






## Other Opamp Nonidealities

- The open loop gain is generally so large that we can neglect its impact on the closed-loop circuit gain
- But a significant nonideality that we cannot ignore is the finite open-loop gain as a function of frequency
- **Parasitic capacitance** causes the gain to fall off at high frequency (can't make  $\omega_H$  infinite for any amplifier!)
- The gain may be designed to change with frequency to ensure stability ----  
**compensation**

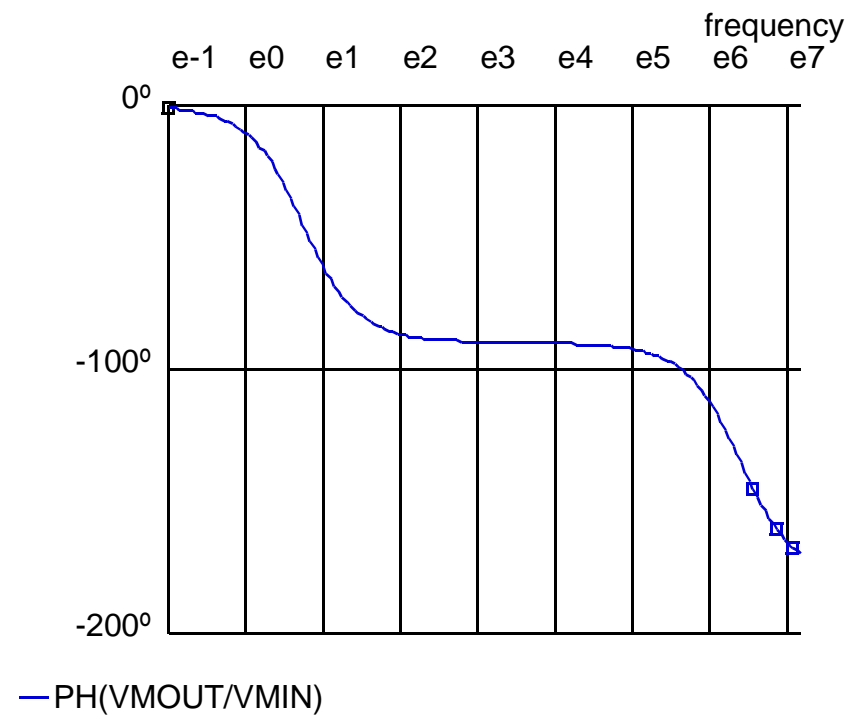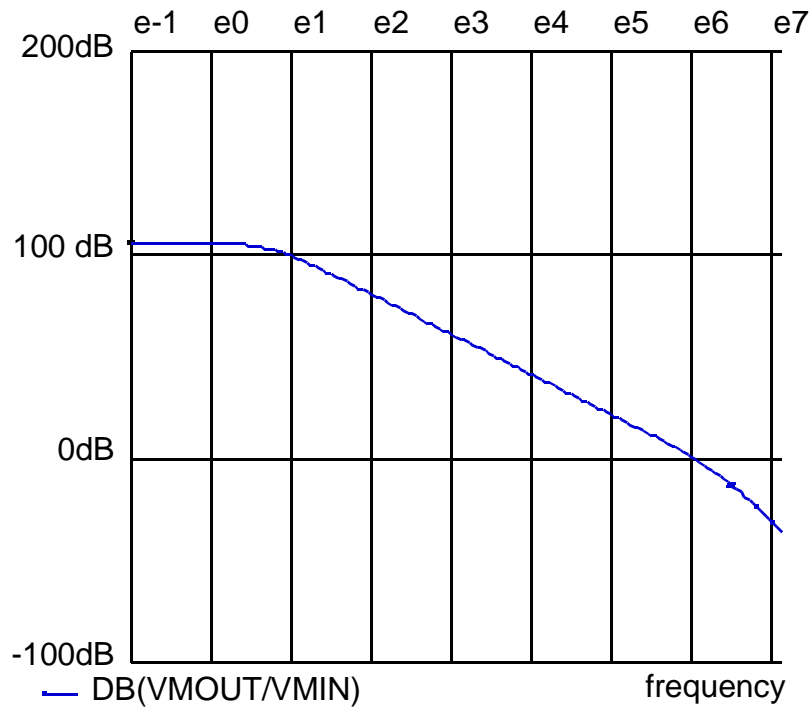
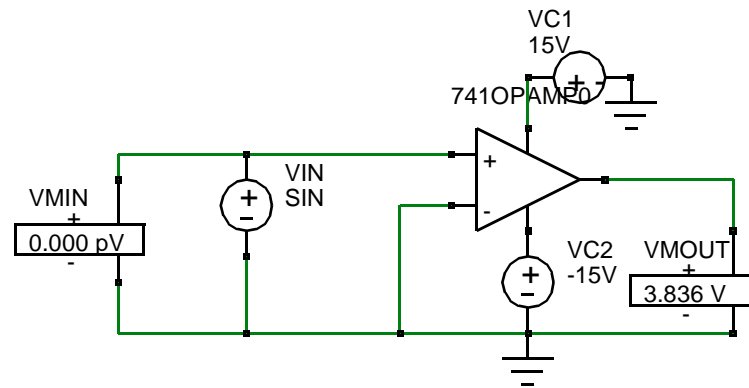
# 741 Opamp

- One of the most popular, general purpose opamps are the 741-type



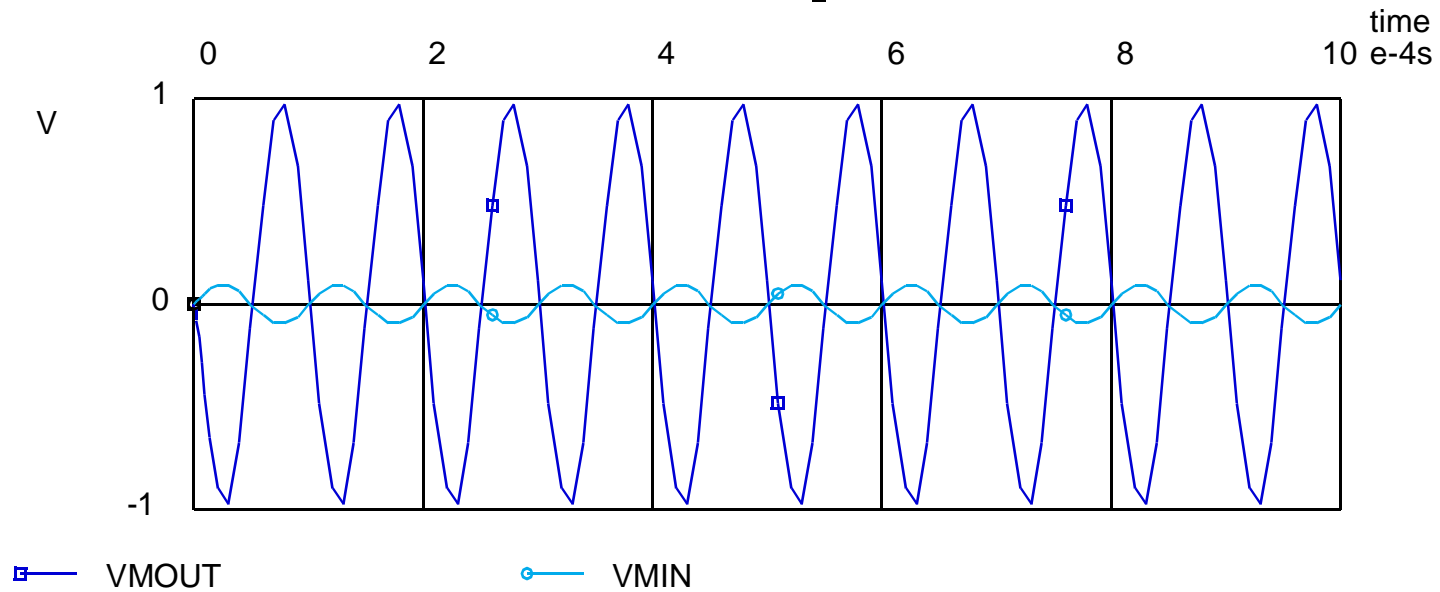
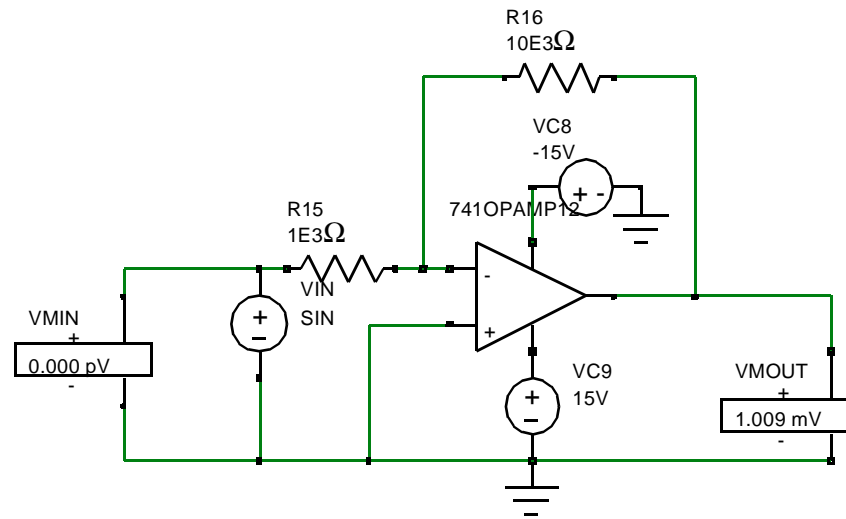
# 741 Opamp Example

- A gain of 10, or 20dB is possible at 10kHz:






# 741 Opamp Example

- But not at 100kHz:

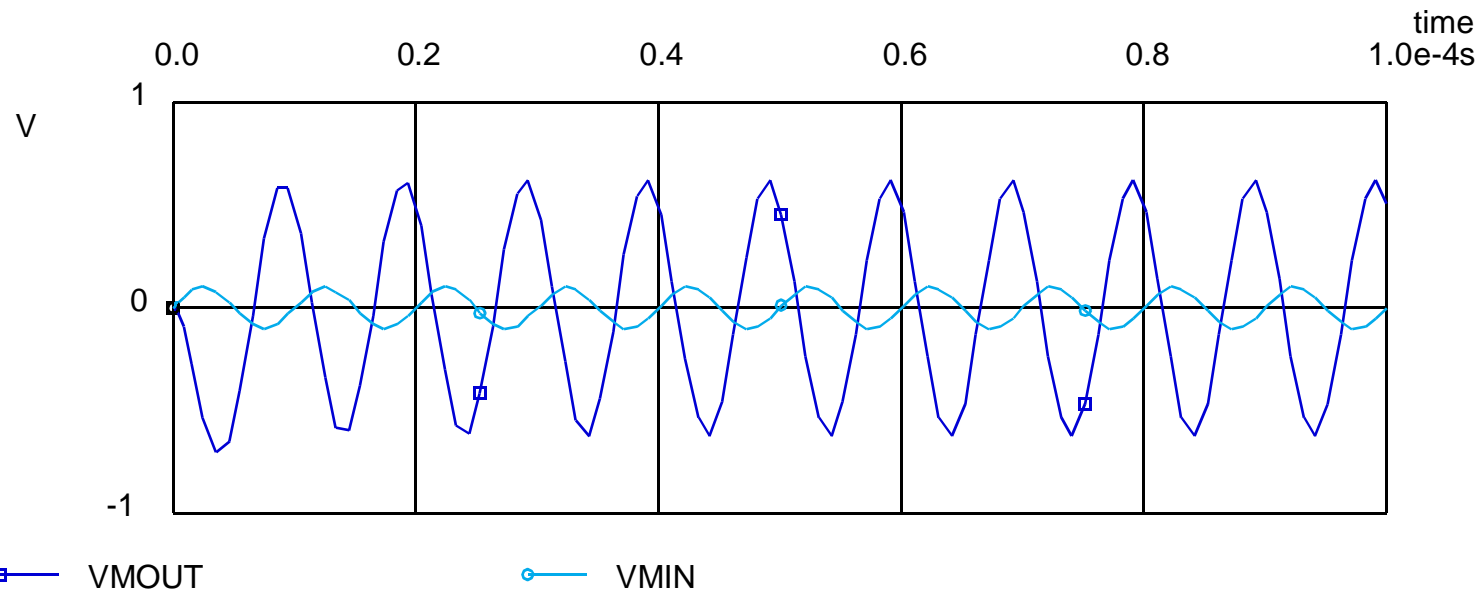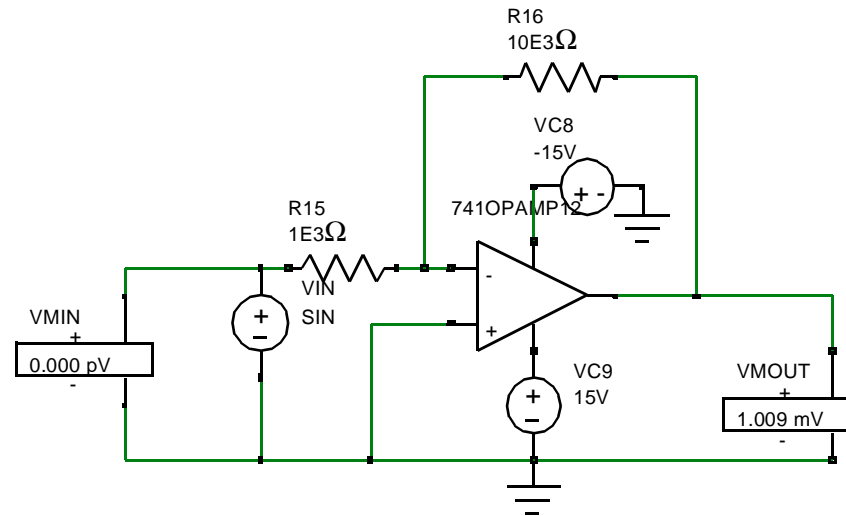
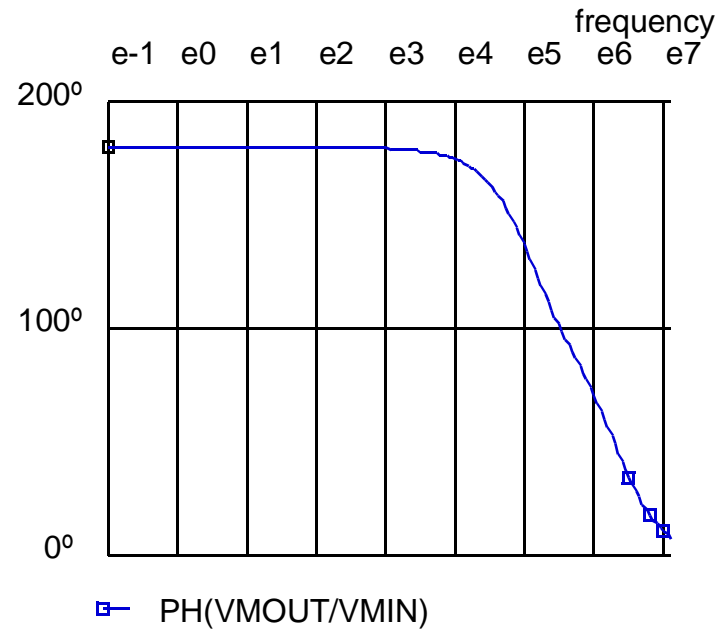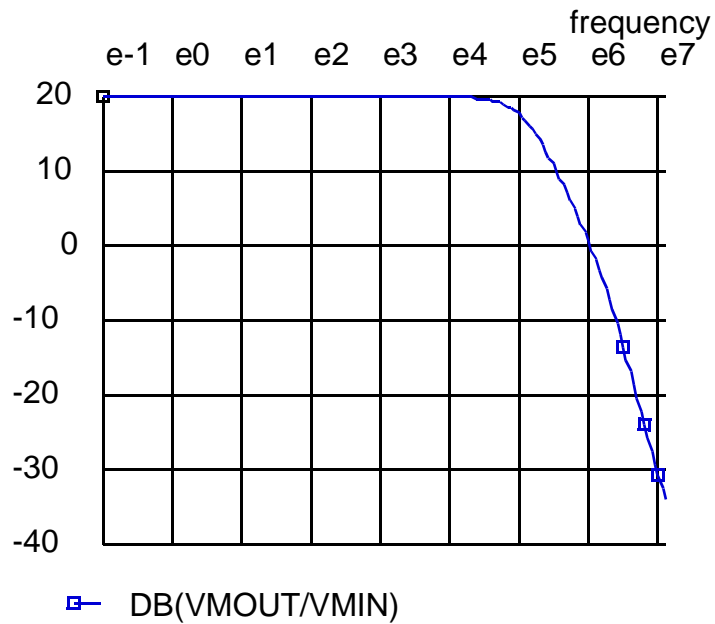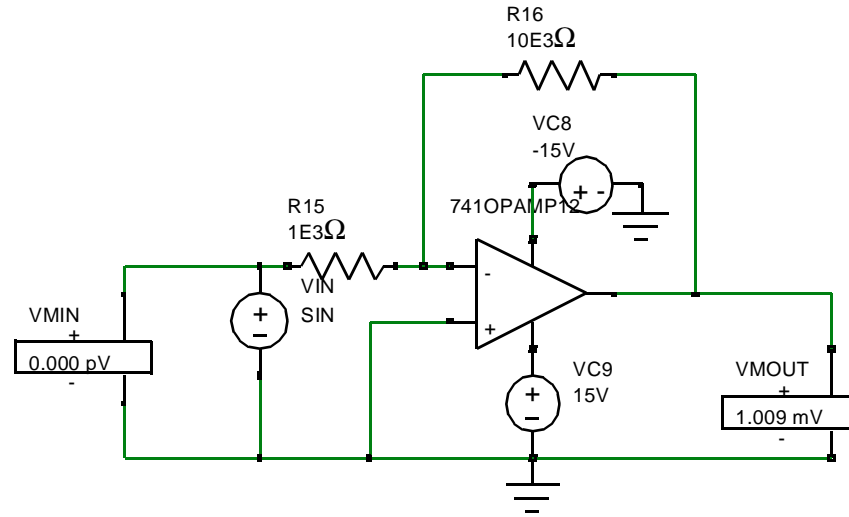
# 741 Opamp Example


- This decrease in gain is evident from a frequency domain analysis



# Gain as a Function of Frequency

- Will the closed-loop gain (with feedback) will always be less than or equal to the open loop gain as a function of frequency?

open  
loop  
gain


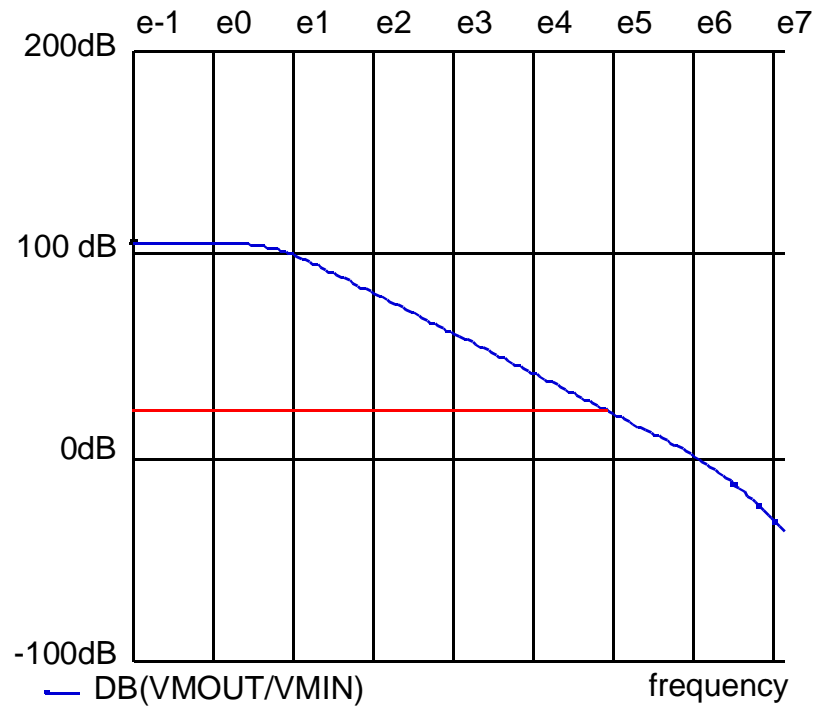




# Gain as a Function of Frequency

- We can assume that the close-loop response will follow the open loop characteristic beyond the frequency at which they intersect if the load capacitance and input terminal capacitances are small
- Why are the other capacitors a factor?



## 741 Open Loop Characteristics

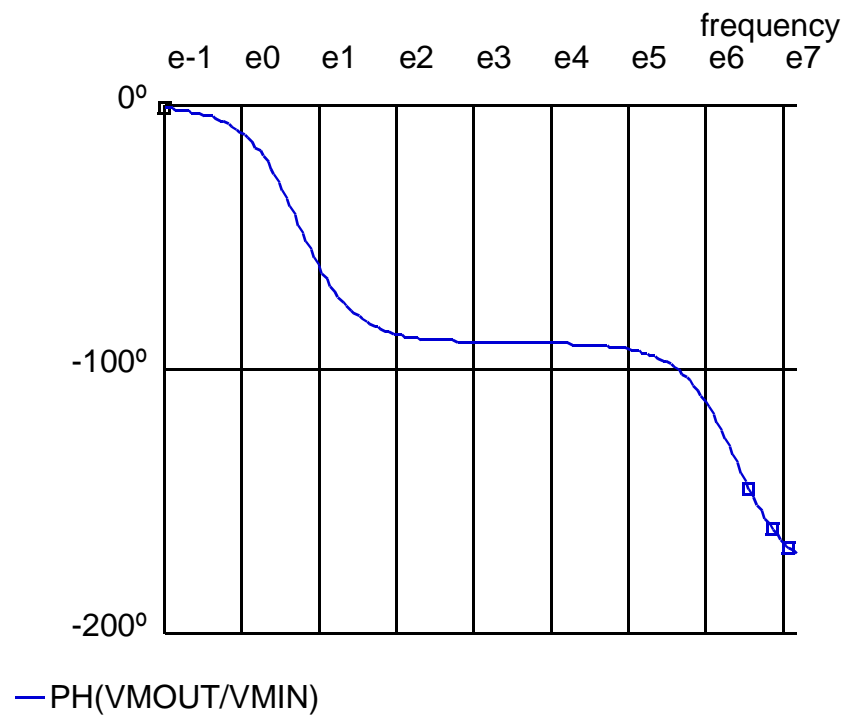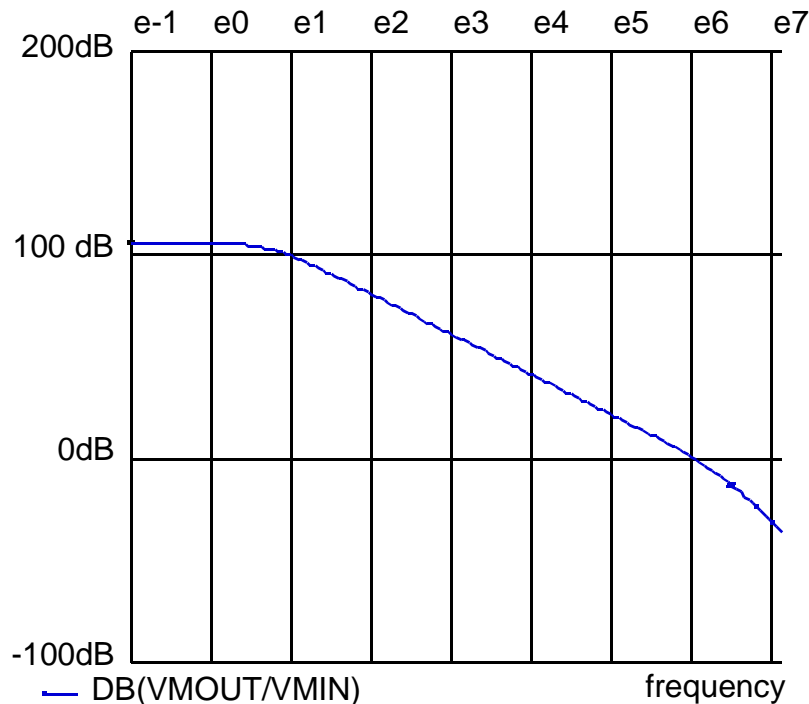

# Gain as a Function of Frequency


- It is important that the open loop characteristic has a phase shift of less than  $180^\circ$  (a change in gain of less than 40dB per decade) at the point of intersection with the closed-loop characteristic --- why?

## 741 Open Loop Characteristics

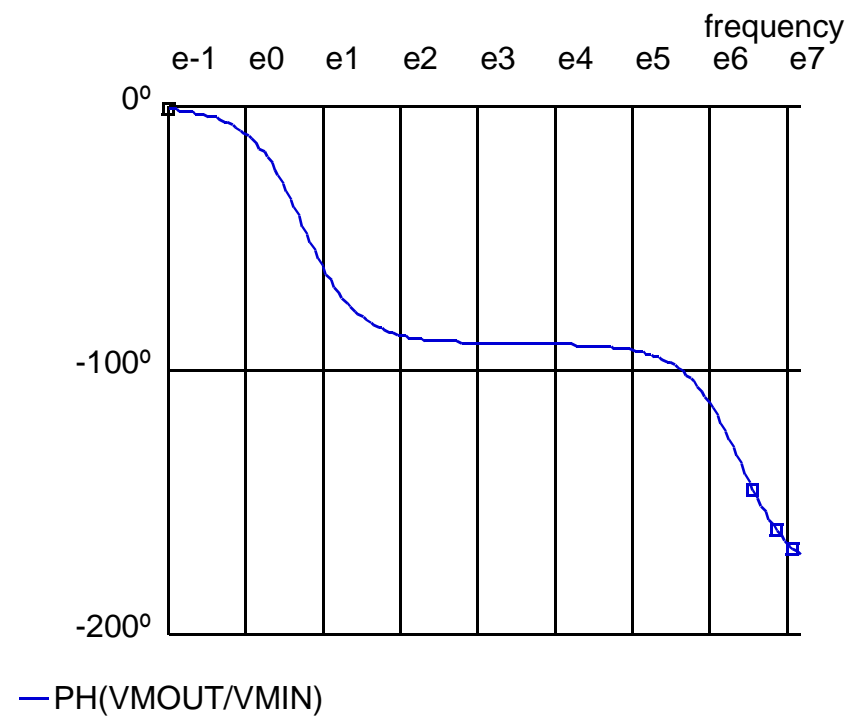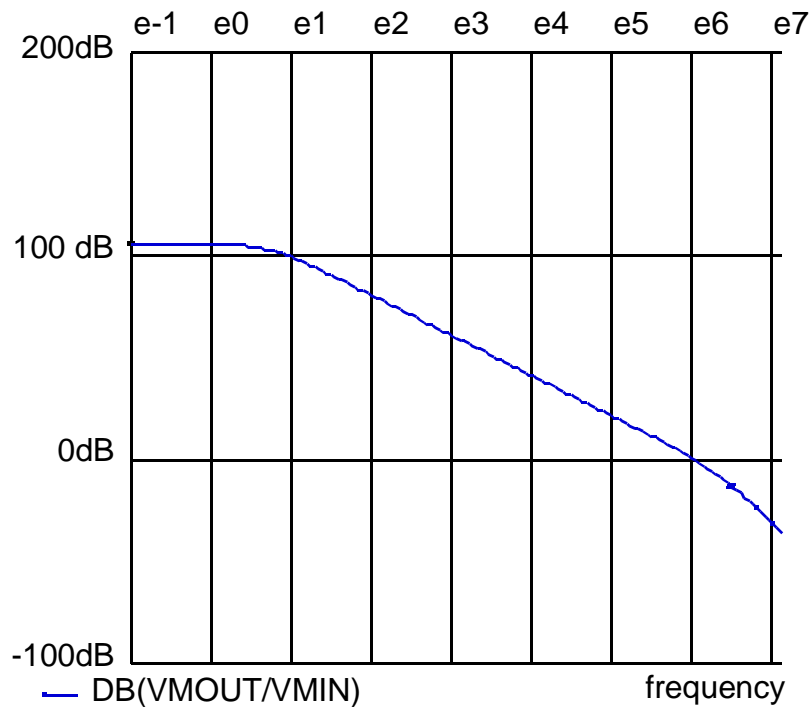

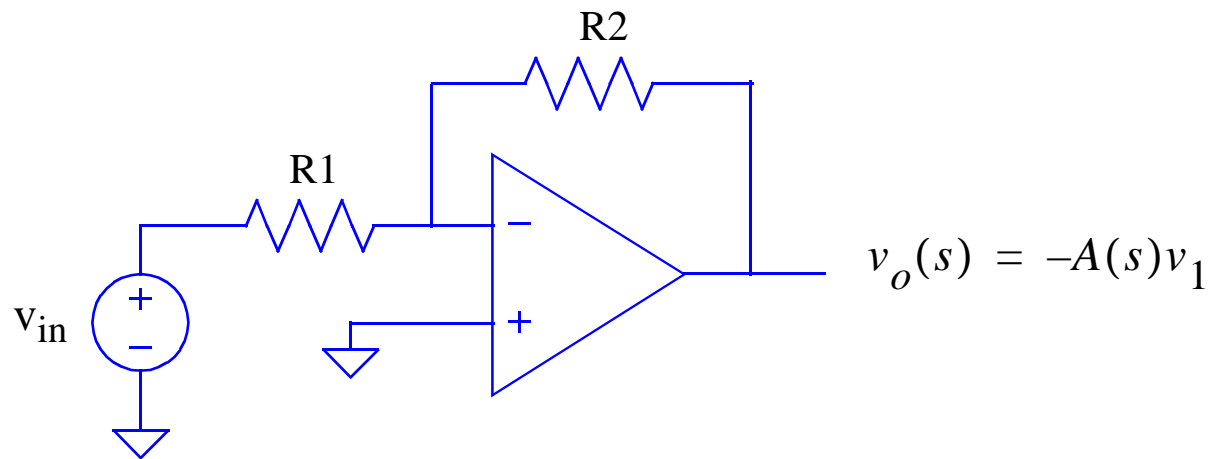
# Stability

- If the open loop gain has a phase shift of  $180^\circ$ , and we connect the opamp with negative feedback (which represents another phase shift of  $180^\circ$ ), then the total phase shift will be  $360^\circ$  which is like **positive feedback**


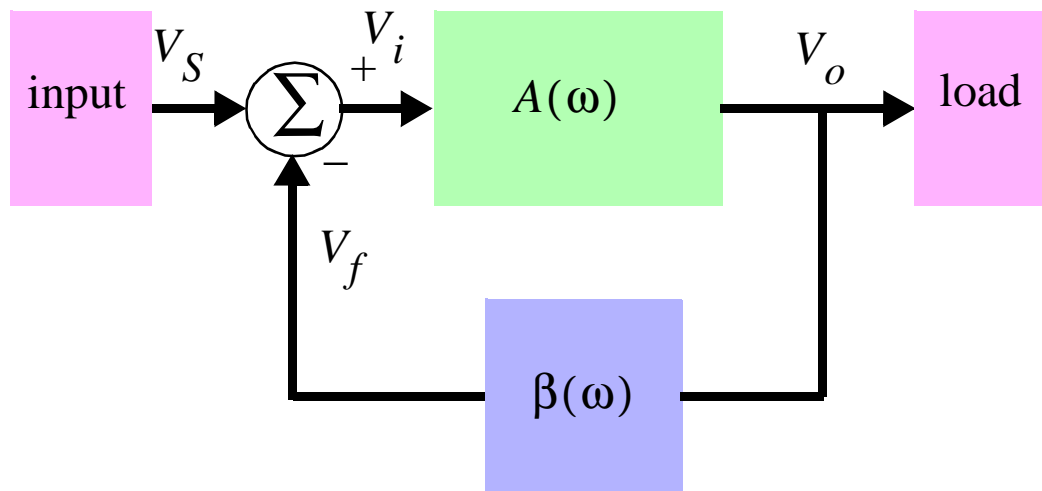
# Feedback


- The feedback can further complicate matters if it is also a function of frequency



$$A_f(\omega) = \frac{A(\omega)}{1 + \beta(\omega)A(\omega)}$$

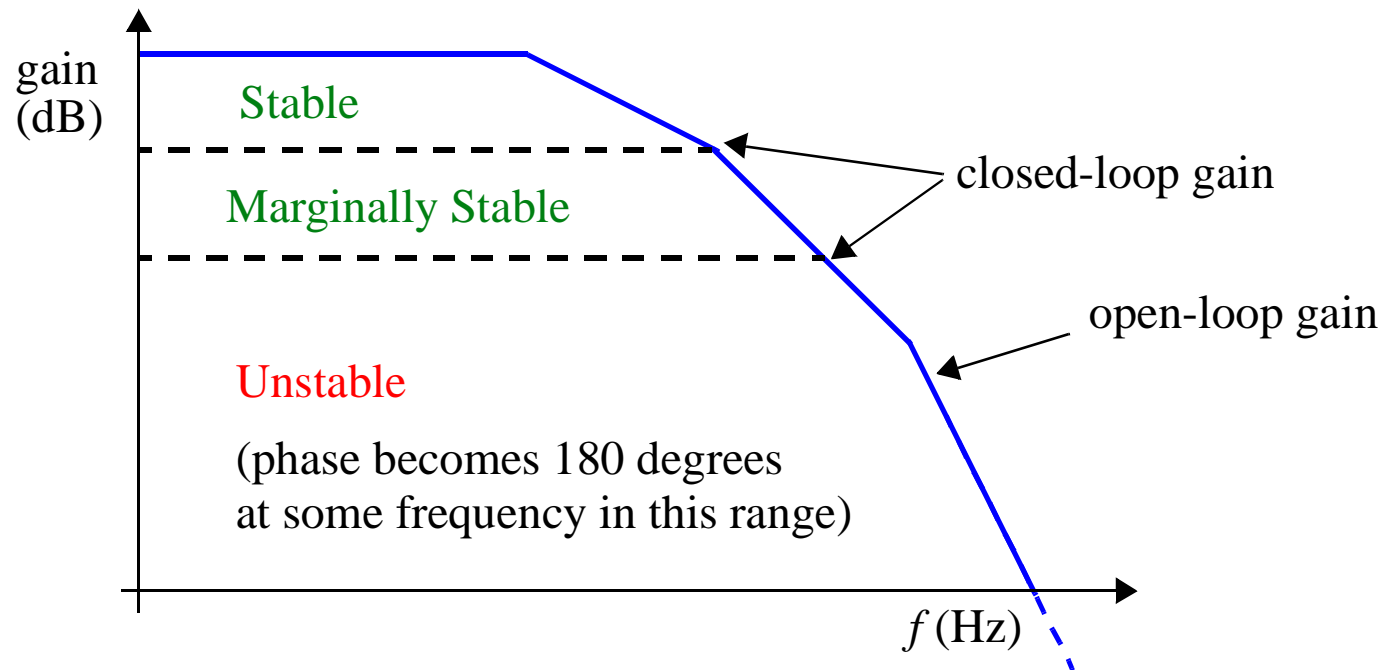
# Stability

- The circuit will be unstable with this positive feedback
- What causes the gain characteristic to exhibit these unwanted phase shifts?


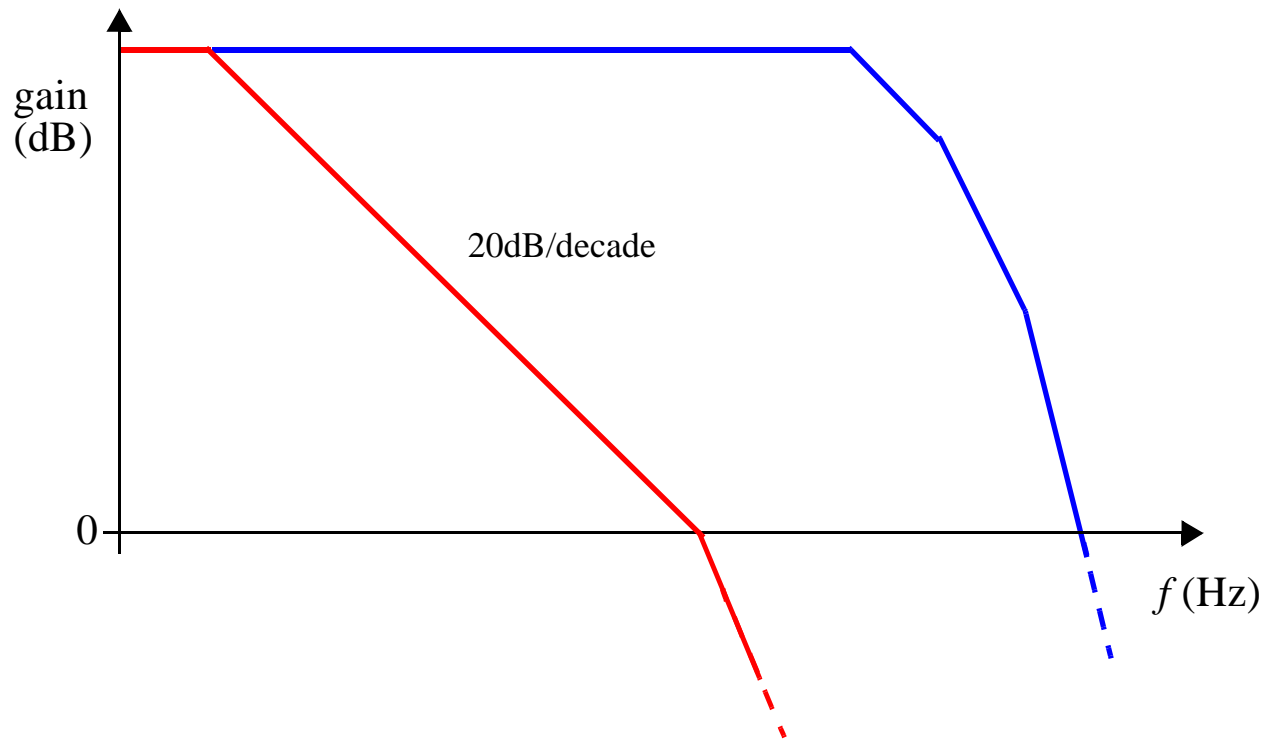
# Internal Compensation


- **Compensation capacitors** are added to purposely place a low frequency (dominant) pole so that the change in gain will be 20dB/decade up until the **unity gain frequency**
- Why isn't the phase a concern beyond this frequency?



- Sacrifices gain for stability
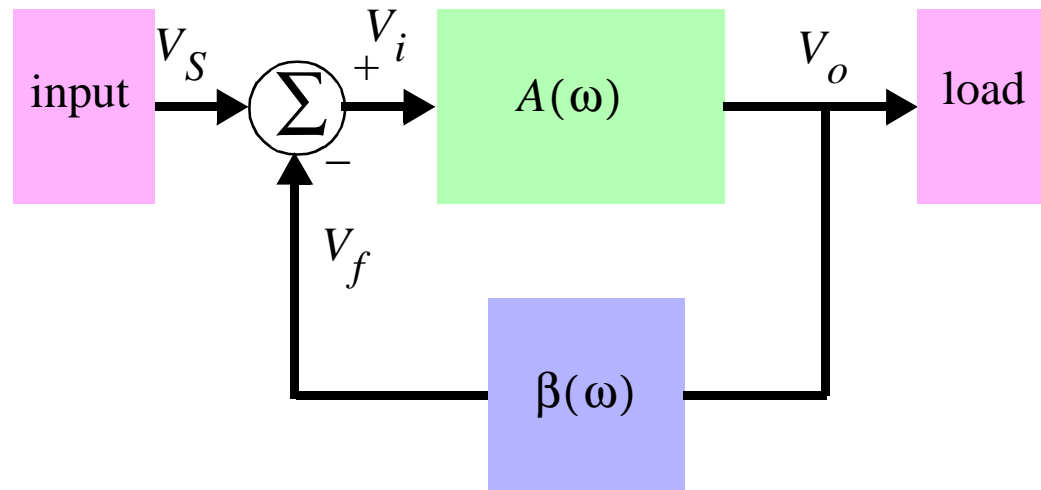
# Feedback


- Most feedback we've considered has no phase shift (resistors), so compensation will ensure stability
- However, frequency dependent feedback can pose a problem even for compensated opamps



$$A_f(\omega) = \frac{A(\omega)}{1 + \beta(\omega)A(\omega)}$$
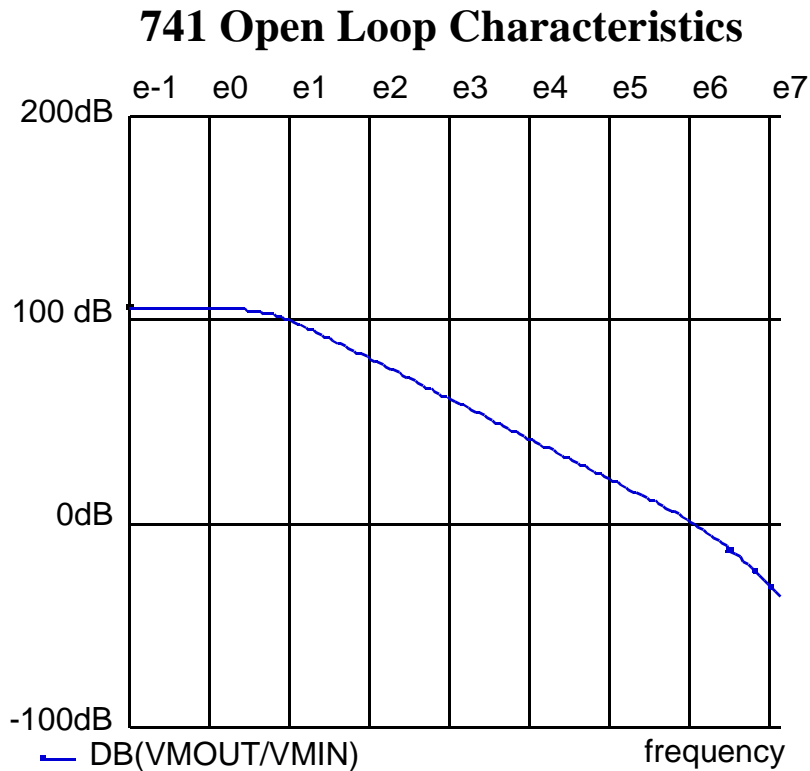
# Modeling Gain as a Function of Frequency

- With compensation, the frequency response appears like a STC




$$A(s) = \frac{A_o}{1 + s/\omega_b}$$



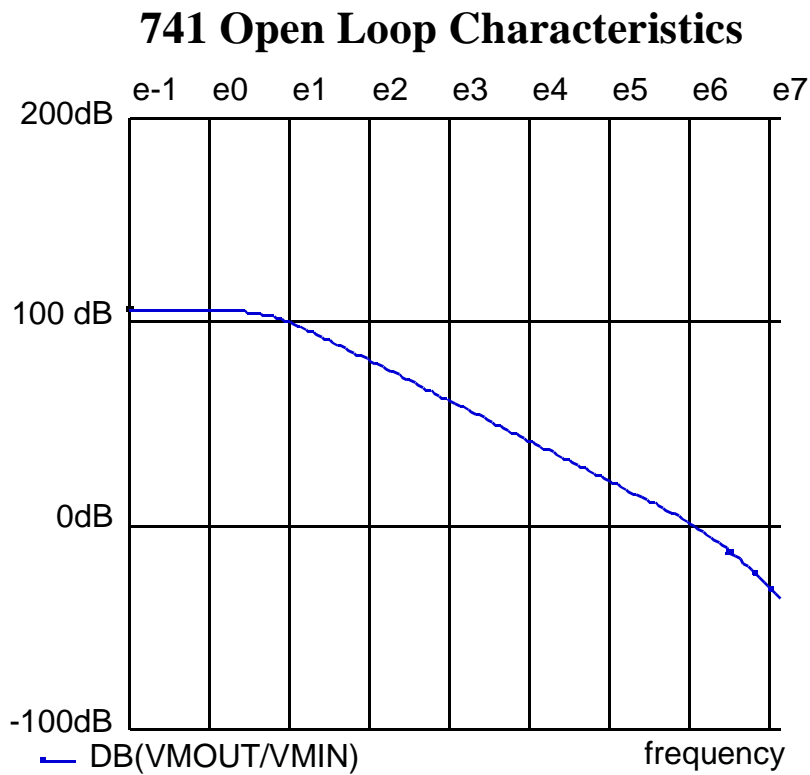
# Unity Gain Bandwidth

- We can easily solve for the frequency,  $\omega_t$ , at which the gain is 0dB


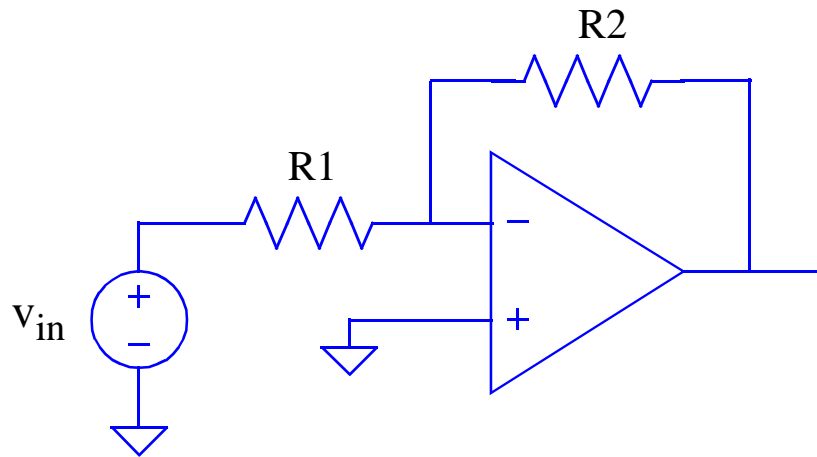
## Frequency Dependence of Gain

- Using these expressions for gain as a function of frequency we can approximate the inverting amplifier circuit gain as a function of frequency



$$\frac{V_o}{V_i} = \frac{-\frac{R_2}{R_1}}{1 + \frac{R_2}{A(s)}}$$

$$A(s) = \frac{A_o}{1 + s/\omega_b}$$

$$\frac{V_o}{V_i} = \frac{-\frac{R_2}{R_1}A_o}{A_o + \left(1 + \frac{R_2}{R_1}\right) + \frac{s}{\omega_b}\left(1 + \frac{R_2}{R_1}\right)}$$

## Frequency Dependence of Gain

- We can assume that the closed-loop gain is much smaller than the **dc open loop gain**


$$\frac{V_o}{V_i} = \frac{-\frac{R_2}{R_1}A_o}{A_o + \left(1 + \frac{R_2}{R_1}\right) + \frac{s}{\omega_b}\left(1 + \frac{R_2}{R_1}\right)}$$

# Frequency Dependence of Gain

- Does this result seem correct?
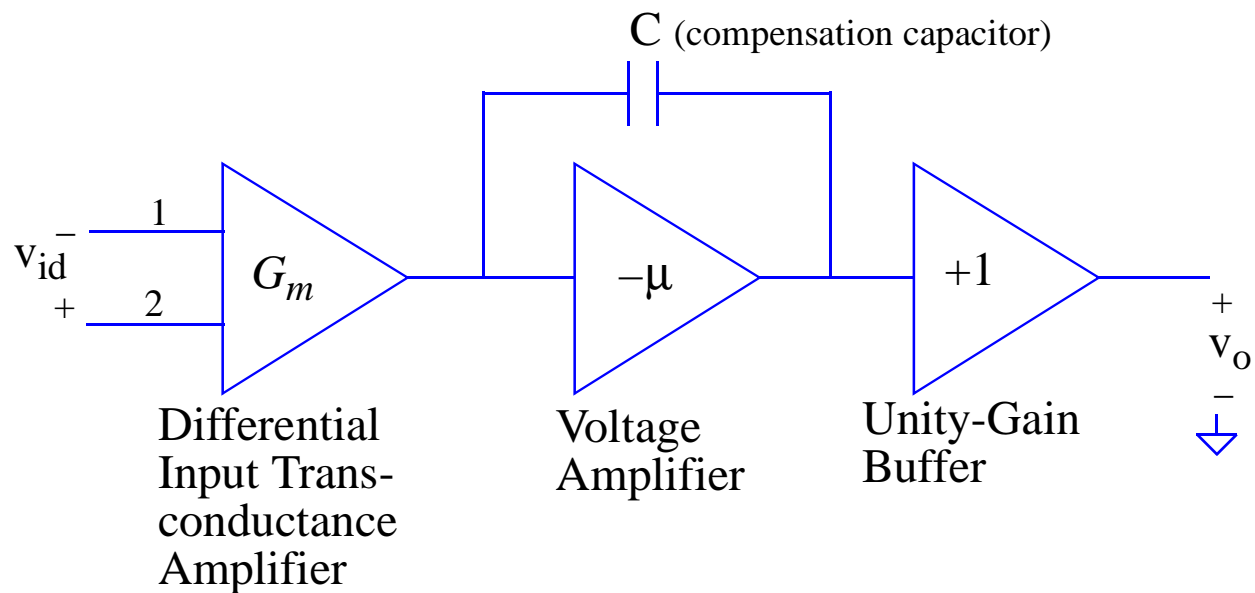
# Opamp Macromodels


- We can model the frequency dependence of the gain using a macromodel for the opamp
- Internal structure of an opamp:




- We'll build all of these transistor level components later in the course
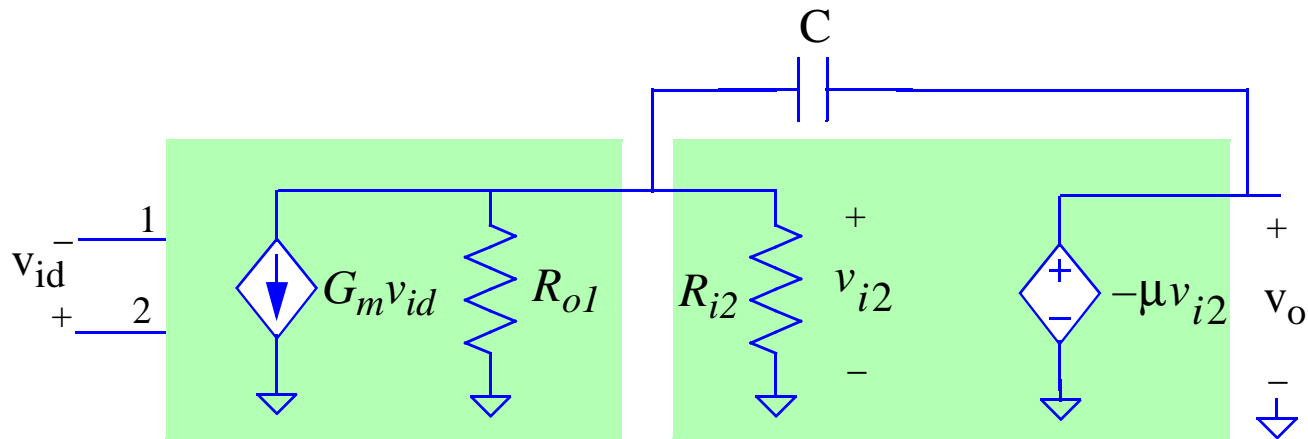
# Opamp Macromodels

- We can model the first two stages (the last is trivial) using controlled sources, R's and C's:




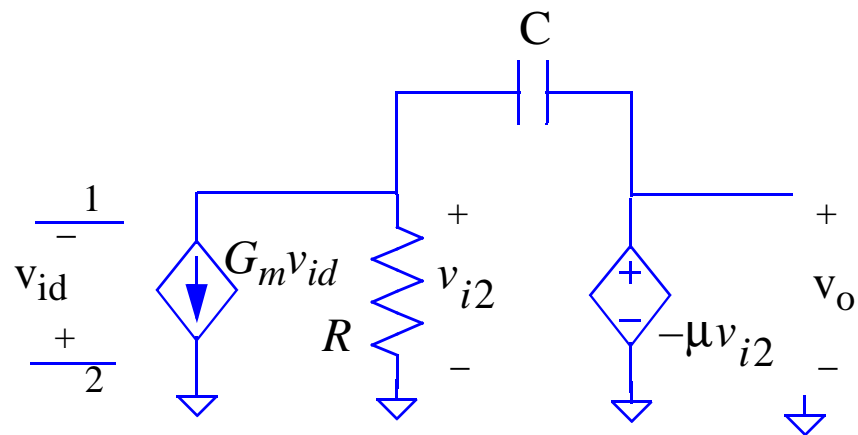- Which we can simplify by combining the parallel R's



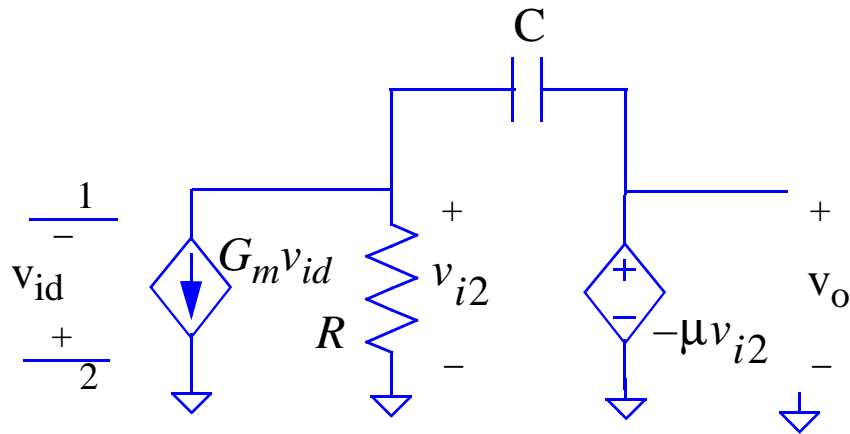
# Opamp Macromodel

- This circuit has the same STC form as a compensated opamp



# Opamp Macromodel

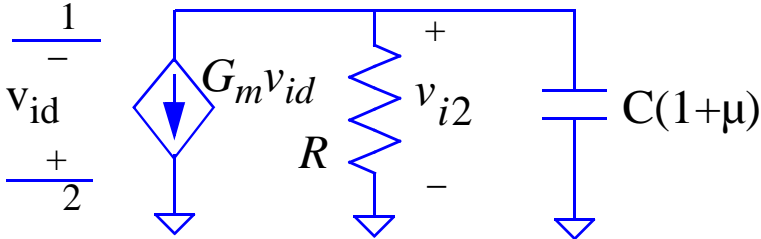




# Opamp Macromodel

- The parameters for a 741 macromodel are:

$$G_m = 0.19 \frac{mA}{volt} \quad \mu = 529 \quad R_{i2} = 4M\Omega \quad R_{o1} = 6.7M\Omega \quad C = 30pF$$

## 741 Open Loop Characteristics

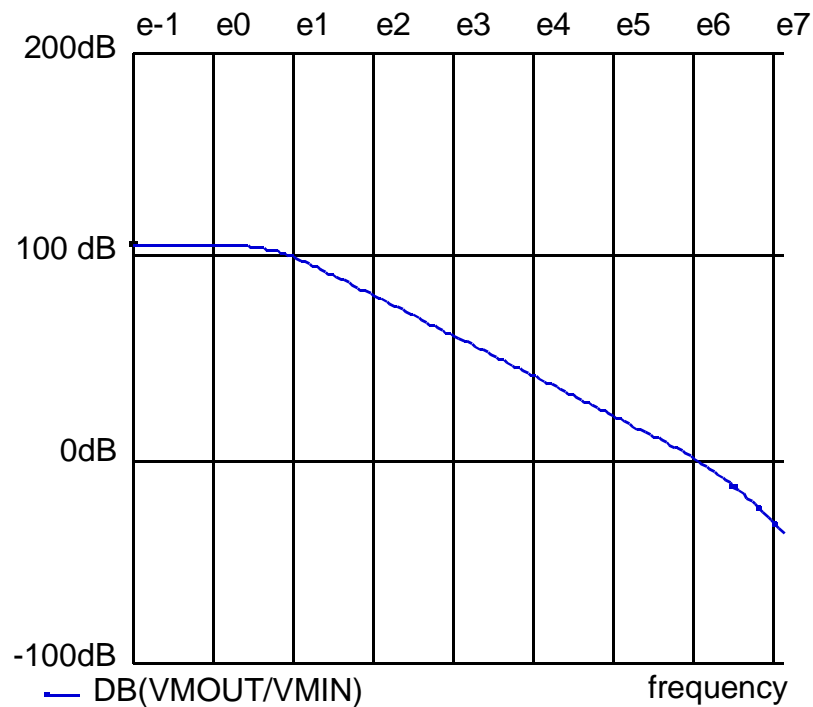

## Macromodel

