


# Arithmetic Building Blocks

## Low-Power Design



Lecture 12  
18-322 Fall 2002


Textbook: [Chapter 7, Section 4.4]

## Outline




- Arithmetic building blocks
  - ☒ Adders
  - ☒ Multipliers
  
- Low-power design
  - ☒ Reducing power consumption
  - ☒ Data-path/Control circuitry

# A Generic Digital Processor

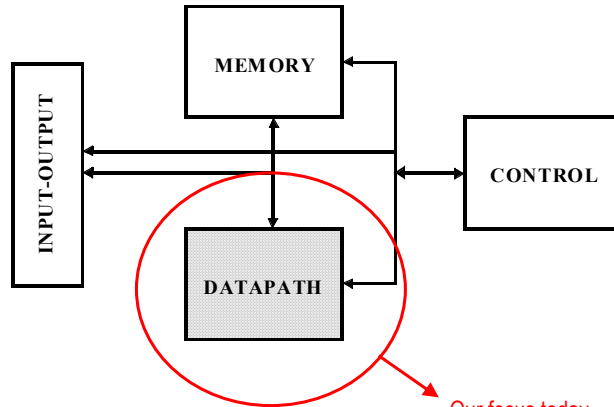

Our focus today.  
Also, main emphasis in the project!


# The Binary Adder

 


$$\begin{aligned} S &= A \oplus B \oplus C_i \\ &= \overline{A}\overline{B}C_i + \overline{A}B\overline{C}_i + A\overline{B}\overline{C}_i + ABC_i \\ C_o &= AB + BC_i + AC_i \end{aligned}$$

# Static CMOS Full Adder:

Is this a great implementation?

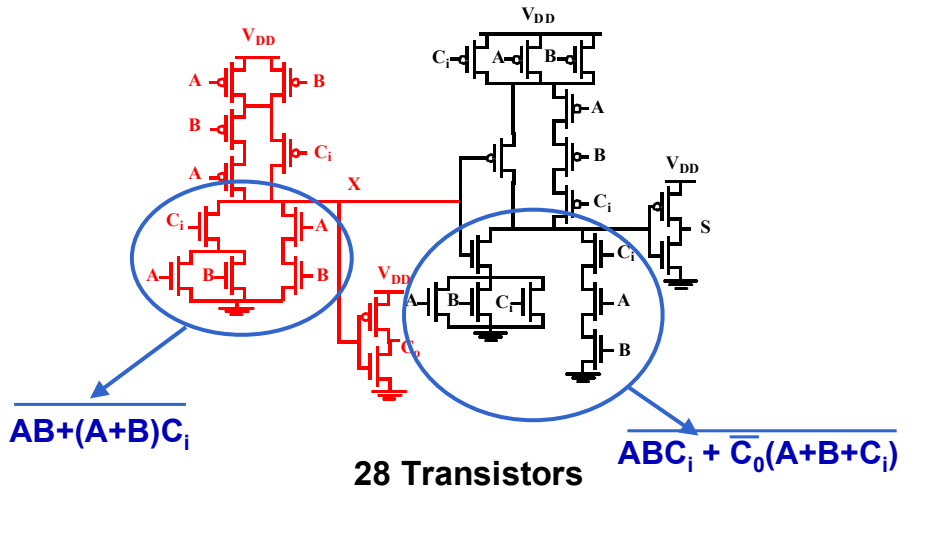

# The Ripple-Carry Adder

 


Worst case delay linear with the number of bits

$$t_d = O(N)$$

$$t_{\text{adder}} \approx (N-1)t_{\text{carry}} + t_{\text{sum}}$$

Goal: Make the fastest possible carry path circuit


# Inversion Property

 

$$\bar{S}(A, B, C_i) = S(\bar{A}, \bar{B}, \bar{C}_i)$$

$$\bar{C}_o(A, B, C_i) = C_o(\bar{A}, \bar{B}, \bar{C}_i)$$
 
# Minimize Critical Path by Reducing the Number of Inverting Stages



Exploit Inversion Property

Note: Needs 2 different types of cells

# Express Sum and Carry using P, G, D

Define 3 new variable which ONLY depend on A, B

**Generate (G) = AB**

**Propagate (P) = A ⊕ B**


**Delete =  $\bar{A}\bar{B}$**

$$C_o(G, P) = G + PC_i$$


$$S(G, P) = P \oplus C_i$$

Can also derive expressions for S and  $C_o$  based on D and P

# A better structure: the Mirror Adder

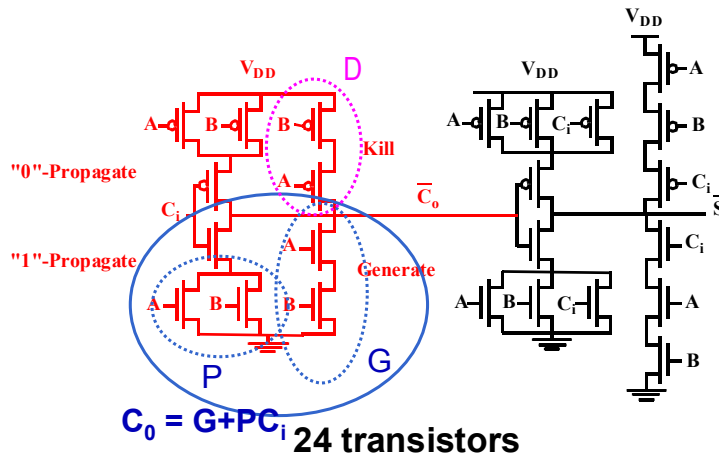


# Carry-Bypass Adder

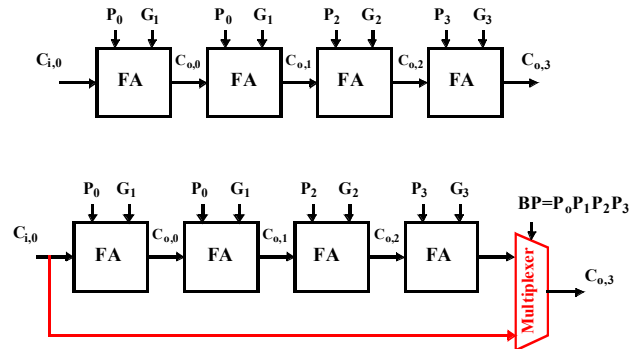


Idea: If ( $P_0$  and  $P_1$  and  $P_2$  and  $P_3 = 1$ ) then  $C_{03} = C_0$ , else "kill" or "generate".

# Carry-Bypass Adder (cont.)

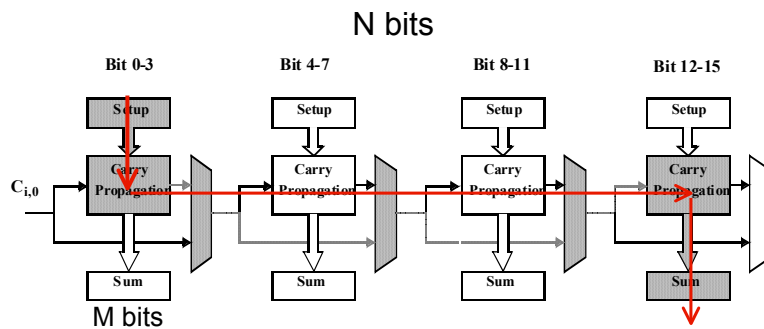


**Note:** the topological path worst-case delay is much higher than the true critical path!


# Carry Ripple vs. Carry Bypass

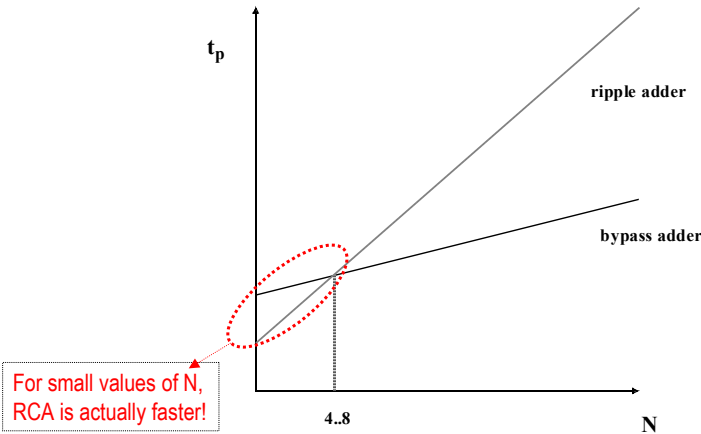


# Carry-Select Adder

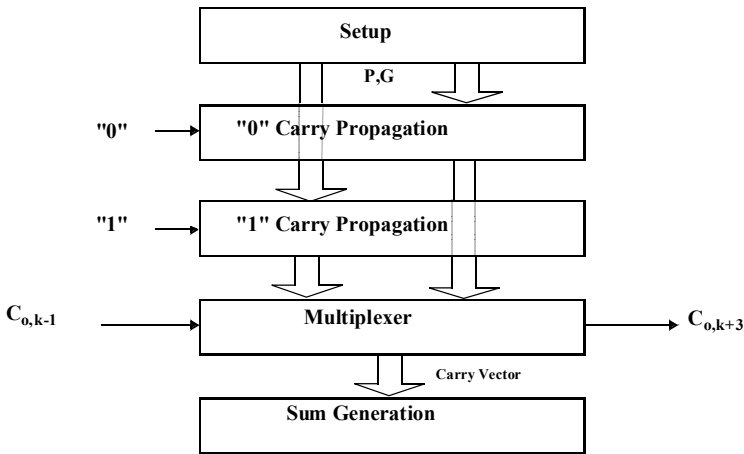

# Carry Select Adder: Critical Path

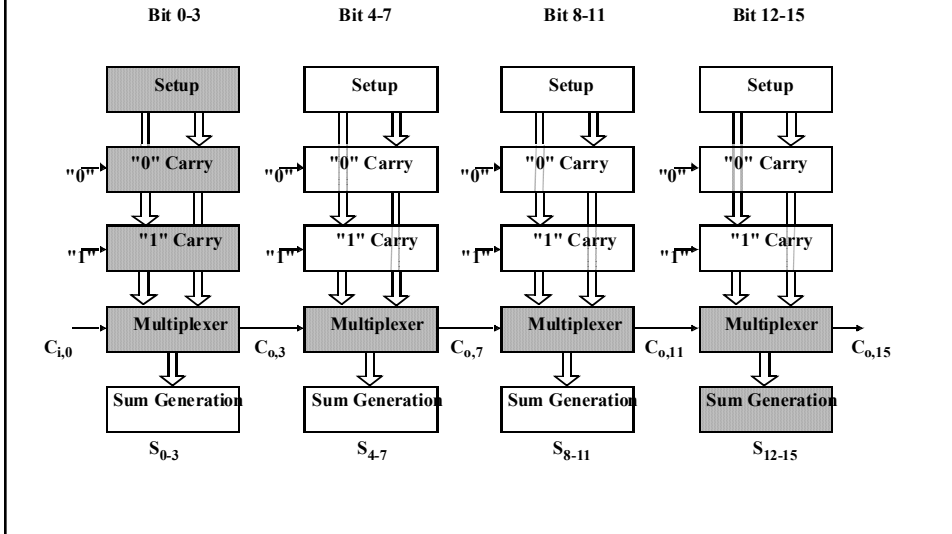


# Adder Delays - Comparison

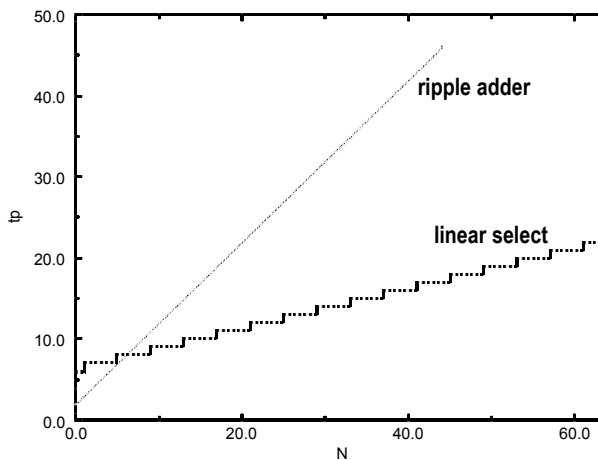



# Look Ahead - Basic Idea


 


$$C_{0,k} = G_k + P_k C_{0,k-1}$$

$$C_{0,k} = G_k + P_k (G_{k-1} + P_{k-1} (\dots + P_1 (G_0 + P_0 C_{i,0})))$$

The look ahead structure is useful for small values of  $N$  ( $N < 4$ )

# Design as a Trade-Off

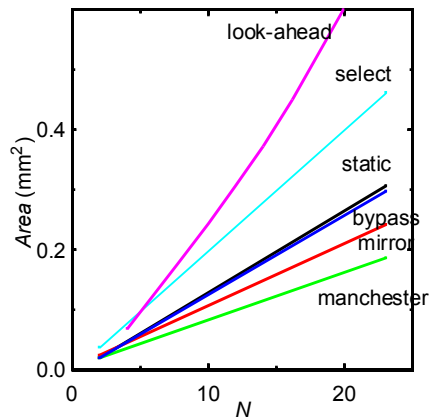 

# The Binary Multiplication


- Multiplications are *expensive* and *slow* operations

- Performance is often dominated by the speed at which multiplications can be executed

$$\begin{array}{r}
 101010 \text{ (multiplicand)} \\
 \times 1011 \text{ (multiplier)} \\
 \hline
 101010 \\
 101010 \\
 000000 \\
 + 101010 \\
 \hline
 111001110
 \end{array}$$


partial product  
(this corresponds to  
a AND operation)

# The Array Multiplier

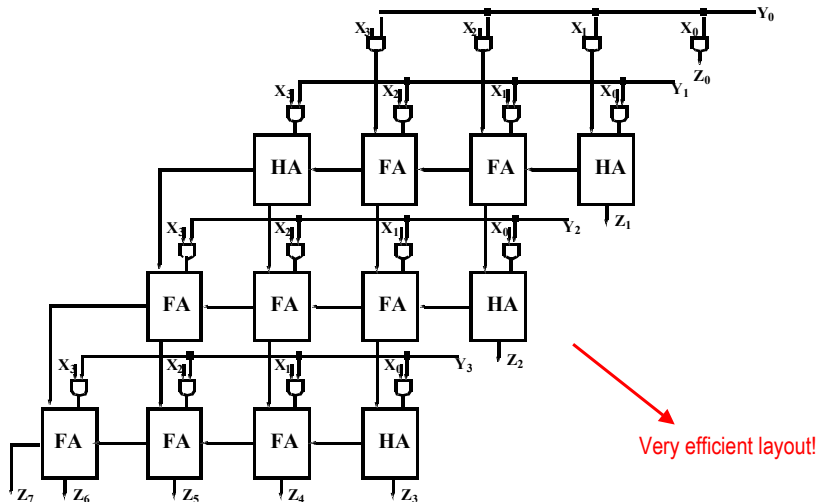

# The MxN Array Multiplier


## — Critical Path

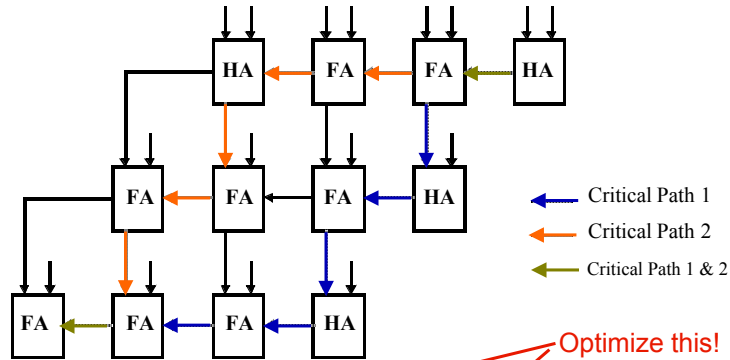

$$t_{mult} \approx [(M-1) + (N-2)]t_{carry} + (N-1)t_{sum} + (N-1)t_{and}$$

Optimization is very difficult since there exists several critical paths!


# Carry-Save Multiplier

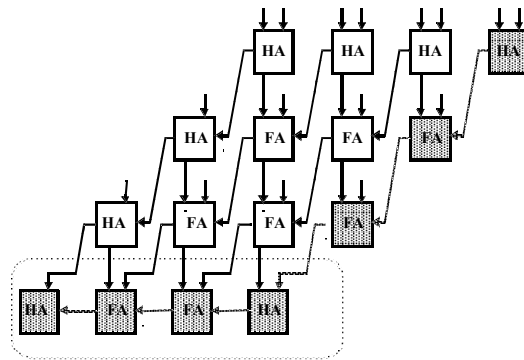

$$t_{mult} = (N-1)t_{carry} + (N-1)t_{and} + t_{merge}$$

Optimization becomes easier (unique critical path)!

## Wallace-Tree Multiplier

 

## Multipliers —Summary

- Optimization Goals Different compared to the Binary Adder
- Once Again: **Identify the Critical Path**
- Other possible techniques
  - Logarithmic versus Linear (Wallace Tree Multiplier)
  - Data encoding (Booth)
  - Pipelining

# Outline


- ✓ Arithmetic building blocks
  - ☒ Adders
  - ☒ Multipliers
- Low-power design
  - ☒ Reducing power consumption
  - ☒ Data-path/Control circuitry

## How about POWER?


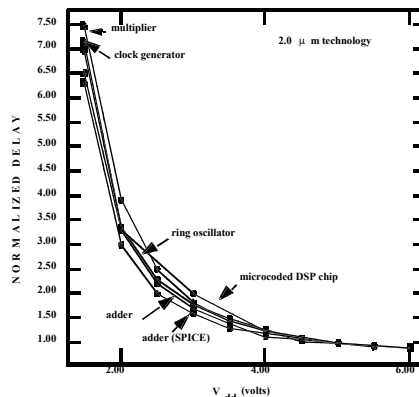
### Ways to reducing power consumption

- Load capacitance ( $C_L$ )
  - ☒ Roughly proportional to the chip area
- Switching activity (avg. number of transitions/cycle)
  - ☒ Very data dependent
  - ☒ A big portion due to glitches (real-delay)
- Clock frequency ( $f$ )
  - ☒ Lowering only  $f$  decreases average power, but total energy is the same and throughput is worse

- Voltage supply ( $V_{DD}$ )
  - Biggest impact



## Using parallelism (1)

 
 


Area = 636 x 833  $\mu^2$

$$P_{\text{ref}} = C_{\text{ref}} V_{\text{DD}}^2 f_{\text{ref}}$$

Assume:  $t_p = 25\text{ns}$  (worst-case, *all* modules) at  $V_{\text{DD}} = 5\text{V}$


## Using parallelism (2)

  

Area = 1476 x 1219  $\mu^2$


- $C_{\text{par}} = 2.15C$  (extra-routing needed)
- $f_{\text{par}} = f/2$  ( $t_{p,\text{new}} = \frac{1}{2}(50)\text{ns} \Rightarrow V_{\text{DD}} \sim 2.9\text{V}; V_{\text{DD,par}} = 0.58 V_{\text{DD}}$ )
- $P_{\text{par}} = C_{\text{par}} V_{\text{DD}}^2 f_{\text{par}} = 0.36 P_{\text{ref}}$

## Using pipelining

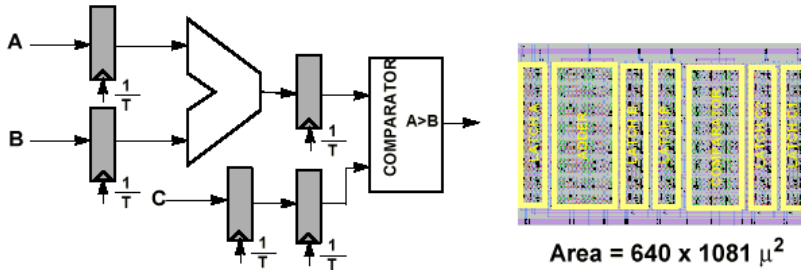

- $C_{\text{pipe}} = 1.15C$
- Delay decreases 2 times ( $V_{DD,\text{pipe}} = 0.58 V_{DD}$ )
- $P_{\text{pipe}} = 0.39 P$

## Chain vs. balanced design

 

### ■ Question for you:

☒ Which of the two designs is more energy efficient?

☒ Assume:


- Zero-delay model
- All inputs have a signal probability of 0.5

☒ Hint: Calculate  $p_{0 \rightarrow 1}$  for W, X and F

## Low energy gates – transistor sizing

- Use the *smallest transistors* that satisfy the delay constraints
  - ☒ Increasing transistor size improves the speed but it also increases power dissipation (since the load capacitances increases)
    - ☒ Slack time - difference between required time and arrival time of a signal at a gate output
      - Positive slack - size down
      - Negative slack - size up
- Make gates that toggle more frequently smaller
- Slope engineering to reduce short circuit currents

 
## Low energy gate netlists – pin ordering



- Better to postpone the introduction of signals with a high transition rate (signals with signal probability close to 0.5)




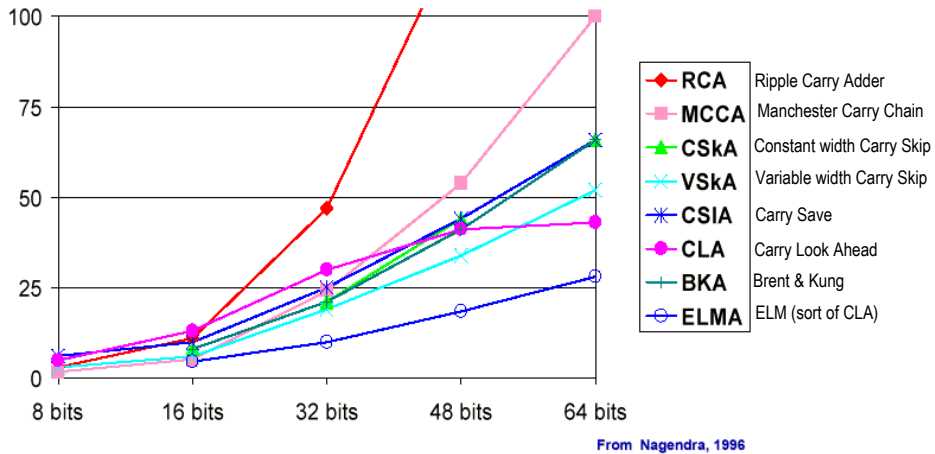
## Power×Delay trade-off for various adders



Use a design that is fast enough and consumes the least power!

## Control circuits

  

- State encoding has a **big impact** on the power efficiency
- **Energy driven** -> try to minimize number of bit transitions in the state register
  - ☒ Fewer transitions in state register
  - ☒ Fewer transitions propagated to combinational logic

# Bus encoding

- Reduces number of bit toggles on the bus
- Different flavors
  - ☒ Bus-invert coding
    - ☒ Uses an extra bus line *invert*:
      - if the number of transitions is  $< K/2$ , invert = 0 and the symbol is transmitted as is
      - if the number of transitions is  $> K/2$ , invert = 1 and the symbol is transmitted in a complemented form
  - ☒ Low-weight coding
    - ☒ Uses *transition* signaling instead of *level* signaling



# Bus invert coding

