

18-322


Lecture 19


CMOS Gates: Sizing and Delay

- Load Capacitance
- Fall and rise time analysis.
- Analytical models.
- Propagation delay analysis.
- Fall and rise time formulas
- Transistor sizing
- Multi-input gates




Text: Sections 3.3.3 and 4.2

CMOS Inverter's Load

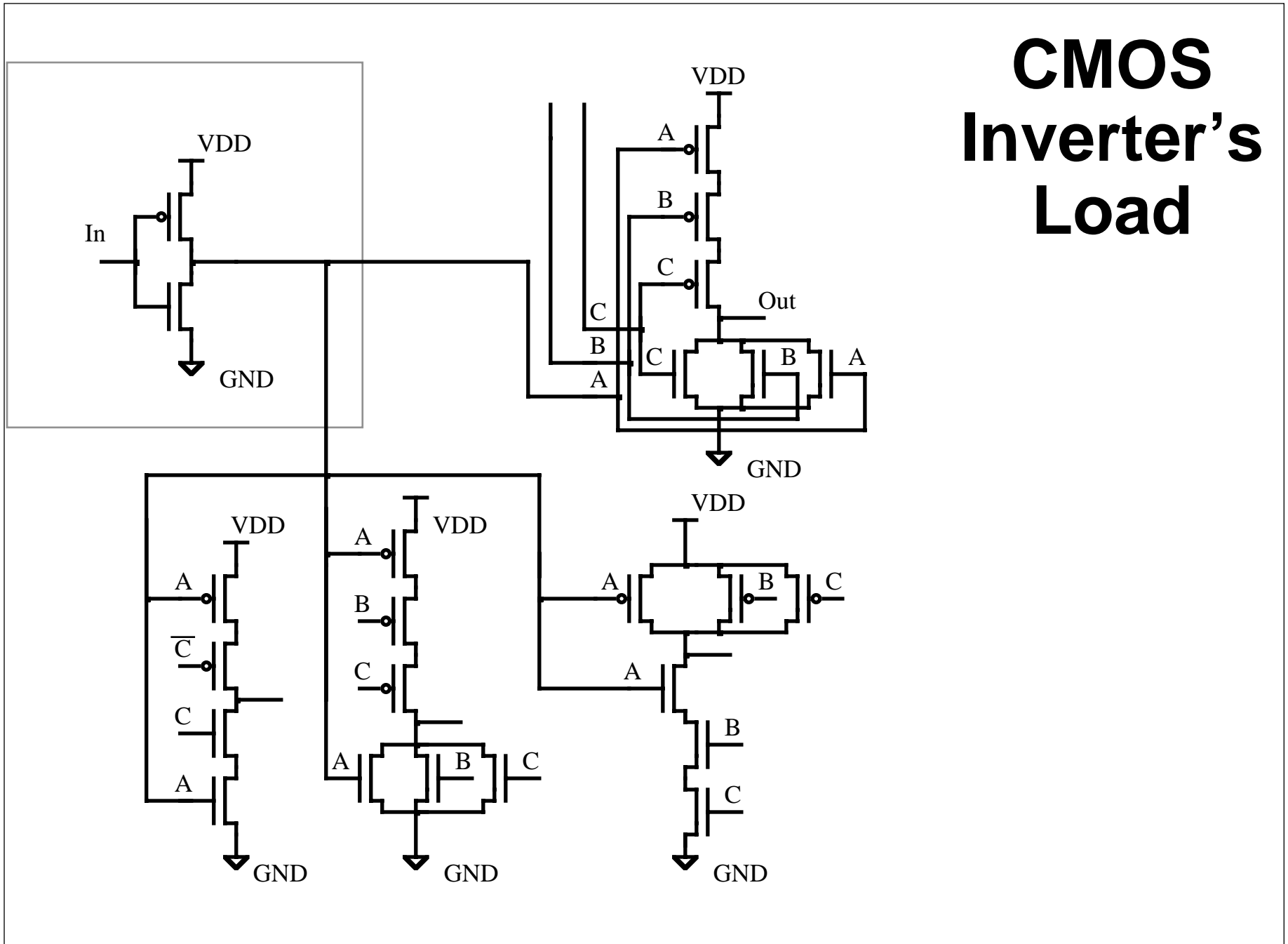

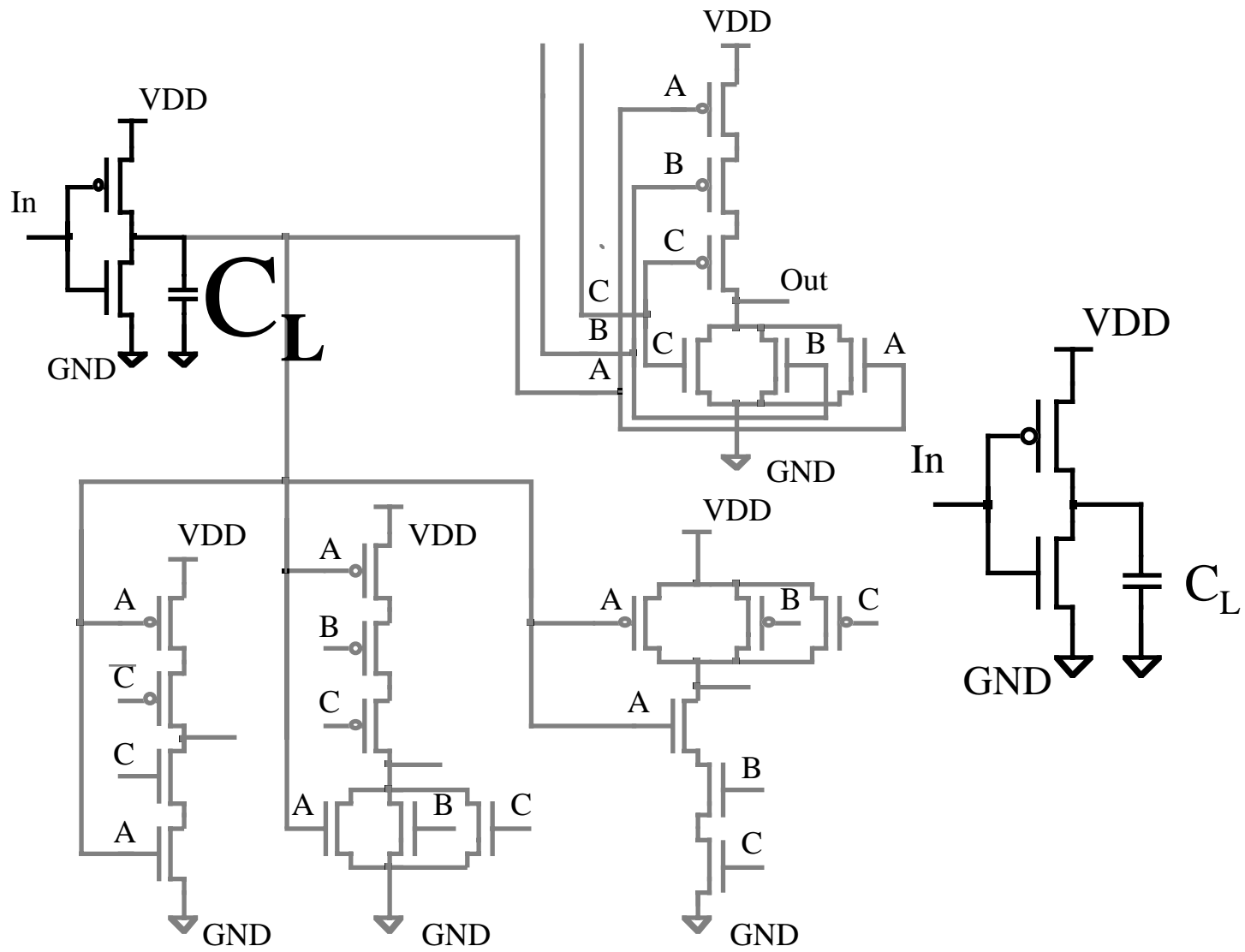

CMOS Inverter - Switching

   

Device equations (NMOS)

Non-Sat:

$$I_{ds} = \beta_n \left[(V_{gs} - V_{tn}) V_{ds} - \frac{1}{2} V_{ds}^2 \right]$$


Saturation:

$$I_{ds} = \frac{\beta_n}{2} (V_{gs} - V_{tn})^2$$



where

$$\beta_n = \mu \frac{\epsilon}{t_{ox}} \left(\frac{W}{L} \right)_n$$


Inverter Switching

 


NMOS trajectory: V_{out} falling.

 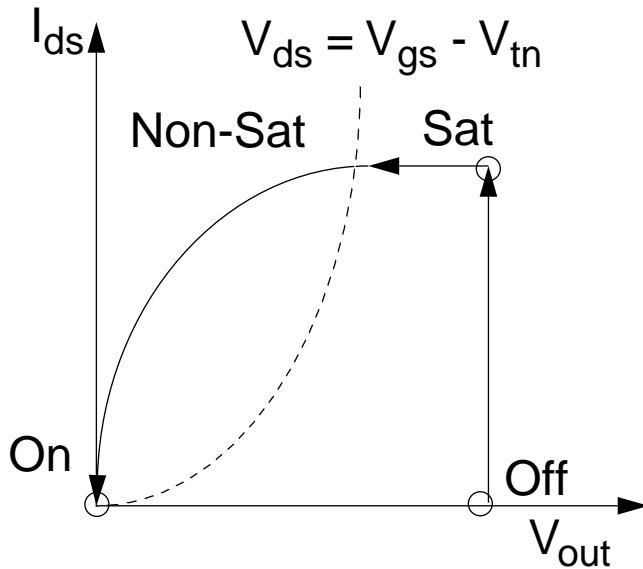


CMOS Inverter - Switching

 

Output Fall Time Analysis

 


 
NMOS saturated: $V_{out} \geq V_{DD} - V_{tn}$




NMOS non-saturated: $0 < V_{out} \leq V_{DD} - V_{tn}$

$$t_f = k \frac{C_L}{\beta_n V_{DD}}$$


CMOS Inverter - Switching

  

Output Rise Time Analysis

 

PMOS saturated: $V_{out} \leq |V_{tp}|$

 

PMOS non-saturated: $|V_{tp}| < V_{out} < V_{DD}$

$$t_r = k \frac{C_L}{\beta_p V_{DD}}$$

Inverter Rise/Fall Time Equalization

- Fall, Rise times:


$$\left(t_f = k \frac{C_L}{k_n \left(\frac{W}{L} \right)_n V_{DD}} \right), \left(t_r = k \frac{C_L}{k_p \left(\frac{W}{L} \right)_p V_{DD}} \right)$$

- To equalize rise, fall times:


$$(\mu_n = 2\mu_p) \Rightarrow \left(\left(\frac{W}{L} \right)_p \approx 2 \left(\frac{W}{L} \right)_n \right)$$

Propagation Delays

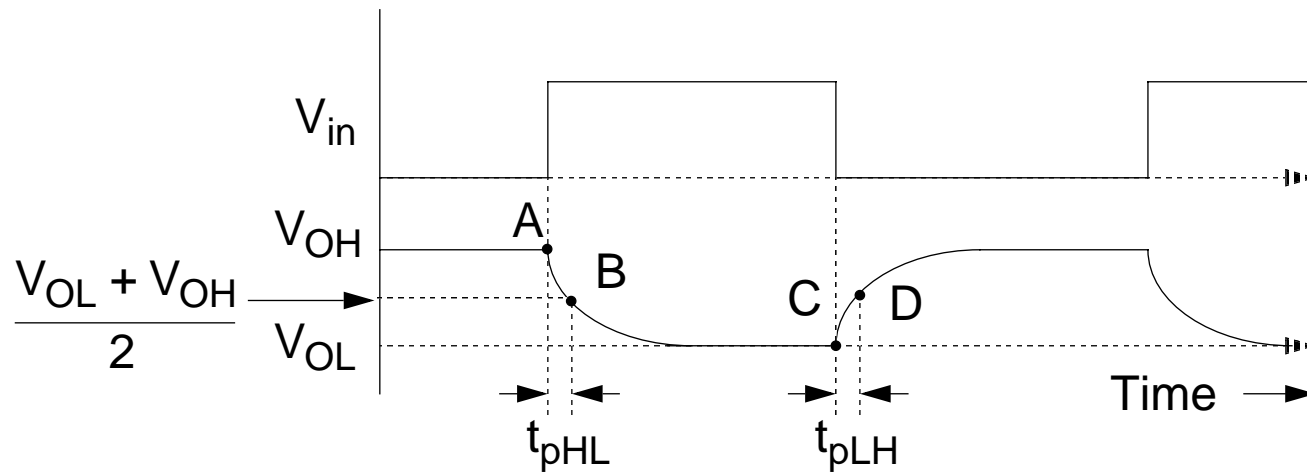- $$\Delta t = \frac{\Delta Q}{I_{\text{avg}}} = C_L \frac{\Delta V}{I_{\text{avg}}}$$




Propagation delay - t_{pHL}

 



- $$t_{pHL} = C_L \frac{\frac{1}{2}(V_{OH} - V_{OL})}{I_{avg}}, \quad I_{avg} = \frac{I_A + I_B}{2} .$$

Propagation delay - t_{pLH}

 

- $$t_{pLH} = C_L \frac{\frac{1}{2}(V_{OH} - V_{OL})}{I_{avg}}, \quad I_{avg} = \frac{I_C + I_D}{2} .$$

Inverter Switching

 
 


Inverter Rise/Fall Time

Simplifications:

$$t_f = k \frac{C_L}{\beta_n V_{DD}} = R_n C_L = \tau_f$$
  
$$t_r = k \frac{C_L}{\beta_p V_{DD}} = R_p C_L = \tau_r$$



Inverter Sizing


- Fall, Rise times:

$$\left(t_f = k \frac{C_L}{k_n \left(\frac{W}{L} \right)_n V_{DD}} \right), \left(t_r = k \frac{C_L}{k_p \left(\frac{W}{L} \right)_p V_{DD}} \right)$$

- To equalize rise, fall times:


$$(\mu_n = 2\mu_p) \Rightarrow \left(\left(\frac{W}{L} \right)_p \approx 2 \left(\frac{W}{L} \right)_n \right)$$

Inverter Sizing

 


$$t_f = t_r = 3RC$$

Transistor sizing: Cascaded inverters

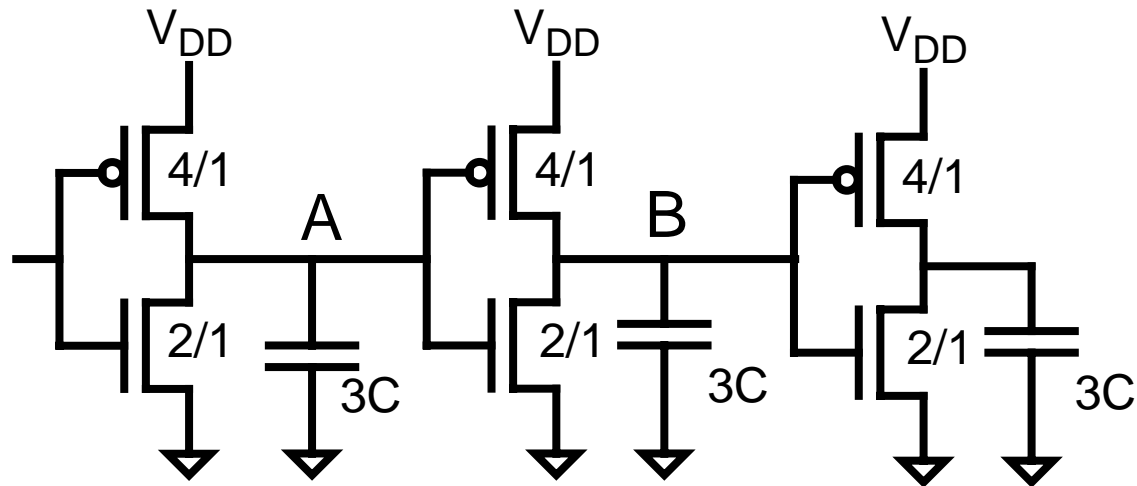


$$t_{dr} = t_{f1} + t_{r2}$$

$$t_{df} = t_{r1} + t_{f2}$$

 


Transistor sizing: Cascaded inverters

 - $t_{df} = R3C + R3C = 6RC$
 $t_{dr} = R3C + R3C = 6RC$



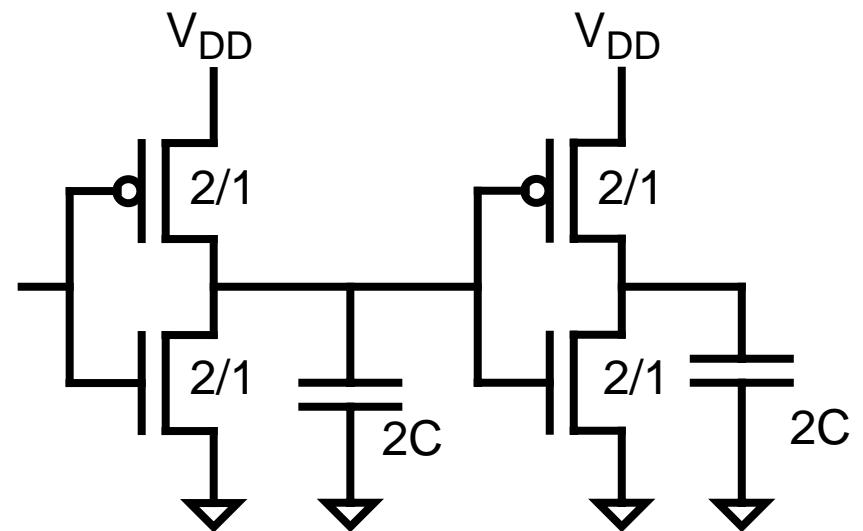
- $t_{df} = 2R2C + R2C = 6RC$
 $t_{dr} = R2C + 2R2C = 6RC$



Stage Ratios

 Problem:


Driving large load capacitances (long buses, I/O pads)



Solution:

Inverter chain with stage ratio $a = 2 - 5$

Stage Ratios

 

$$\begin{aligned}t_{dr} &= R(2aC) + \\ &\quad (2R/a)(2a^2C) + \\ &\quad (R/a^2)(2a^3C) + \\ &\quad (2R/a^3)(C_L) \\ &= 8RaC + 2RC_L/a^3\end{aligned}$$

$$C_L = 100 C$$

$$\text{for } a = 1, t_{dr} = 208RC$$


$$\text{for } a = 2, t_{dr} = 41RC$$

Sizing multi-input gates


$$t_f = k \frac{C_L}{\frac{\beta_n}{3} V_{DD}}$$

$$t_f = 3R_n C_L$$

$$t_r = R_p C_L$$

 


Sizing multi-input gates

 

$$t_f = R_n C_L$$

$$t_r = 3R_p C_L$$

Sizing complex gates

 

$$t_f = 3R_n C_L$$

$$t_r = 2R_p C_L$$