

3/29/21

DIGITAL FILTER IMPLEMENTATION

BUILDING A FILTER ...

(OSYP 6.0-6.5)


1. ESTABLISH SPECS

2. DEVELOP EQUATIONS
THAT MEET SPECS

(FILTER DESIGN, OSYP CHAP 2)

3. IMPLEMENT EGS. IN
HARDWARE OR SOFTWARE

(FILTER IMPLEMENTATION, OSYP CHAP 6)

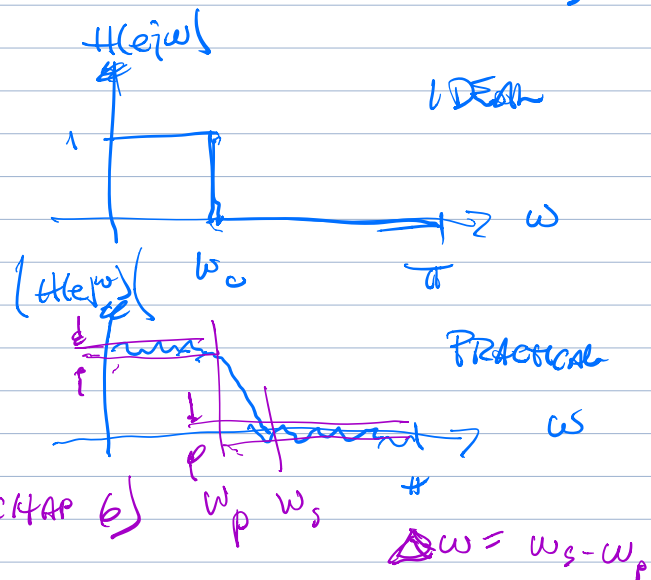

TWO FILTER TYPES

IIR - $h[n]$ RIGHT-SIDED, LEFT-SIDED, BOTH-SIDED

POLES + ZEROS

FIR - $h[n]$ FINITE DURATION

ZEROS ONLY EXCEPT FOR Z=0

ADVANTAGES of IIR FILTER

- * MOST EFFICIENT DESIGN TO REALIZE SPECS
- * DESIGN METHODS TO TRANSFORM GOOD CT FILTER DESIGNS INTO GOOD DT FILTER DESIGNS

ADVANTAGES of FIR FILTERS

- * ALWAYS STABLE
- * ALWAYS CAN BE LINEAR PHASE
- * CAN IMPLEMENT CONVOLUTION USING FFTS

SIGNAL FLOW NOTATION

ADDITION



MULT BY CONST.




UNIT DELAY



$$y[n] = \frac{1}{4} y[n-1] - \frac{1}{8} y[n-2] + 3x[n] - \frac{3}{4} x[n-1]$$

IIR IMPLEMENTATION
$$Y(z) \left(1 - \frac{1}{4} z^{-1} - \frac{1}{8} z^{-2} \right) = X(z) \left(3 - \frac{3}{4} z^{-1} \right)$$
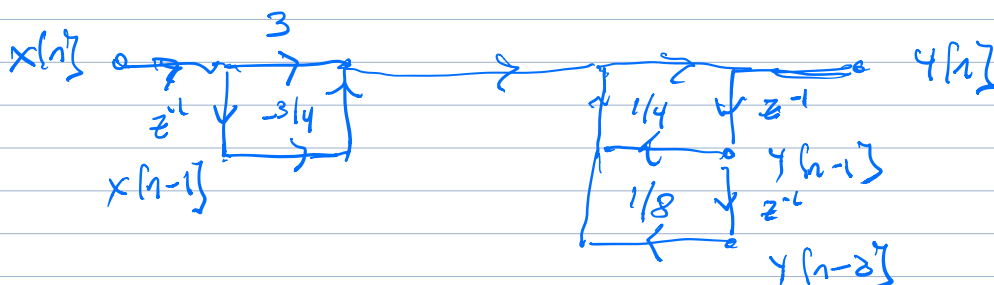
$$y[n] = \frac{1}{4} y[n-1] + \frac{1}{8} y[n-2] + 3x[n] - \frac{3}{4} x[n-1]$$





IN GENERAL,

$$H(z) = \frac{\sum_{l=0}^M b_l z^{-l}}{1 - \sum_{k=1}^N a_k z^{-k}} = \frac{Y(z)}{X(z)} = \frac{b_0 + b_1 z^{-1} + b_2 z^{-2} + \dots + b_M z^{-M}}{1 - a_1 z^{-1} - a_2 z^{-2} - \dots - a_N z^{-N}} = \frac{B(z)}{A(z)}$$

[OR $b_1 z^{-1} + a_1 z^{-1} + a_2 z^{-2} + \dots + a_N z^{-N}$]

$$y[n] = \sum_{k=1}^N a_k y[n-k] + \sum_{l=0}^M b_l x[n-l]$$

DIRECT
FORM I

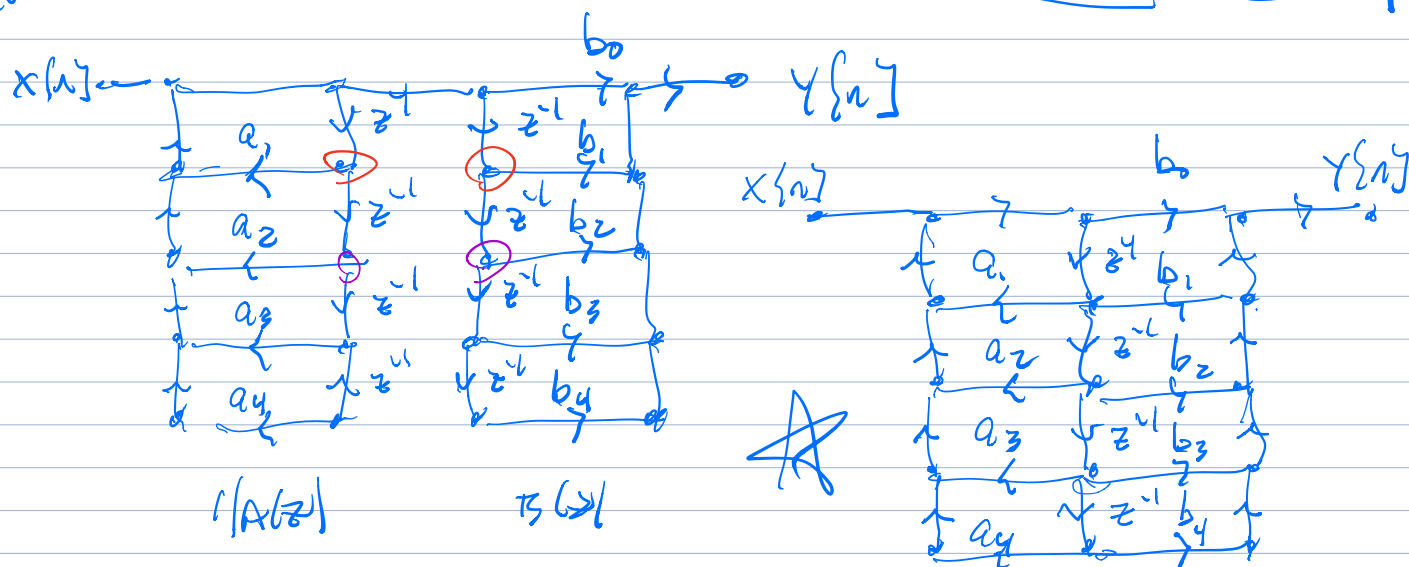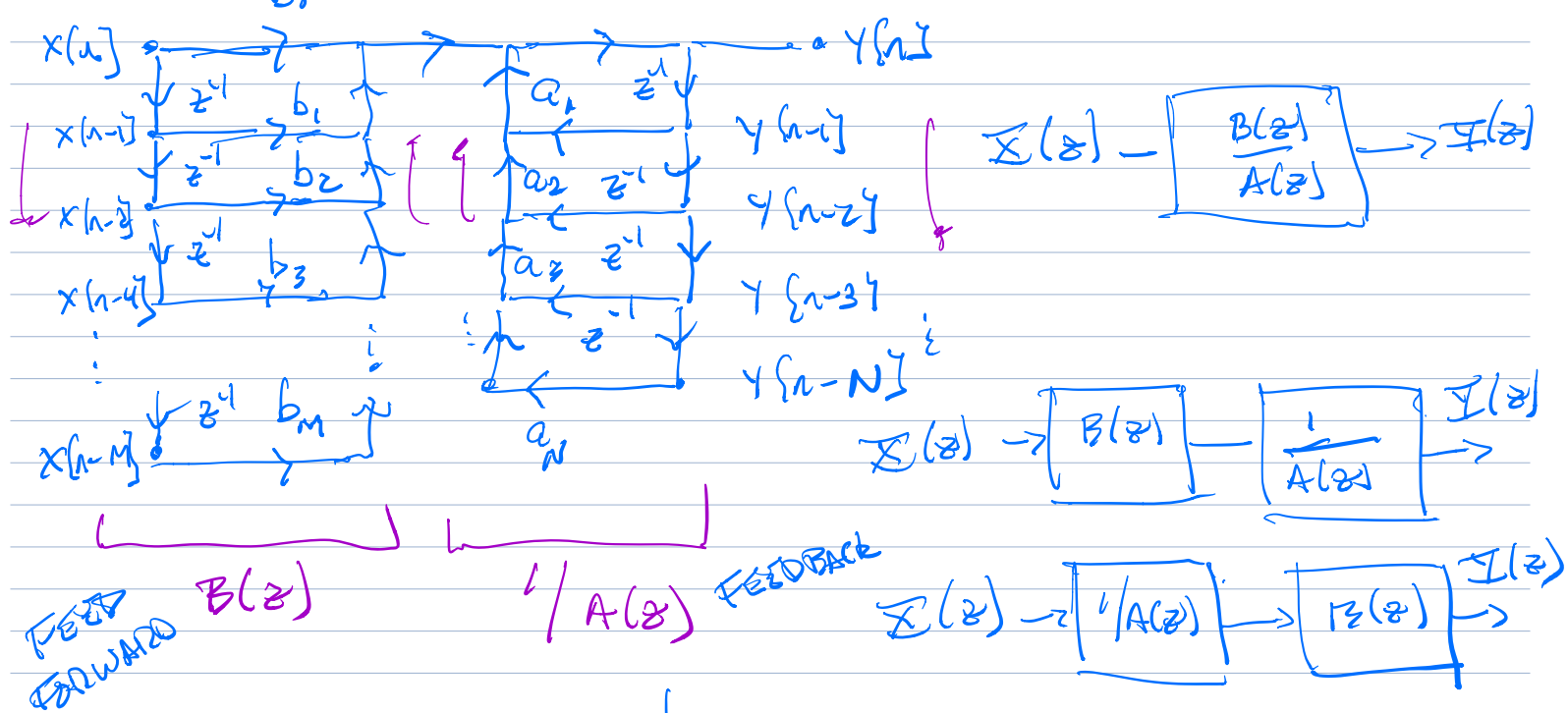

DIRECT FORM II

THE CANONICAL FORM

ALTERNATE FORMS

TRANSPOSED FORMS



NETWORK TRANSPOSITION
LEMMA (S. I. MASON)

IF



1. REVERSE ARROWS

2. INTERCHANGES INPUT

+ OUTPUT $\Rightarrow$ SAME TRANSFER FN.

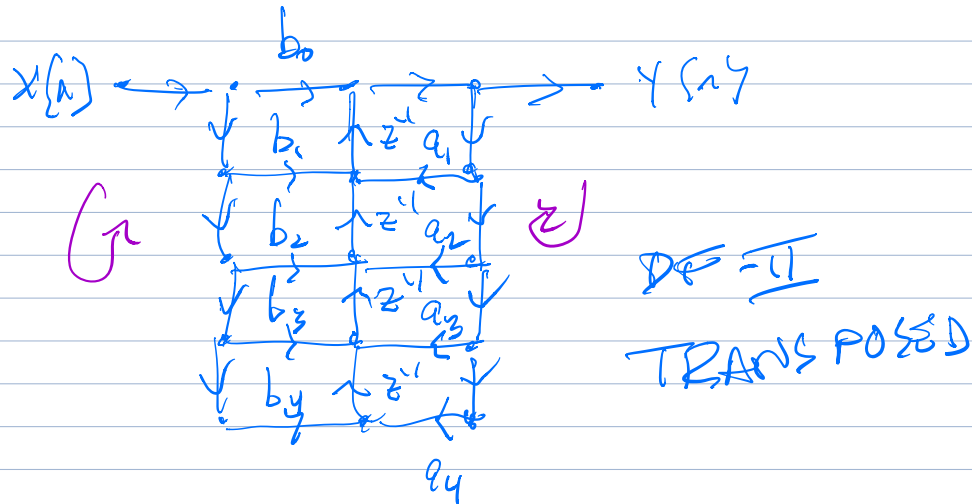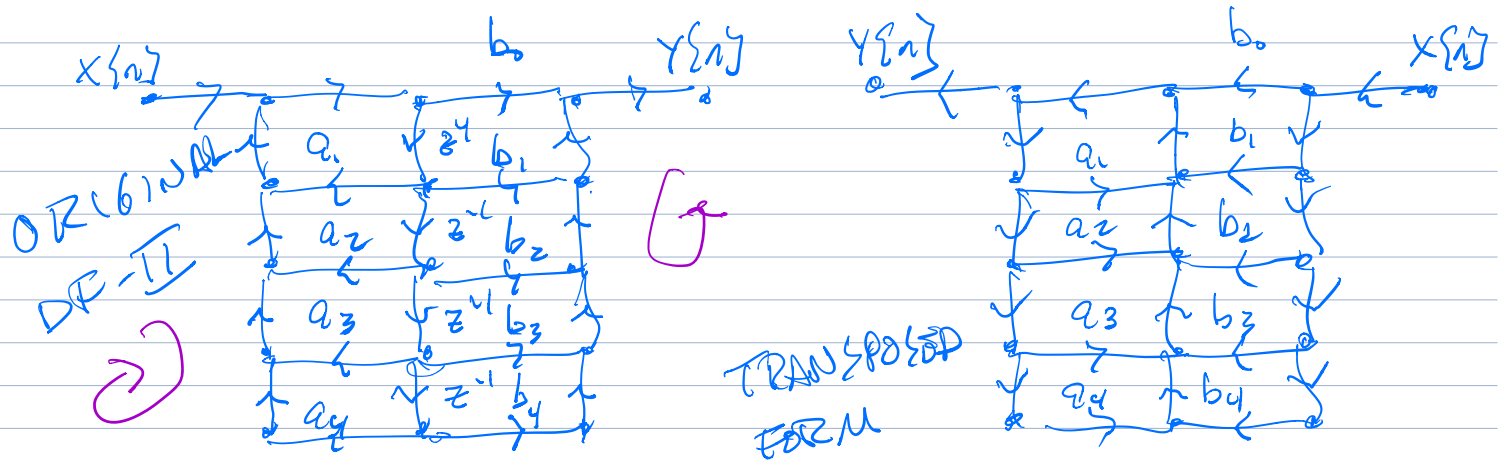

BREAKING $H(z)$ INTO SUBNETWORKS

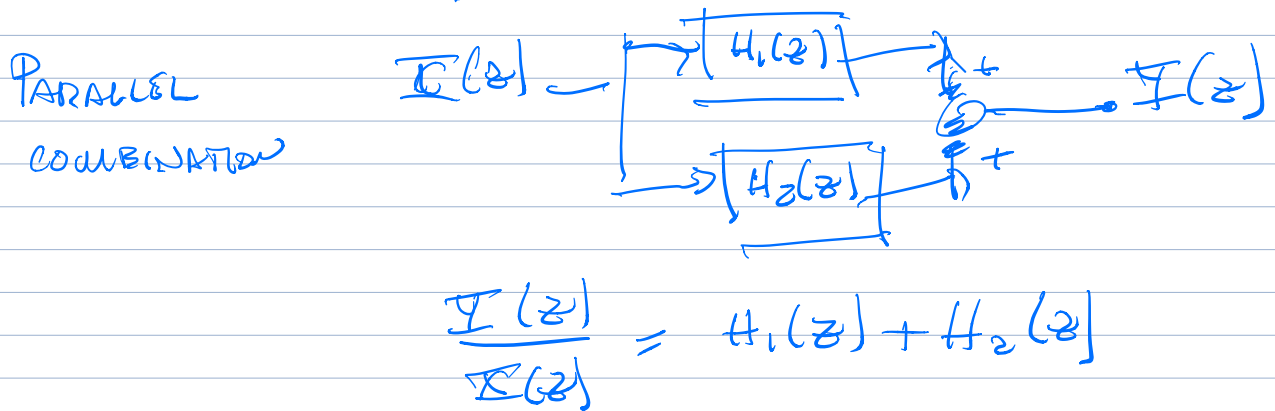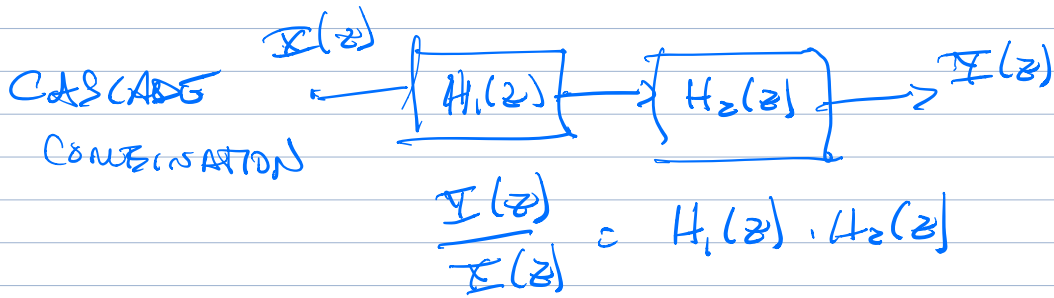

CASCADE FILTER FORM

$$H(z) = \frac{\sum_{l=0}^M b_l z^{-l}}{1 - \sum_{k=1}^N a_k z^{-k}} = \frac{b_0 \prod_{l=1}^M (1 - c_l z^{-1})}{\prod_{k=1}^N (1 - d_k z^{-1})}$$

$$= b_0 \prod_{k=1}^{\max(M, N)/2} \frac{b_{0k} + b_{1k} z^{-1} + b_{2k} z^{-2}}{1 - a_{1k} z^{-1} - a_{2k} z^{-2}}$$

CONSIDER Z-POLES $\odot d_k d_k^*$

$$(1 - d_k z^{-1})(1 - d_k^* z^{-1})$$

$$= 1 - z^{-1}(d_k + d_k^*) + z^{-2} d_k \cdot d_k^*$$

$$= 1 - z^{-1} 2\operatorname{Re}(d_k) + z^{-2} |d_k|^2$$

$$a_{1k} = 2\operatorname{Re}(d_k)$$

$$a_{2k} = -|d_k|^2$$

