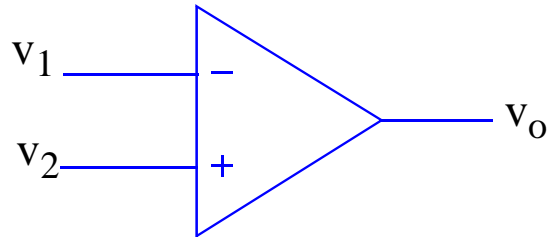


CMRR


- One important measure of the goodness of an opamp or an opamp circuit is the **common mode rejection ratio** (CMRR)
- Ideally, opamps are expected to amplify the differences between v_1 and v_2 with nearly infinite gain
- Due to transistor nonidealities, some small amount of amplification occurs due to the **common signal** of both inputs

open
loop
gain



$$A = \frac{v_o}{v_2 - v_1}$$

common
mode
gain

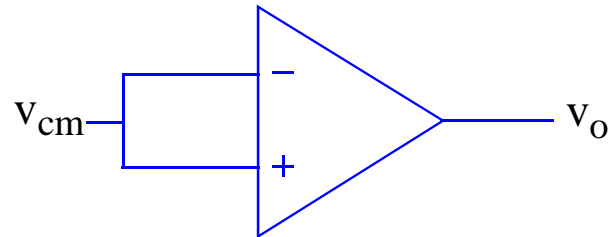

$$A_{cm} = \frac{v_o}{v_{cm}}$$


$$CMRR = \frac{A}{A_{cm}}$$

CMRR

- We would like to have an infinite CMRR

$$v_{id} = v_2 - v_1$$


$$v_{Icm} = \frac{v_2 + v_1}{2}$$

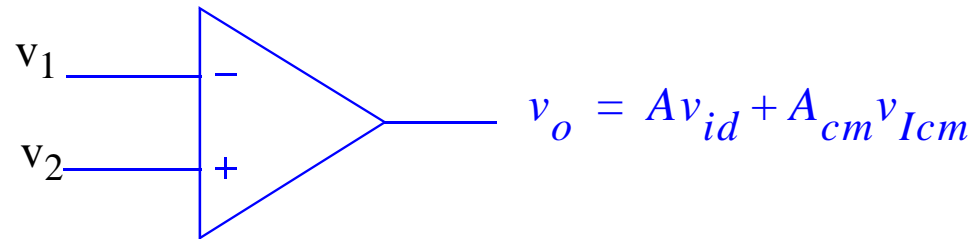


- A typical CMRR is 80-100dB at low frequency
- Would the CMRR improve, or get smaller with increasing frequency?

CMRR

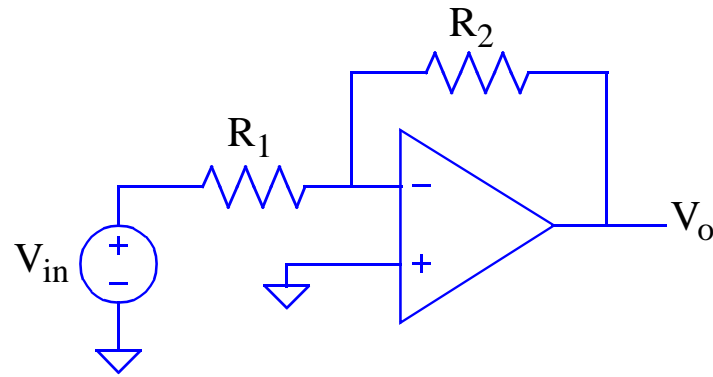- Not really a problem for inverting amplifier configurations --- why?




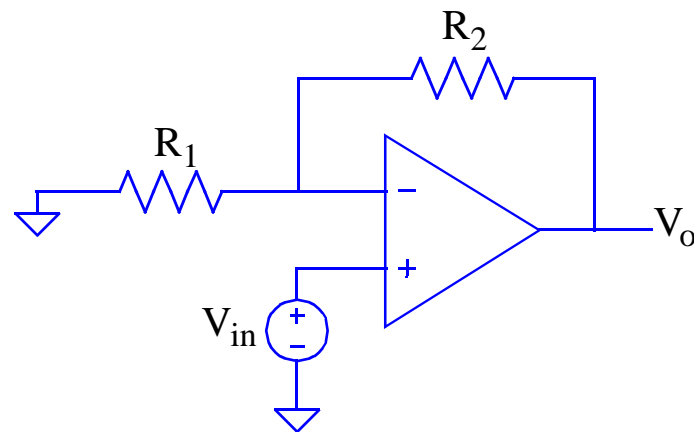- But definitely a problem for noninverting amplifier configurations --- why?




Difference Amplifier

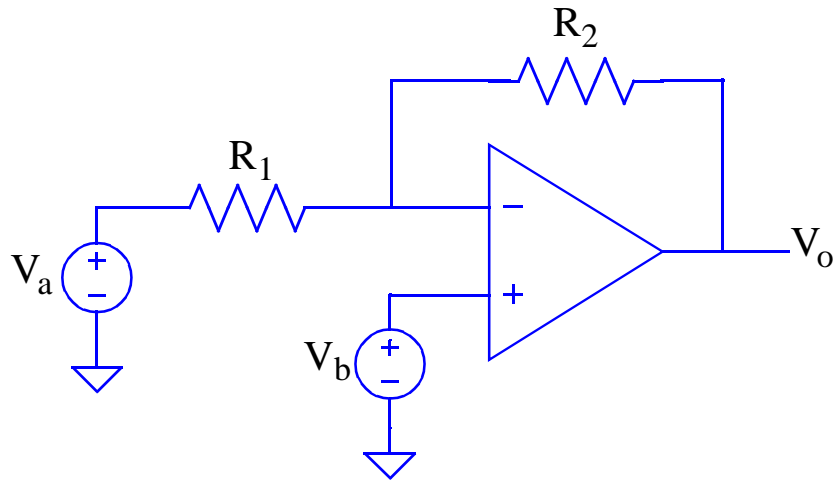- Also a problem for difference amplifiers




Difference Amplifier

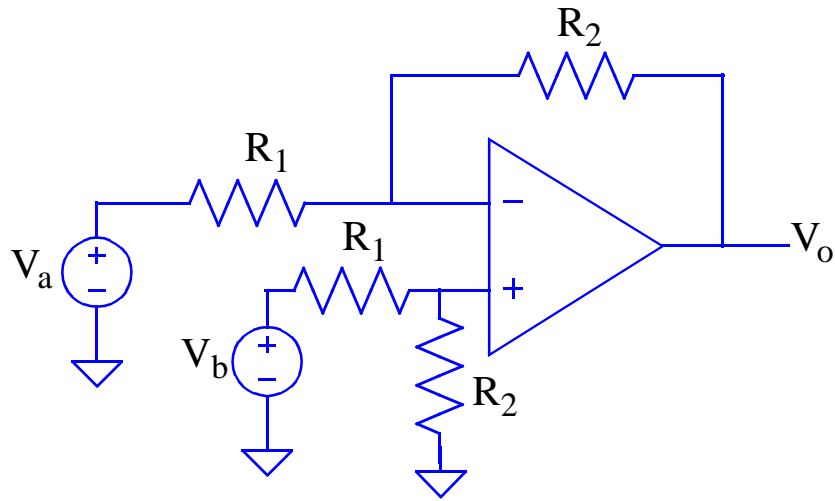- We have to scale the voltage v_b to achieve balanced amplification of $v_b - v_a$



CMRR

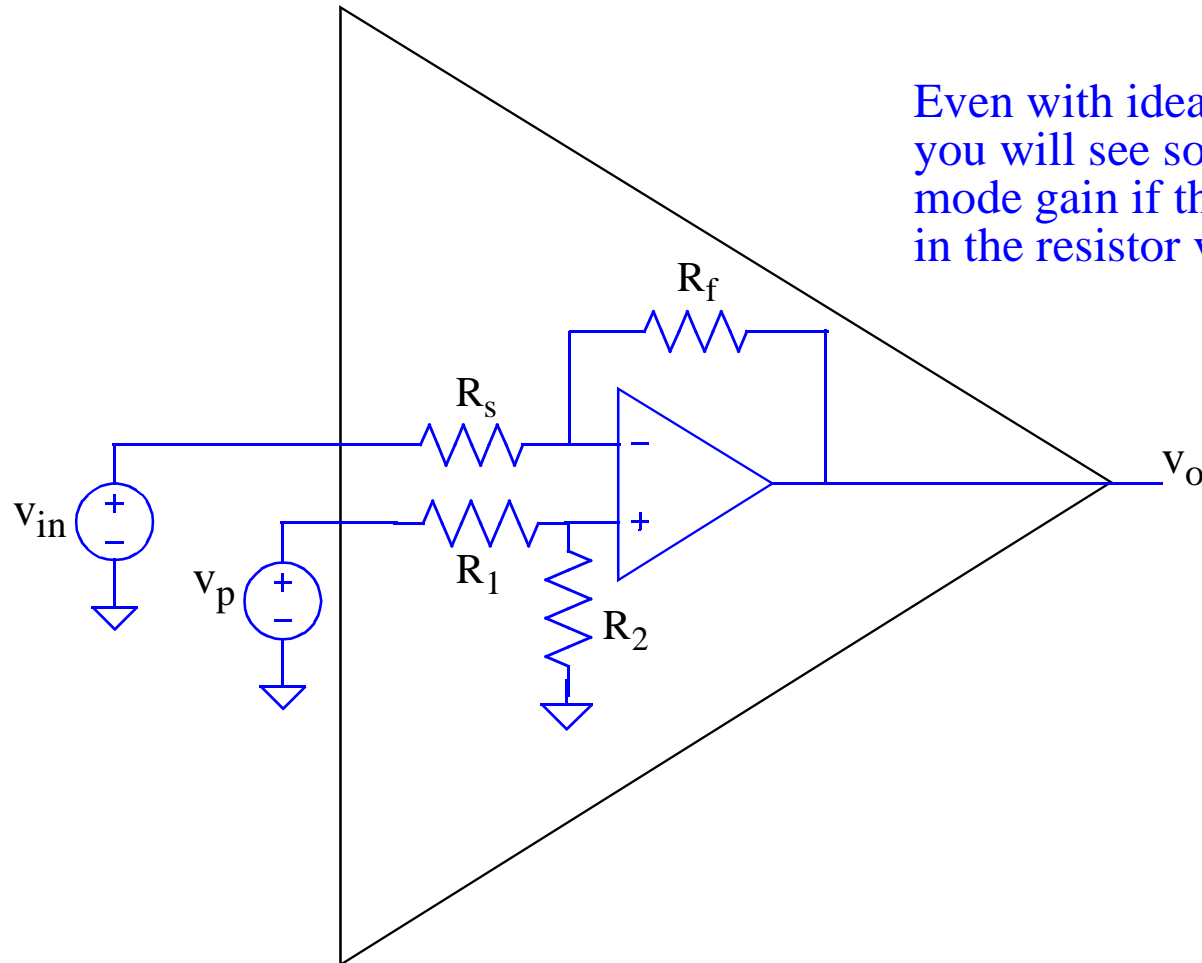
- Opamp data sheets specify the CMRR for the opamp itself, but the opamp differential amplifier circuit also has a CMRR





Even with ideal opamp model you will see some common mode gain if there is a mismatch in the resistor values

Input-Currents and -Resistances

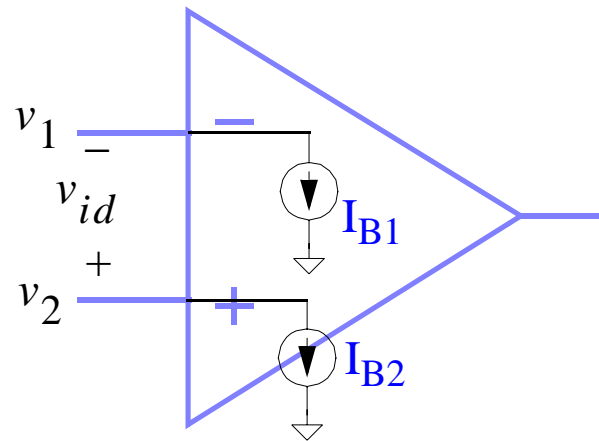- There is some small dc current flowing into/out of the inputs at all times -- **input bias current**




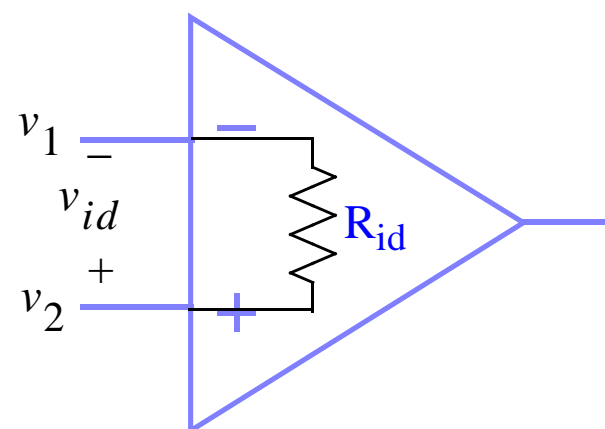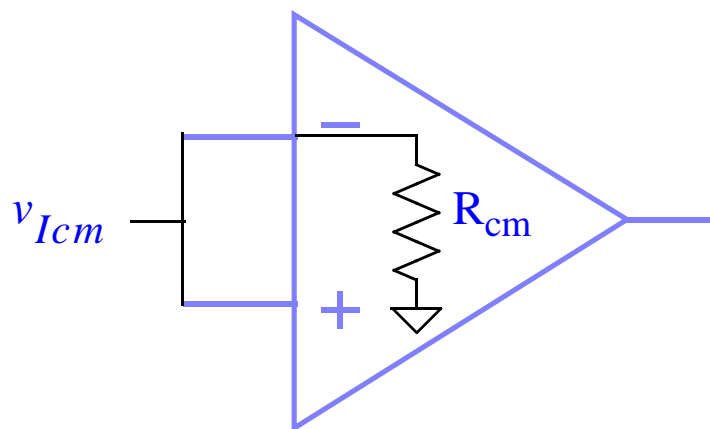- There is also a component of input current that changes with input voltage (both common mode and differential) --- **input resistances**




Input Resistance

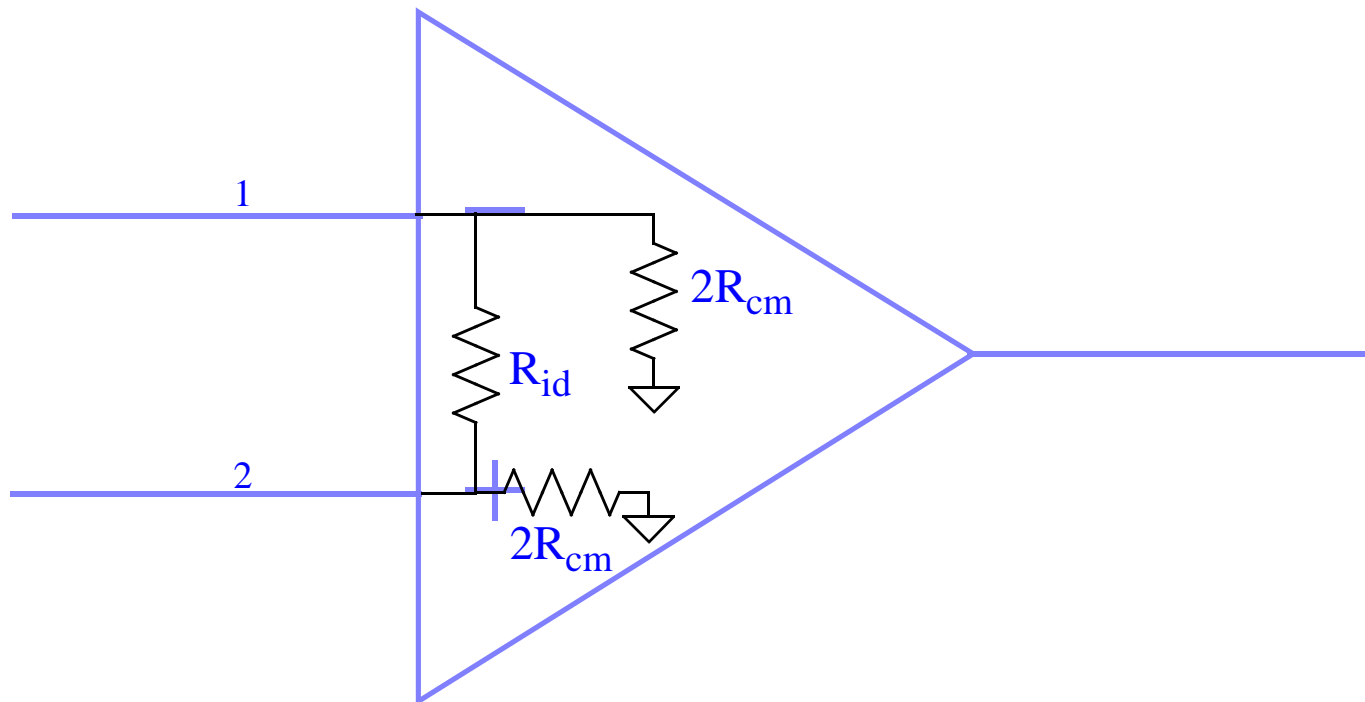- These resistances are generally quite large: $R_{cm} \sim 100M\Omega$, and $R_{id} \sim 1M\Omega$
- These resistances are even larger for MOS opamps




Input Resistance

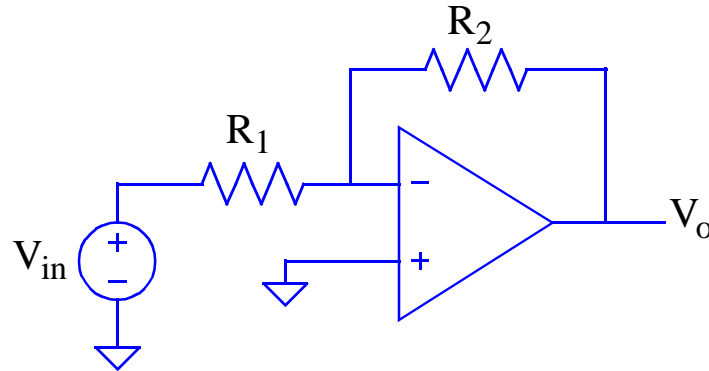- These opamp input resistances do not affect an inverting amplifier configuration as long as R_1 is much less than R_{id} and R_{cm}




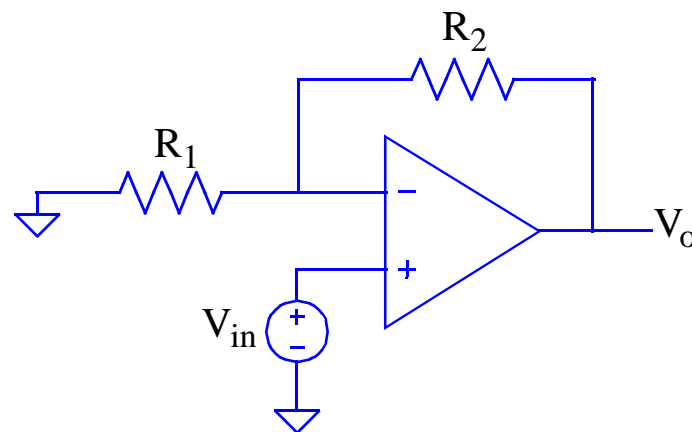- But these resistances are what determines the input resistance of a non-inverting amplifier configuration




Input Resistances

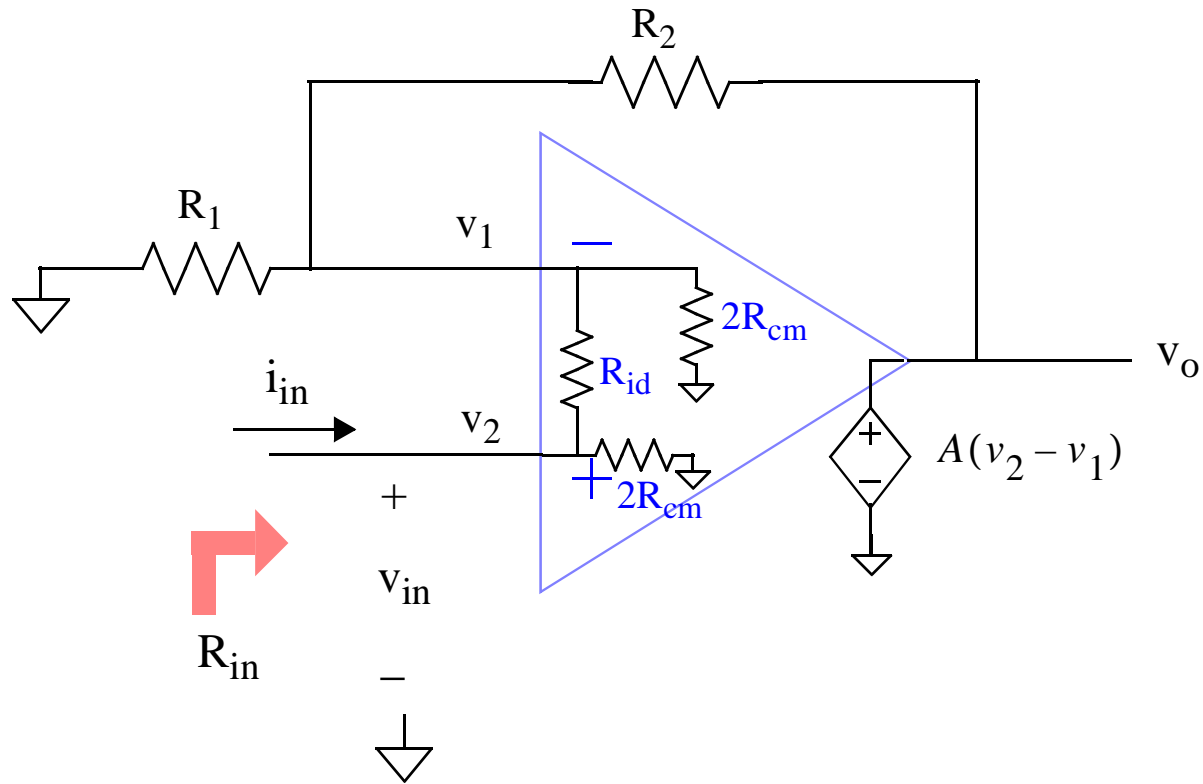- The resistors R_1 and R_2 should be kept significantly smaller than the input resistances for the gain to be close to ideal




Input Resistances

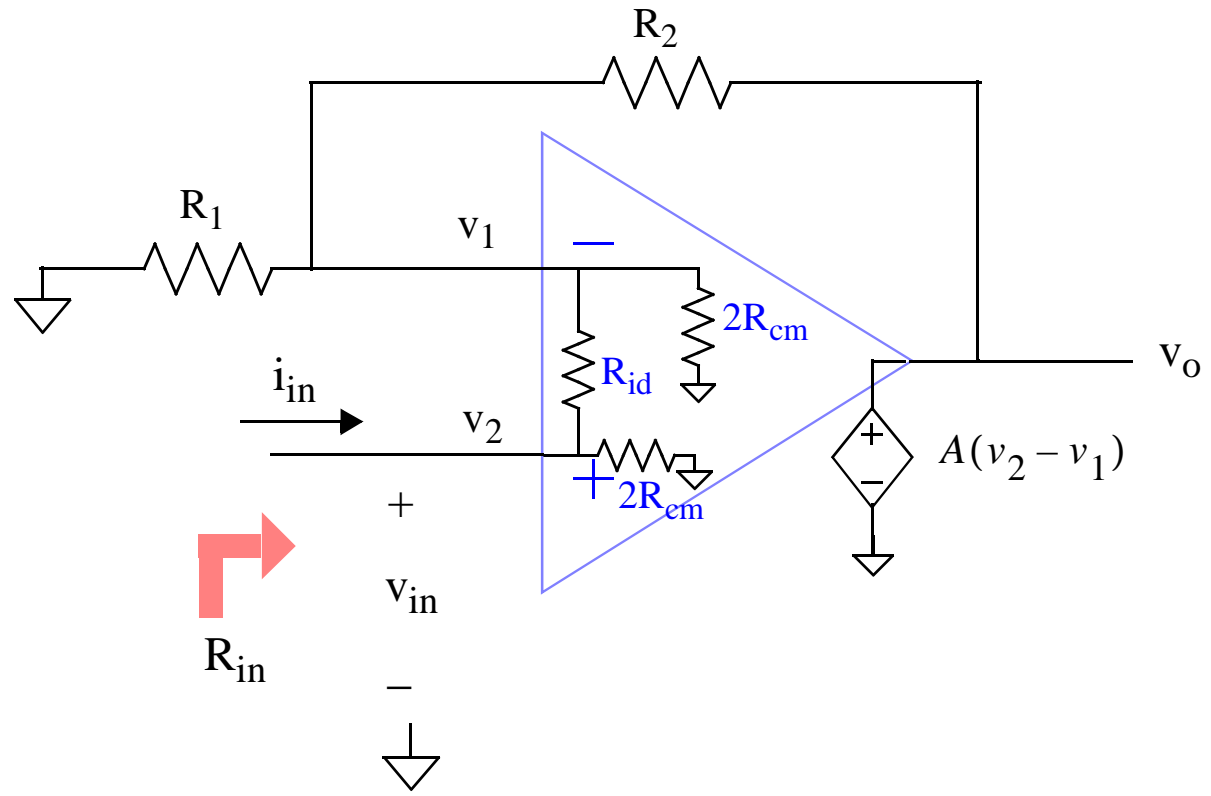


Nonzero Output Resistance

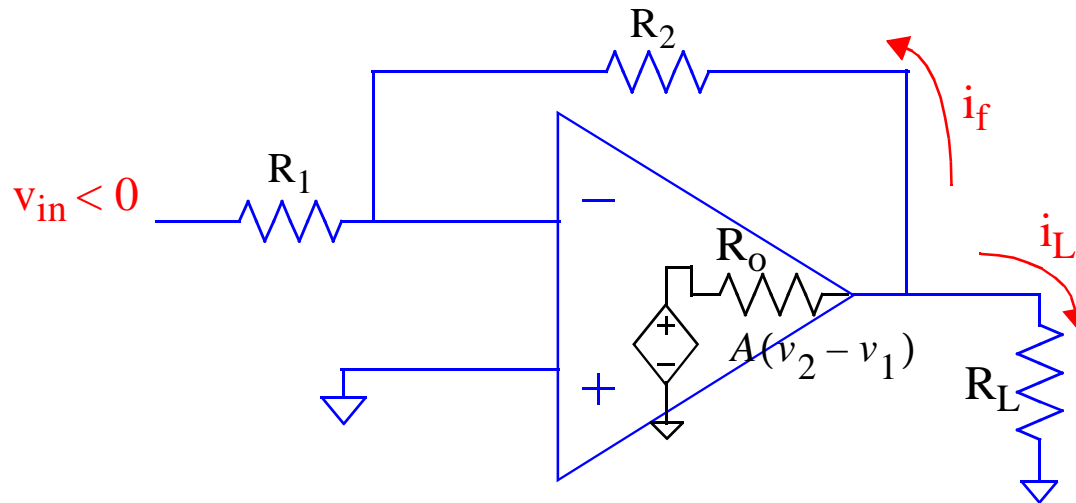- We also have to keep in mind that the opamp output cannot source an infinite amount of current --- so we can't drive arbitrarily small resistance loads
- This is modeled by an output resistance, R_o



note that v_o
definition is
changed when
output resistance
is added to
the model

Measuring Output Resistance

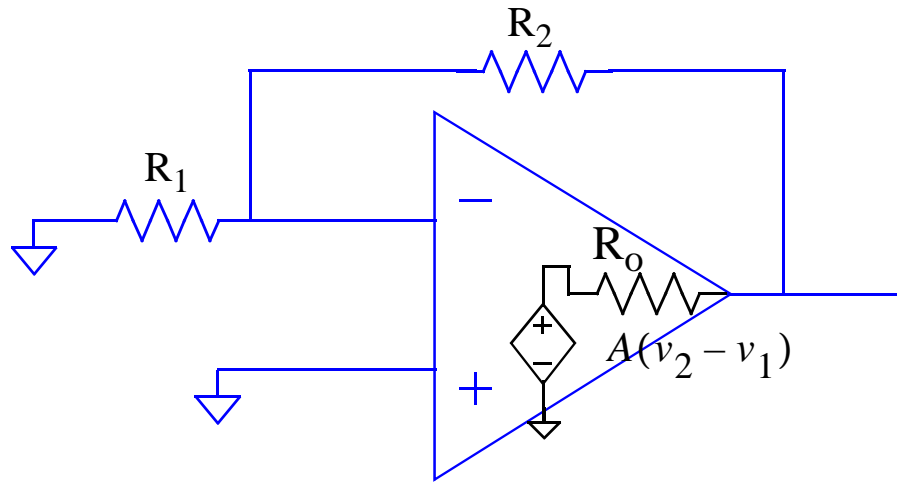


Modeling Output Resistance

- Since the open loop gain depends on frequency, so does the opamp circuit output impedance


Input Bias Current

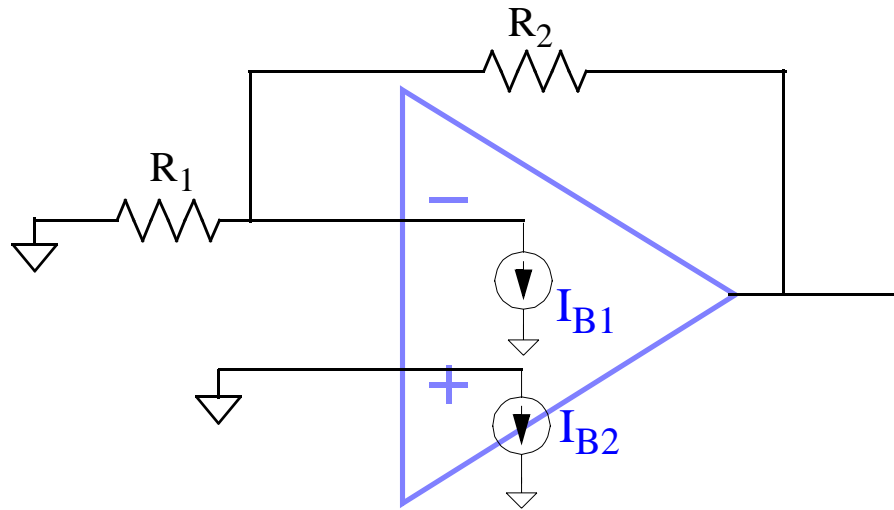- The input bias current is not frequency dependent, but can cause an unwanted dc output response




Compensating for I_B

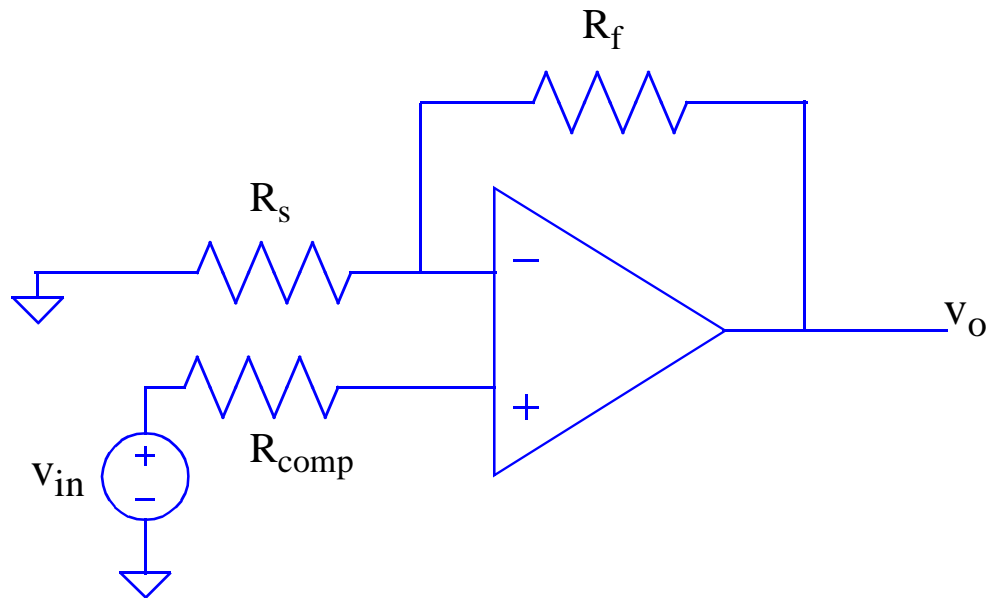- In practice, a resistor is added so that the bias current drops are compensated properly between the two ports




Compensating for I_B

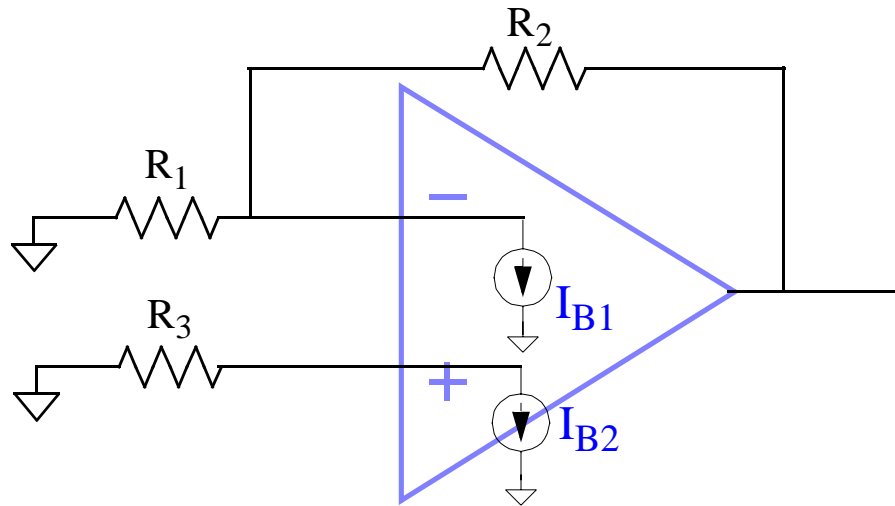


dc Offset Voltage

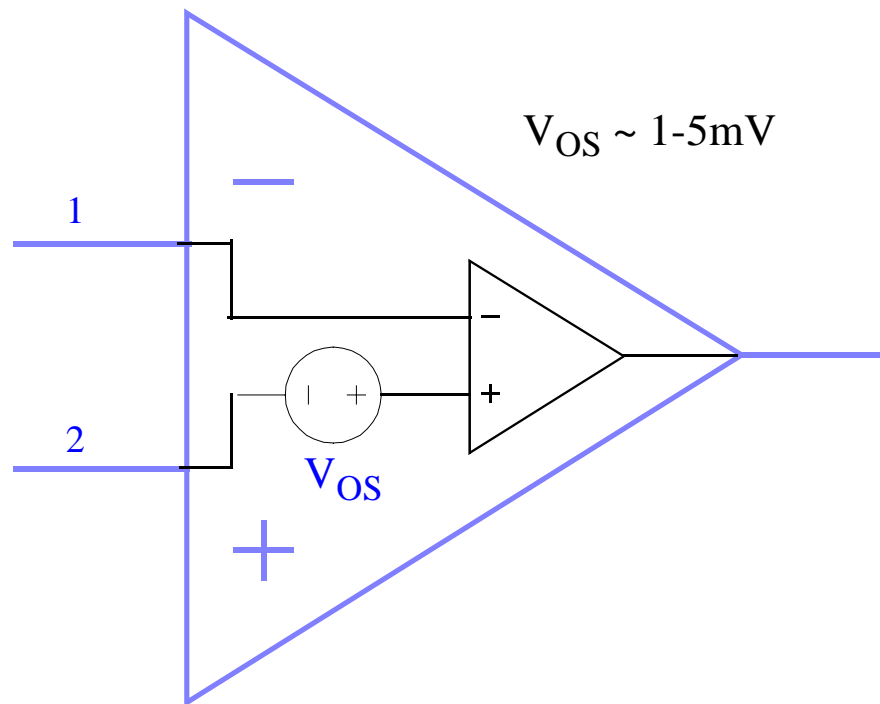- Another unwanted dc output signal is due to the **dc offset voltage**
- A dc differential input is required for a real opamp to zero the output
- This offset is due to mismatch in transistor parameters, and is temperature dependent --- more on this later in the course



dc Input Offset Voltage

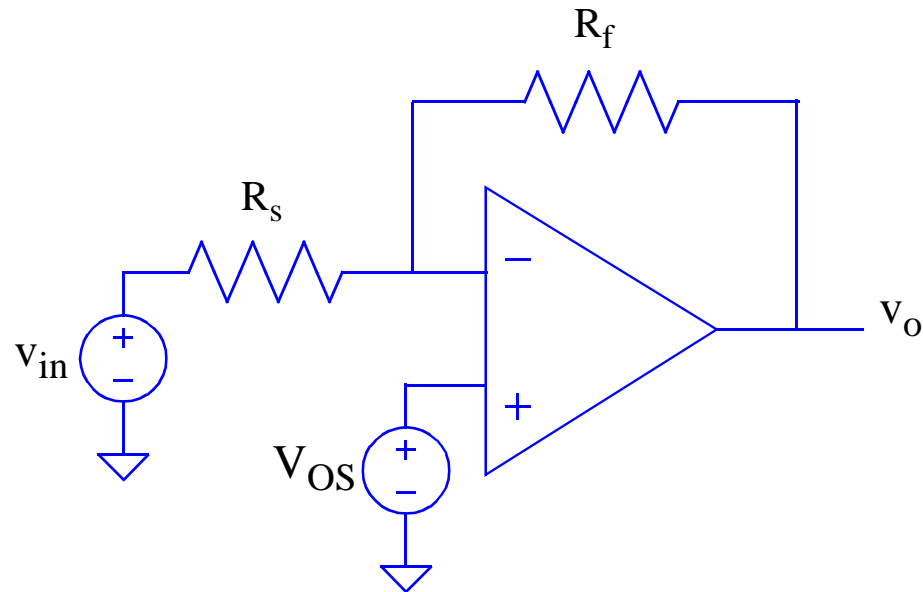- Calculate output voltage due to dc input offset voltage



ac Coupling

- We can avoid this offset voltage at the output by using ac coupling

